

# CLASS NOTES OF “FUNDAMENTALS OF ELECTRICAL AND ELECTRONIC ENGG”



## Technical Classes

✓ Technical Classes के Course में उपलब्ध फीचर्स

1. सभी कक्षाएं स्मार्ट बोर्ड पर Live
2. विशेषज्ञ शिक्षको द्वारा पठन पाठन
3. Lecture के दौरान डाउट सॉल्विंग
4. Recorded Lecture (VOD)
5. प्रत्येक क्लास का PDF नोट्स
6. SBTE Exam की तैयारी के लिए ब्रह्मास्त्र क्लास
7. Laptop में क्लास देखने की सुविधा

Call/WhatsApp - 93347 89450 / 91555 63777

नोट :-

1. सभी ऑफलाइन कक्षाएं Technical Classes के कैंपस तथा सभी ऑनलाइन कक्षाएं Technical Classes के एप्लीकेशन पर चलेगी।
2. यह नोट्स टेक्निकल क्लासेस के स्टूडेंट्स के लिए है, तथा क्लास करने के बाद अधिक प्रभावी होगा।

By Er. Anirudh Sir

- I) **Course Curriculum Detailing:** This course curriculum detailing depicts learning outcomes at course level and session level and their attainment by the students through Classroom Instruction (CI), Laboratory Instruction (LI), Term Work (TW) and Self Learning (SL). Students are expected to demonstrate the attainment of Theory Session Outcomes (TSOs) and Lab Session Outcomes (LSOs) leading to attainment of Course Outcomes (COs) upon the completion of the course. While curriculum detailing, NEP 2020 related reforms like Green skills, Sustainability, Multidisciplinary aspects, Society connect, Indian Knowledge System (IKS) and others must be integrated appropriately.

J) **Theory Session Outcomes (TSOs) and Units:T2420103**

Major Theory Session Outcomes (TSOs)		Units	Relevant COs Number(s)
TSO.1a	Apply the concept of charge, voltage and current in the given electrical circuit	<b>Unit-1.0 Basic Electrical Parameters and Concepts</b>  1.1 Electric charge, flow of charges, Electric Current D.C and A.C, Concept of ideal and practical current sources 1.2 Analogy of charge, potential /Voltage difference D.C and A.C, Induced emf/voltage, Terminal voltage, Concept of Ideal & Practical voltage sources 1.3 Resistor - Properties, Classification, Practical application of resistors, Effect of temperature on resistance, Series and parallel combination of resistors, Phase difference 1.4 Heating, magnetic and chemical effect of current, Electrical work, Power and energy, Open and short circuit condition of electric circuit 1.5 Capacitors – Properties, Capacitance formation, Expression for capacitance, Capacitive reactance, Energy stored in capacitor, Series & parallel combination of capacitors, Types of capacitors including super capacitors and their applications 1.6 Inductors – Properties, Self and mutual inductance, inductive reactance, Voltage and current equations of inductor, Energy stored in inductor, Inductance in A.C. and D.C. circuits, Types of Inductors including MEMS inductor and their applications	CO-1
TSO.1b	Differentiate between AC and DC currents.		
TSO.1c	Differentiate between practical and Ideal current/voltage source		
TSO.1d	Calculate work, power, and energy in the given circuit		
TSO.1e	Calculate the equivalent resistance/Capacitance/ inductance in the given series and parallel electric circuit.		
TSO.1f	Explain the heating/magnetic/chemical effect of the electric current with a relevant application.		
TSO.1g	Calculate the energy stored in a given resistor/capacitor/inductor.		
TSO.1h	Explain the effect of various media on capacitance		
TSO.1i	Explain behavior of current in a resistor/capacitor/inductor.		
TSO.2a	Differentiate between- • AC and DC current in all aspects (Generation, Waveforms and applications) • Active and passive elements • Linear & Non-linear circuit • Unilateral and Bilateral circuit • Loop and mesh in a given circuit	<b>Unit-2.0 Fundamentals of D.C. and A.C. Circuits</b>  <b>DC Circuits</b> 2.1 AC and DC current, voltage and Power 2.2 Ohm's law, Kirchhoff's Current Law, Kirchhoff's Voltage law 2.3 Active & Passive elements, Linear & Non-linear circuit, unilateral and Bilateral circuit element, 2.4 Node, Branch, Loop, Mesh <b>A.C Circuits</b> 2.5 Frequency, Time period, Amplitude, Angular Velocity, RMS Value, Average Value, Form factor, Peak factor, Power factor 2.6 Phasor representation and transformation from Polar to rectangular form and vice versa of alternating quantities	CO1, CO2
TSO.2b	Apply Ohm's law and Kirchhoff's laws to determine current and voltage in a given circuit.		
TSO.2c	Explain various AC fundamental parameters.		
TSO.2d	Use operator 'j' to calculate various quantities in A.C circuit		



Major Theory Session Outcomes (TSOs)	Units	Relevant COs Number(s)
TSO.3a Explain various terms related to magnetic circuit. TSO.3b Calculate various parameters of a given magnetic circuit. TSO.3c Plot B-H curve and Hysteresis loop of a given magnetic materials TSO.3d Explain the phenomenon of induced e.m.f and current TSO.3e Apply principles of Faraday's law to calculate induced e.m.f in the given circuit TSO.3f Apply various Laws in a given magnetic circuits	<b>Unit-3.0 Magnetic Circuits and Electromagnetic Induction</b>  3.1 Magnetic flux, Magnetomotive force, Magnetic field strength, Permeability, Reluctance. 3.2 Magnetic leakage, leakage coefficient 3.3 Magnetic Hysteresis, Hysteresis loop, 3.4 Magnetization (B-H) Curve 3.5 Analogy between electric and magnetic circuits 3.6 Electromagnetism 3.7 Induced e.m.f -Statically (self and mutual) and dynamically induced emf, 3.8 Faraday's Laws of electromagnetic Induction. 3.9 Lenz's Law, Fleming's R.H. rule; direction of induced E.M.F, Fleming's L.H. rule, Ampere's Law	CO2, CO3
TSO.4.a Describe the construction and working principle of the given type of semiconductor TSO.4.b Describe the principle of the given type of semiconductor. TSO.4.c Describe between the given type insulator, conductor and semiconductor based on energy band theory. TSO.4.d Describe working principle, characteristics and application of the given type of diode. TSO.4.e Describe working principle of the given type of Bipolar Junction Transistor. TSO.4.f Describe working principle of the given type of Field Effect Transistor.	<b>Unit-4.0 Basic Electronic Components</b>  4.1 Semiconductors: Definition, types of semiconductors and their materials. Energy band theory and effect of temperature. 4.2 Diodes: Basic Concept of Diodes, N-type & p-type PN Junction Diode – Forward and Reverse Bias Characteristics i.e., PN junction Barrier voltage, depletion region, Junction Capacitance. Forward biased & reversed biased junction, Diode symbol 4.3 Bipolar Junction Transistor (BJT): NPN and PNP Transistor – Operation and characteristics. symbol 4.4 Field Effect Transistor (FET): FET – Operation and characteristics, Classification FET and advantages, FET symbol	CO4
TSO.5a Convert one number system to other number system. TSO.5b Use Boolean Algebra to solve expressions TSO.5c Implement Boolean expressions for given logic gates	<b>Unit-5.0 Overview of Digital Electronics</b>  5.1 Introduction to different Number systems: Binary, Octal, Decimal & Hexadecimal & their Conversion from one another 5.2 Introduction to Boolean Algebra, rules and Laws of Boolean Algebra – DE Morgan's Law 5.3 Study of logic gates (NOT, OR, NOR, AND, NAND) Symbolic representation, Truth Table and Implementation of Boolean expressions	CO4, CO5

**Note:** One major TSO may require more than one Theory session/Period.

Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24



# Charge

Charge is the inherent [Physical] property of material

Which experience force on itself or another body.

It is denoted by 'Q' or 'q'

It's Unit is Coulomb [C]

There are two types of Charge:-

TECHNICAL CLASSES

## Charges

+ve Charge

-ve Charge

+ve Charge is carried by Proton

-ve Charge is carried by electron.

Proton has  $+1.6 \times 10^{-19} \text{ C}$

Electron has  $-1.6 \times 10^{-19} \text{ C}$

→ In Any atom, No. of Protons is equal to No. of electrons  
So Atom is electrically neutral.

E.g:- Na → 11

No. of Protons in Na = 11 Charges →  $+1.6 \times 10^{-19} \times 11$

+ No. of electrons in Na = 11 Charges →  $-1.6 \times 10^{-19} \times 11$

Total Charges =  $(+1.6 \times 10^{-19} \times 11) - 1.6 \times 10^{-19} \times 11 = 0$





\* Electron jumps from lower energy band to higher energy band, when electron absorbs energy.



Electron jumps from higher energy level to lower energy level then electron releases energy.


TECHNICAL CLASSES



In a Sodium atom one electron releases then remaining No. of electrons = 10.



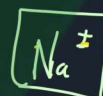While No. of Proton = 11 Charges  $\rightarrow +1.6 \times 10^{-19} \text{ C} \times 11$   
 10 electrons Charges  $\rightarrow -1.6 \times 10^{-19} \text{ C} \times 10$



$$\text{Total Charges} = (+1.6 \times 10^{-19} \text{ C} \times 11) + (-1.6 \times 10^{-19} \text{ C} \times 10) \\ + 1.6 \times 10^{-19} \text{ C} (11 - 10) = +1.6 \times 10^{-19} \text{ C} \times 1$$

Revision




No. of Protons = 12 Charges  $\rightarrow +1.6 \times 10^{-19} \text{ C} \times 12$

No. of electrons = 12 - 2 = 10 Charges  $\rightarrow -1.6 \times 10^{-19} \text{ C} \times 10$

$$\text{Total Charges} = (+1.6 \times 10^{-19} \text{ C} \times 12) + (-1.6 \times 10^{-19} \text{ C} \times 10)$$

$$= +1.6 \times 10^{-19} \text{ C} (12 - 10)$$
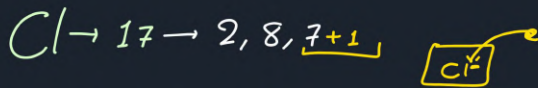
$$= +1.6 \times 10^{-19} \text{ C} \times 2 \quad \text{Mg}^{++}$$



No. of Proton = 17  $\xrightarrow{\text{Charges}}$   $+1.6 \times 10^{-19} \text{ C} \times 17$

No. of electron = 17  $\xrightarrow{\text{Charges}}$   $-1.6 \times 10^{-19} \text{ C} \times 17$

Total Charge =  $+1.6 \times 10^{-19} \text{ C} \times 17 - 1.6 \times 10^{-19} \text{ C} \times 17$   
 $= +1.6 \times 10^{-19} \text{ C} (17 - 17)$   
 $= +1.6 \times 10^{-19} \text{ C} \times 0 = 0$

One electron adds in Cl-atom.

total No. of  $e = 18$

No. of Proton = 17  $\xrightarrow{\text{Charges}}$   $+1.6 \times 10^{-19} \text{ C} \times 17$

No. of electron = 18  $\xrightarrow{\text{Charges}}$   $-1.6 \times 10^{-19} \text{ C} \times 18$

Total Charge =  $+1.6 \times 10^{-19} \text{ C} \times 17 - 1.6 \times 10^{-19} \text{ C} \times 18$   
 $= +1.6 \times 10^{-19} \text{ C} (17 - 18)$   
 $= +1.6 \times 10^{-19} \text{ C} \times -1$   
 $= -1.6 \times 10^{-19} \text{ C}$

TECHNICAL CLASSES

Charge is created on atom by Gaining or losing electron

Loss of electron  $\rightarrow$  +ve Charge

Gain of electron  $\rightarrow$  -ve Charge

Charge

+ve Charge

+ve Charge is Carried by Proton

$P = +1.6 \times 10^{-19} \text{ C}$

-ve Charge

-ve Charge is Carried by electrons.

$e = -1.6 \times 10^{-19} \text{ C}$

★ When electron removes from matter then +ve Charge is created.

★ When electron enters in atom then -ve Charge is created.



Diagram showing a box with two arrows pointing outwards, labeled  $+1.6 \times 10^{-19} C$ .

$q = 1.6 \times 10^{-19} C$

If 1 electron removes  $= +1.6 \times 10^{-19} C \times 1 = 1e$   
 2 electrons removes  $= +1.6 \times 10^{-19} C \times 2 = 2e$   
 3 electrons removes  $= +1.6 \times 10^{-19} C \times 3 = 3e$   
 $+ne$

Diagram showing a box with one arrow pointing inwards, labeled  $e$ .

If 1 electron enters  $= -1 \times 1.6 \times 10^{-19} C$   
 If 2 electrons enter  $= -2 \times 1.6 \times 10^{-19} C$   
 ...  
 $= -ne$


# TECHNICAL CLASSES

## → Quantisation of Charge:-

Charge on any material is integral multiple of ' $e$ '

i.e.  $q = \pm ne$

Diagram showing a box with one arrow pointing outwards, labeled  $e$  and  $1e$ .

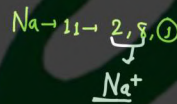

$\therefore 1e = -1.6 \times 10^{-19} C$

$1C = 625 \times 10^{16} \text{ electrons}$

$1.6 \times 10^{-19} C = 1e$

$1C = \frac{1}{1.6 \times 10^{-19}} e$

$1C = \frac{10}{1.6} \times 10^{19} e$

$1. \frac{10}{1.6} \times 10^{19} = 625 \times 10^{16} \text{ electrons}$

4)  $\frac{250}{24} \frac{625}{10} \frac{1}{1.6} \frac{10^{19}}{10^{19}} = 625 \times 10^{16}$

$\frac{1.6 \times 10^{-19} C}{1.6 \times 10^{-19} C} = 1e$

$1C = \frac{1}{1.6 \times 10^{-19}} e$

$1C = \frac{10}{1.6} \times 10^{19} e$

$1C = \frac{10 \times 10^{19}}{1.6} e$



\* Charge:-

\* Current:-




→ Charges flow per unit time is called Electric current.

$$I = \frac{q}{t} \rightarrow \frac{1C}{1sec} = \frac{62.5 \times 10^{16} \text{ electrons}}{Sec}$$

→ Current is the flow of free electrons.

TECHNICAL CLASSES

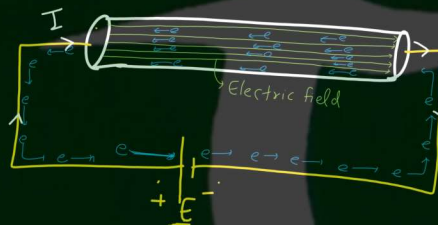

$$F \propto q_1 q_2 \quad \text{--- (1)}$$

$$F \propto \frac{1}{r^2} \quad \text{--- (2)}$$

\* Current flows in any metal due to applied electric field.  $F \propto \frac{q_1 q_2}{r^2}$

\* Current flows in the direction of electric field.

\* -ve Charges flow against the electric field.  
While +ve Charges flow in the direction of electric field.

\* Current flows in the opposite direction of electrons movement.

$$F = \frac{1}{4\pi\epsilon_0} \times \frac{q_1 q_2}{r^2}$$

\* Current density (J)

→ Current flows per unit cross sectional area is called Current density. It is denoted by J.

$$\text{i.e. } J = \frac{I}{A} \rightarrow \frac{\text{Amp}}{\text{m}^2}$$



i.e.

$$A \text{ m}^2 = I$$

Unit of Current density is Amp/m<sup>2</sup>


$$\frac{1 \text{ m}^2}{A} = \frac{I}{A} = J$$




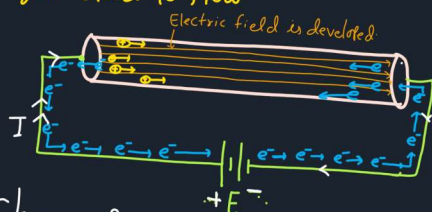
## flow of charges $\Rightarrow$

$\rightarrow$  When Electric field applied on any metal then Charges start to flow.



+ve Charges flow in the direction of Electric field.

-ve Charges flow in opposite direction of Electric field.  
 $\downarrow$   
 electron has -ve Charges

TECHNICAL CLASSES

## Concept of Current

\* Current  $\rightarrow$  Charges flow per Unit time is called electric Current. It is denoted by 'I'

$$I = \frac{Q}{t}$$



Where I is Current. It's Unit is Ampere.

Q is Charge. It's Unit is Coulomb.

t is time. It's Unit is Second.

$\therefore$  As we know that


$$1 e^- \longrightarrow \underline{1.6 \times 10^{-19} C}$$

$$1.6 \times 10^{-19} C \longrightarrow 1 \text{ electron}$$

$$1 C \longrightarrow \frac{1}{1.6} \times 10^{19} \text{ electrons}$$

$$1 C \longrightarrow \frac{10}{1.6} \times 10^{18} \text{ electrons}$$
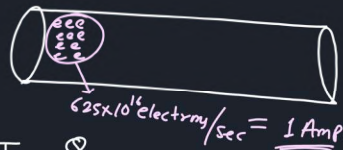
$$\underline{1 C} \longrightarrow \frac{10000}{1.6} \times 10^{16} = 625 \times 10^{16} \text{ electrons}$$



$$I = \frac{Q}{t}$$

$$2 \text{ Amp current} = 2 \times 625 \times 10^{16} \text{ electrons/sec}$$

$$5 \text{ Amp current} = 5 \times 625 \times 10^{16} \text{ electrons/sec}$$

Charges flow per unit time

i.e. If  $1\text{C}$  charge flows in one second, then it is known as One Ampere current  
 $\approx 625 \times 10^{16}$  electrons flow in one second, then current is One Ampere.

TECHNICAL CLASSES


\* Current density :-

Current flows per unit area is known as Current density.

It is denoted by 'J'

$$J = \frac{I}{A}$$

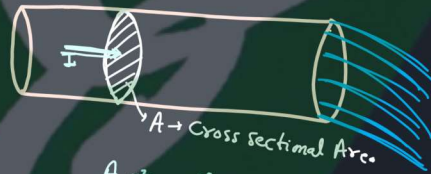Unit of Current density is Ampere/m<sup>2</sup>.





$$A \text{ m}^2 = I \text{ current}$$

$$1 \text{ m}^2 = \frac{I}{A} = \text{Current density (J)}$$


Concept

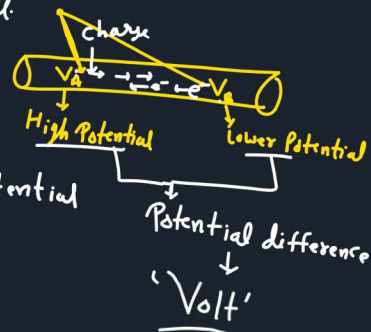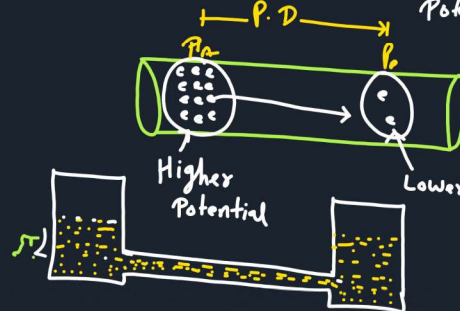Potential → Work done to bring Unit charge from infinite Position to Particular Position of ckt is called Potential.






## Potential difference & E.M.F

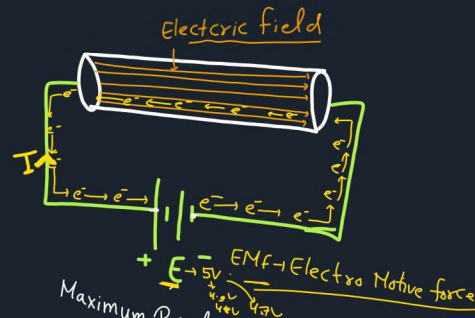

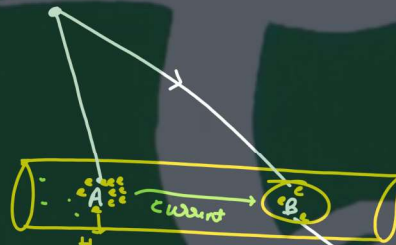Maximum P.D between both Electrode of Cell/Battery Under no current is called EMF



Potential → Work done to bring Unit Charge from infinite Potiom is called Potential.

## Voltage :-

Voltage is the Pressure from an Electrical Circuit Power Sources that Pushes Charges (Electrons) in Electrical Circuit or loop.

$$V = \frac{W}{q}$$

in Short we can say that

Voltage = Pressure

S.I Unit of Voltage is Volt. It is equal Joule/Coulomb




## \* Electric field Intensity (E)

→ Voltage developed per unit length in a ckt is called Electric field Intensity.

It is denoted by  $E$ .

ie.  $E = \frac{V}{l}$

It's Unit is Volt/m



$$l_m = \frac{V}{l} \text{ Voltage}$$

$$1m = \frac{V}{l} \text{ Voltage/m}$$

Current

Current density

Voltage

Electric field Intensity

Current density

$$J = \frac{I}{A}$$

Electric field Intensity

$$E = \frac{V}{l}$$





# Ohm's Law $\rightarrow$

$$R = \rho \frac{l}{A} \quad (\rho \rightarrow \text{Resistivity or Specific Resistance})$$

Ohm's Law states that:-

At constant temperature & pressure Current density in a circuit/conductor is directly proportional to the Electric field intensity.

ie  $J \propto E$  or  $J = \sigma E$

Here  $\sigma$  is Conductivity or Specific conductance  
 $\sigma = \frac{1}{\rho}$  where  $\rho$  is resistivity

## TECHNICAL CLASSES

$$J \propto E \Rightarrow \frac{I}{A} \propto \frac{V}{l}$$

cell  $\rightarrow \left(\frac{l}{A}\right) \propto \frac{V}{I}$

$$\boxed{I \propto V}$$

$V \uparrow, I \uparrow$   
 $V \downarrow, I \downarrow$

$$\Rightarrow \boxed{J = \sigma E}$$

$$\frac{I}{A} = \sigma \cdot \frac{V}{l}$$

$$\frac{l}{A} = \sigma \cdot \frac{V}{I}$$

$$\left(\frac{1}{\sigma}\right) \cdot \frac{l}{A} = \frac{V}{I}$$

$$\boxed{\rho \frac{l}{A} = \frac{V}{I}}$$

$$R = \frac{V}{I}$$

$$\boxed{V = IR}$$


$$\frac{V}{R} = I$$

$$I = \left[\frac{1}{R}\right] \times V \quad \left[\frac{1}{R} = G\right]$$

$G$  is Conductance

$$\boxed{I = G \times V}$$

$$\boxed{J \propto E}$$

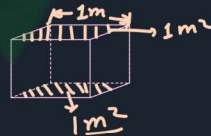

$$J = \sigma E$$

$\sigma$  is Conductivity  
 $\sigma$  is Specific conductance  
 $\sigma = \frac{1}{\rho}$  where  $\rho$  is Resistivity

$$J = \sigma E$$


$$\frac{I}{A} = \sigma \cdot \frac{V}{l}$$

$$\frac{l}{A} = \sigma \cdot \frac{V}{I}$$

$$\left(\frac{1}{\sigma}\right) \cdot \frac{l}{A} = \frac{V}{I}$$

$$\boxed{R = \frac{V}{I}}$$

$$\boxed{V = RI}$$

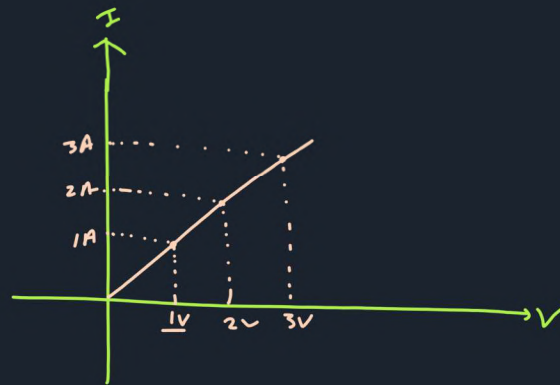

## TECHNICAL CLASSES

### Ohm's Law

$$J \propto E$$

$$J = \sigma E$$

$$V = IR$$

$$I = VG$$


$$J = \frac{dQ}{dt}$$

$$V = R \frac{dQ}{dt}$$
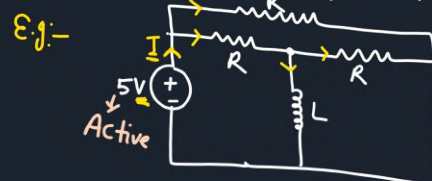
### Electrical Circuit

Any Close loop in which current flows is called Electric Circuit.

Electric circuit consists active and Passive Elements like Energy Source, Resistors, Inductors, Capacitor etc.



\* Voltage

\* Current



## Active Element :-

Element which <sup>(generates)</sup> gives Energy to the Circuit is called active element.

E.g:- Energy Sources, Transistor  
 ↳ It increases the Strength of Signal.

TECHNICAL CLASSES

## Passive Elements

Element which Stores energy or Utilizes Energy is known as Passive Element.


E.g:- Resistor, Inductor, Capacitor
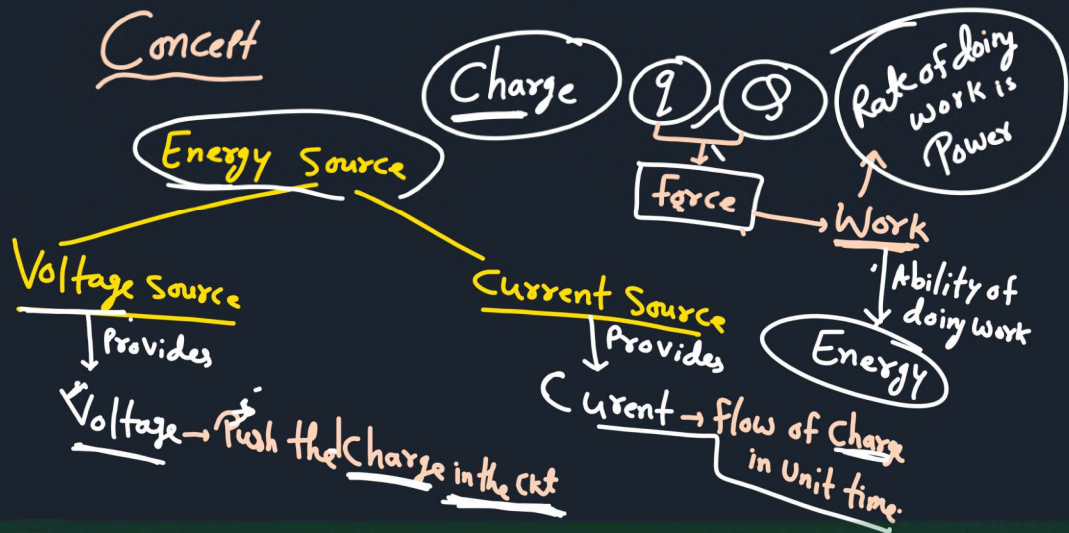
## Energy Sources

The device which is Capable to Provide Energy in Circuit is known as Energy Source.

There are two form of energy Source in Electrical Ckt:-  
 1) Voltage Source 2) Current Source.





## TECHNICAL CLASSES

### Charge

Charge is the inherent [Physical] property of material

Which experience force on itself or another body.

It is denoted by 'Q' or 'q'

It's Unit is Coloumb [C]

There are two types of Charge:-

### Charges

+ve Charge

+ve Charge is carried by Proton

Proton has  $+1.6 \times 10^{-19} \text{ C}$

→ In Any atom, No. of Protons is equal to No. of electrons  
So Atom is electrically neutral.

-ve Charge

-ve Charge is carried by electron.

Electron has  $-1.6 \times 10^{-19} \text{ C}$



E.g:-  $\text{Na} \rightarrow 11$

$$\begin{aligned} \text{No. of Protons in Na} &= 11 \xrightarrow{\text{Charges}} +1.6 \times 10^{-19} \times 11 \\ + \text{No. of electrons in Na} &= 11 \xrightarrow{\text{Charges}} -1.6 \times 10^{-19} \times 11 \\ \hline \text{Total Charges} &= (+1.6 \times 10^{-19} \times 11) - 1.6 \times 10^{-19} \times 11 = 0 \end{aligned}$$

## TECHNICAL CLASSES



\* Electron jumps from lower energy band to higher energy band, when electron absorbs energy.



Electron jumps from higher energy level to lower energy level then electron releases energy.



In a Sodium atom one electron releases then remaining No. of electrons = 10.




$$\begin{aligned} \text{While No. of Proton} &= 11 \xrightarrow{\text{Charges}} +1.6 \times 10^{-19} \times 11 \\ \text{No. of electrons} &= 10 \xrightarrow{\text{Charges}} -1.6 \times 10^{-19} \times 10 \end{aligned}$$

$$\begin{aligned} \text{Total Charges} &= (+1.6 \times 10^{-19} \times 11) + (-1.6 \times 10^{-19} \times 10) \\ &= +1.6 \times 10^{-19} \times (11 - 10) = +1.6 \times 10^{-19} \times 1 \end{aligned}$$





### Revision

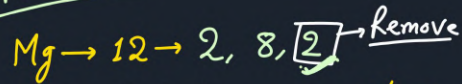

No. of Protons =  $\underline{12}$   $\xrightarrow{\text{Charge}}$   $+1.6 \times 10^{-19} \text{ C} \times 12$


No. of electrons =  $\underline{12} - 2 = 10$   $\xrightarrow{\text{Charge}}$   $-1.6 \times 10^{-19} \text{ C} \times 10$

Total Charges =  $(+1.6 \times 10^{-19} \text{ C} \times \underline{12}) + (-1.6 \times 10^{-19} \text{ C} \times \underline{10})$

$= +1.6 \times 10^{-19} \text{ C} (12 - 10)$

$= +1.6 \times 10^{-19} \text{ C} \times \underline{2}$   $Mg^{++}$

TECHNICAL CLASSES

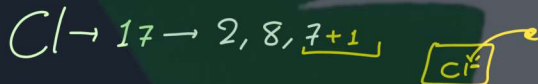

No. of Proton =  $\underline{17}$   $\xrightarrow{\text{Charges}}$   $+1.6 \times 10^{-19} \text{ C} \times 17$

No. of electron =  $\underline{17}$   $\xrightarrow{\text{Charges}}$   $-1.6 \times 10^{-19} \text{ C} \times 17$

Total Charge =  $+1.6 \times 10^{-19} \text{ C} \times \underline{17} - 1.6 \times 10^{-19} \text{ C} \times \underline{17}$

$= +1.6 \times 10^{-19} \text{ C} (\underline{17} - \underline{17})$

$= +1.6 \times 10^{-19} \text{ C} \times \underline{0} = \underline{0}$

One electron adds in Cl-atom.

total No. of e = 18

No. of Proton =  $\underline{17}$   $\xrightarrow{\text{Charge}}$   $+1.6 \times 10^{-19} \text{ C} \times 17$

No. of electron =  $\underline{18}$   $\xrightarrow{\text{Charge}}$   $-1.6 \times 10^{-19} \text{ C} \times 18$

Total Charge =  $+1.6 \times 10^{-19} \text{ C} \times \underline{17} - 1.6 \times 10^{-19} \text{ C} \times \underline{18}$

$= +1.6 \times 10^{-19} \text{ C} (\underline{17} - \underline{18})$

$= +1.6 \times 10^{-19} \text{ C} \times \underline{-1}$

$= -1.6 \times 10^{-19} \text{ C}$

Charge is created on atom by Gaining or losing electron

Loss of electron  $\rightarrow$  +ve charge

Gain of electron  $\rightarrow$  -ve charge



# Charge

+ve Charge

+ve Charge is carried by Proton

$$P = +1.6 \times 10^{-19} \text{ C}$$

-ve Charge



-ve Charge is carried by electrons.

$$e = -1.6 \times 10^{-19} \text{ C}$$

★ When electron removes from matter then +ve Charge is created.

★ When electron enters in atom then -ve Charge is created.



TECHNICAL CLASSES

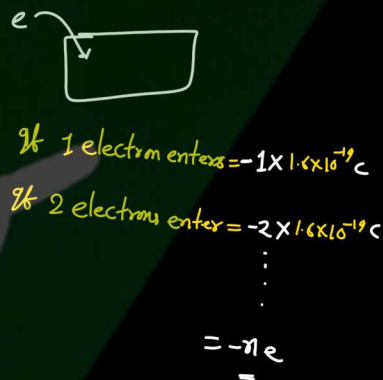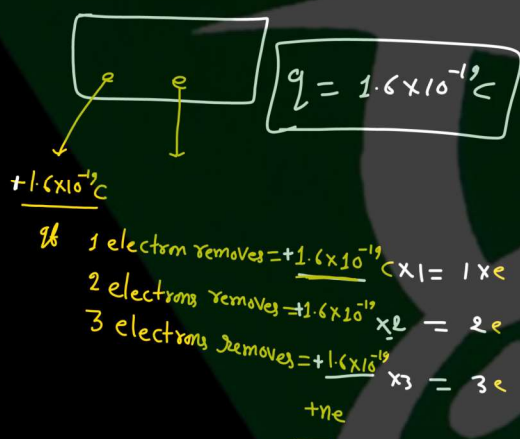

→ Quantisation of Charge:-

Charge on any material is integral multiple of 'e'

i.e.  $q = \pm ne$

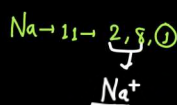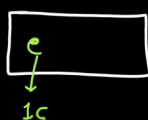





$$\therefore 1e = -1.6 \times 10^{-19} \text{ C}$$

$$1 \text{ C} = 625 \times 10^{16} \text{ electrons}$$

$$1.6 \times 10^{-19} \text{ C} = 1e$$

$$1 \text{ C} = \frac{1}{1.6 \times 10^{-19}} e$$

$$1 \text{ C} = \frac{10}{1.6} \times 10^{19} e$$

$$1. \frac{10}{1.6} \times 10^{19} = 625 \times 10^{16} \text{ electrons}$$

$$4) \frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$\frac{250}{24} \times \frac{10}{1.6} \times 10^{19}$$

$$1.6 \times 10^{-19} \text{ C} = 1e$$

$$1 \text{ C} = \frac{1}{1.6 \times 10^{-19}} e$$

$$1 \text{ C} = \frac{10}{1.6} \times 10^{19} e$$

$$1 \text{ C} = \frac{10 \times 10^{19}}{1.6} e$$

$$1 \text{ C} = \frac{10 \times 10^{19}}{1.6} e$$

\* Charge:-


\* Current:-



→ Charges flow per unit time is called Electric current.

$$I = \frac{q}{t} \rightarrow \frac{1 \text{ C}}{1 \text{ sec}} = \frac{625 \times 10^{16} \text{ electrons}}{\text{Sec}}$$

→ Current is the flow of free electrons.

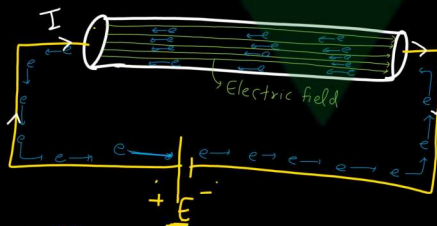

$$F \propto q_1 q_2 \quad \text{--- (1)}$$

$$F \propto \frac{1}{r^2} \quad \text{--- (2)}$$

\* Current flows in any metal due to applied electric field.  $F \propto \frac{q_1 q_2}{r^2}$

\* Current flows in the direction of electric field.

\* -ve Charges flow against the electric field.

While +ve Charges flow in the direction of electric field.

\* Current flows in the opposite direction of electrons movement.

$$F = \frac{1}{4\pi\epsilon_0} \times \frac{q_1 q_2}{r^2}$$



## \* Current density (J)

→ Current flows per unit cross sectional area is called Current density. It is denoted by J.

i.e.  $J = \frac{I}{A}$   $\rightarrow \frac{\text{Amp}}{\text{m}^2}$



i.e.

$$A \text{ m}^2 = I$$


Unit of Current density is  $\text{Amp/m}^2$

$$1 \text{ m}^2 = \frac{I}{A} = J$$

# TECHNICAL CLASSES
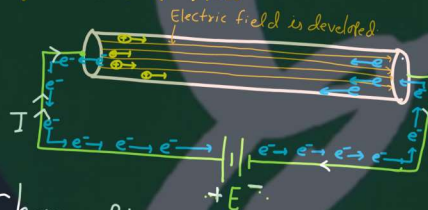
## flow of charges →

→ When Electric field applied on any metal then Charges start to flow.



+ve Charges flow in the direction of Electric field.

-ve Charges flow in opposite direction of Electric field.  
electron has -ve Charges

## Concept of Current

\* Current → Charges flow per unit time is called electric Current. It is denoted by 'I'

$$I = \frac{Q}{t}$$



Where I is Current. It's Unit is Ampere.

Q is Charge. It's Unit is Coulomb.

t is time. It's Unit is Second.

∴ As we know that

$$1 e^{-} \longrightarrow -1.6 \times 10^{-19} C$$


$$1.6 \times 10^{-19} C \longrightarrow 1 \text{ electron}$$

$$1 C \longrightarrow \frac{1}{1.6} \times 10^{19} \text{ electrons}$$

$$1 C \longrightarrow \frac{10}{1.6} \times 10^{18} \text{ electrons}$$

$$1 C \longrightarrow \frac{10}{1.6} \times 10^{18} = 6.25 \times 10^{18} \text{ electrons}$$

TECHNICAL CLASSES

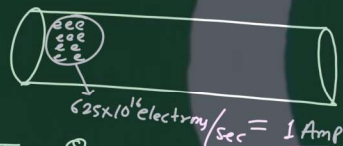

$$I = \frac{Q}{t}$$

$$2 \text{ Amp current} = 2 \times 6.25 \times 10^{18} \text{ electrons/sec}$$

$$5 \text{ Amp current} = 5 \times 6.25 \times 10^{18} \text{ electrons/sec}$$

Charges flow per unit time

i.e. if  $1 C$  charge flows in one second, then it is known as One Ampere current  
 $\approx 6.25 \times 10^{18}$  electrons flow in one second, then current is One Ampere.


\* Current density :-

Current flows per unit area is known as Current density.

It is denoted by 'J'

$$J = \frac{I}{A}$$

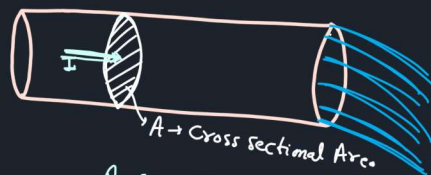
Unit of Current density is Ampere/m<sup>2</sup>.



$$A m^2 = I \text{ current}$$


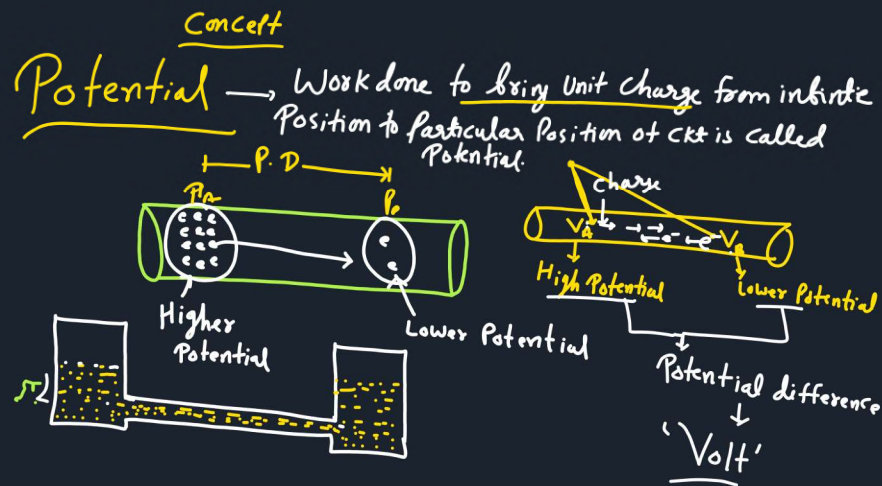
$$1 m^2 = \frac{I}{A} = \text{Current density (J)}$$





# TECHNICAL CLASSES

## Potential difference & E.M.F

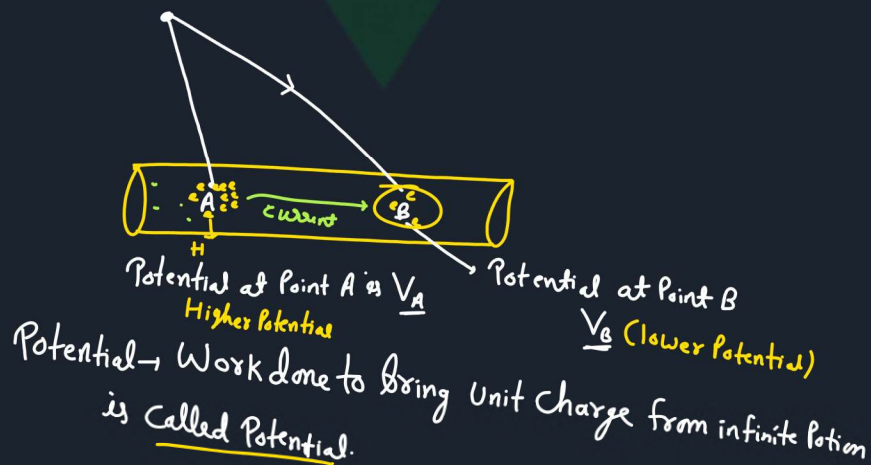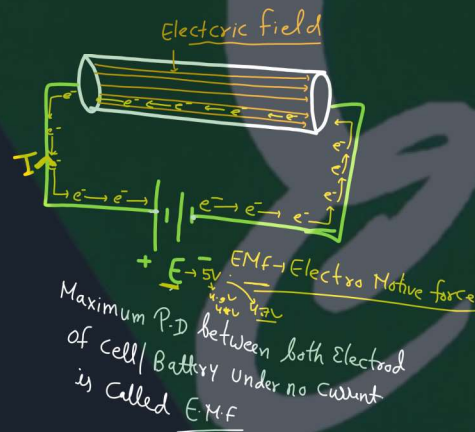



## Voltage:-

Voltage is the Pressure from an Electrical Circuit Power Sources that pushes Charges (Electrons) in Electrical Circuit or loop.

$$V = \frac{W}{q}$$

or  
in short we can say that

Voltage = Pressure

S.I Unit of Voltage is Volt. It is equal Joule/Coulomb


## \* Electric Field Intensity (E)

→ Voltage developed per unit length in a circuit is called Electric field Intensity.

It is denoted by E.

ie.  $E = \frac{V}{l}$

It's Unit is Volt/m



$$l_m = V \text{ Voltage}$$

$$1m = \frac{V}{l} \text{ Voltage/m}$$

Current

Current density

Voltage

Electric field Intensity



Current density

$$\underline{J} = \frac{I}{A} \rightarrow$$

Electric field intensity

$$\underline{E} = \frac{V}{l} \rightarrow$$

# TECHNICAL CLASSES

Ohm's Law  $\rightarrow$

Ohm's Law states that:-

$$R = \rho \frac{l}{A} \quad (\rho \rightarrow \text{Resistivity or Specific Resistance})$$

At constant temperature & pressure Current density in a circuit/conductor is directly proportional to the Electric field intensity.

ie  $J \propto E$  or  $\underline{J} = \sigma \underline{E}$

Here  $\sigma$  is Conductivity or Specific conductance  
 $\sigma = \frac{1}{\rho}$  where  $\rho$  is resistivity

$$J \propto E$$

$$\frac{I}{A} \propto \frac{V}{l}$$

cell  $\rightarrow$   $\left(\frac{l}{A}\right) \propto \frac{V}{I}$

$$\underline{I} \propto \underline{V}$$

$V \uparrow, I \uparrow$   
 $V \downarrow, I \downarrow$

$$\Rightarrow \underline{J} = \sigma \underline{E}$$

$$\frac{I}{A} = \sigma \frac{V}{l}$$

$$\frac{l}{A} = \sigma \frac{V}{I}$$

$$\left(\frac{1}{\sigma}\right) \frac{l}{A} = \frac{V}{I}$$

$$\rho \frac{l}{A} = \frac{V}{I}$$

$$R = \frac{V}{I}$$

$$\underline{V} = \underline{I} \underline{R}$$

$$\frac{V}{R} = I$$


$$I = \left[\frac{1}{R}\right] \times V \quad \left[\frac{1}{R} = G\right]$$

Conductance

$$\underline{I} = \underline{G} \times \underline{V}$$



$$J \propto E$$

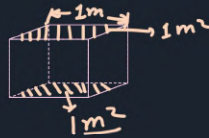

$$J = \sigma E$$

Conductivity  
Sigma - Specific Conductance

$$\sigma = \frac{1}{\rho}$$

Rho - Resistivity

$$J = \sigma E$$

$$\frac{I}{A} = \sigma \frac{V}{l}$$

$$\frac{l}{A} = \sigma \frac{V}{I}$$


$$\frac{1}{\sigma} \cdot \frac{l}{A} = \frac{V}{I}$$

$$\left( \rho \frac{l}{A} \right) = \frac{V}{I}$$

$$R = \frac{V}{I}$$

$$V = R I$$

TECHNICAL CLASSES

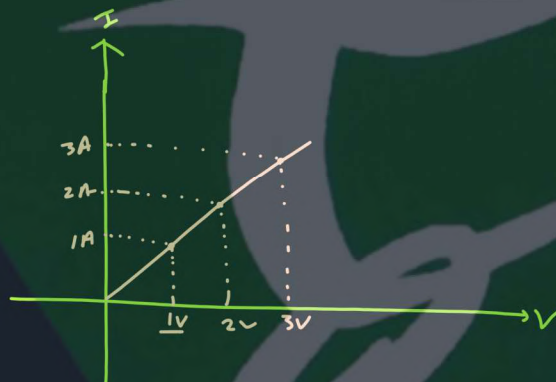

Ohm's Law

$$J = \frac{dQ}{dt}$$

$$J \propto E$$

$$V = I R$$

$$V = R \frac{dQ}{dt}$$

$$J = \sigma E$$

$$I = V G$$



## Electrical Circuit

Any Close loop in which current flows is called Electric Circuit.

Electric circuit consists active and Passive Elements like Energy Source, Resistors, Inductors, Capacitor etc.



## Active Element :-

Element which <sup>(generates)</sup> gives Energy to the Circuit is called active element.

E.g.:- Energy Source, Transistor  
↳ it increases the Strength of Signal.

## Passive Elements


Element which Stores energy or Utilizes Energy is known as Passive Element.

E.g.:- Resistor, Inductor, Capacitor
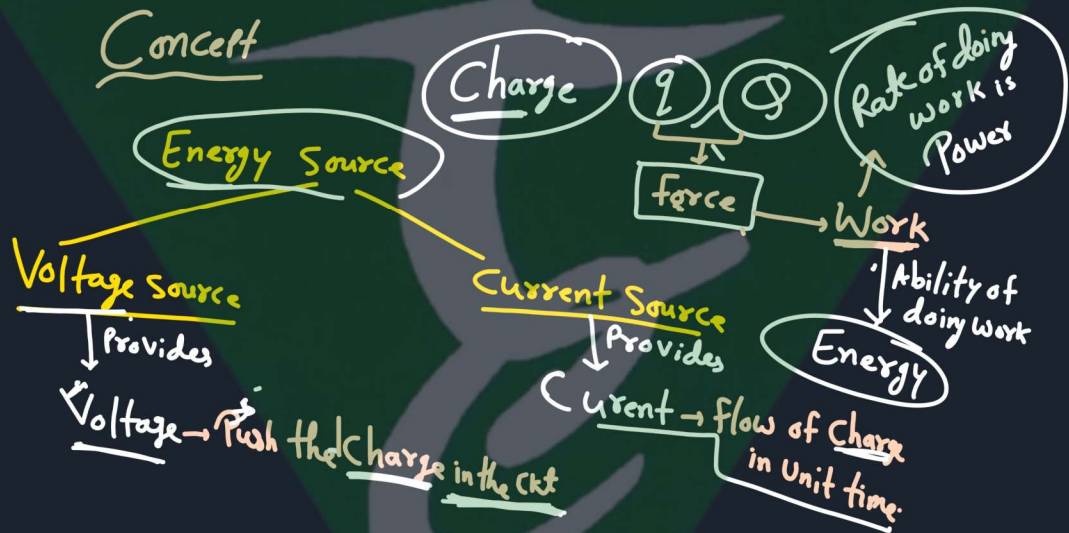
# Energy Sources


The device which is capable to provide energy in circuit is known as Energy Source.

There are two form of energy Source in Electrical Ckt:-  
 1) Voltage Source 2) Current Source.


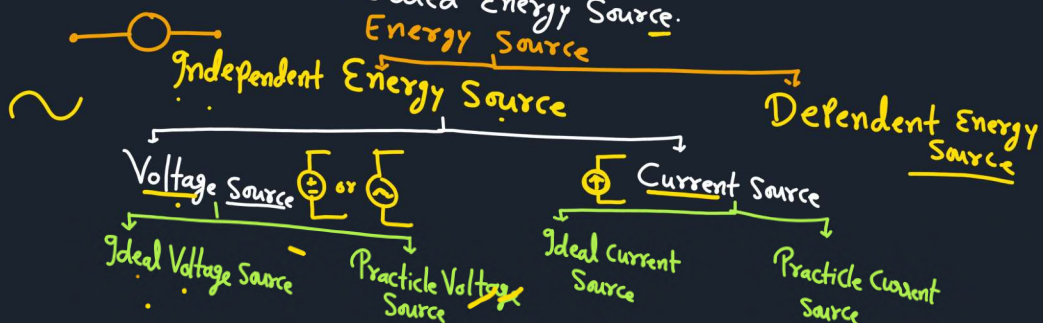
## Energy Source

The device which is capable to give energy to the circuit is called Energy Source.





# Voltage Source

The device which is capable to give Voltage to the Circuit is called Voltage Source.


→ Generally we are discussing about Independent Voltage Source.

→ A device which produces Voltage independently is Independent Voltage Source. It is denoted as:-




A.C

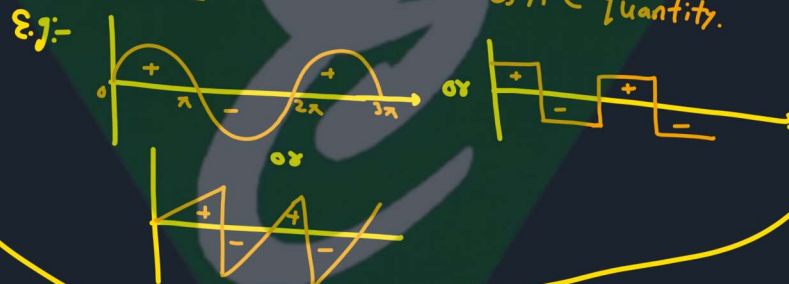Electrical Quantity which <sup>[Direction]</sup> Polarity Changes after fixed interval is known as A.C quantity.



Electrical Q.

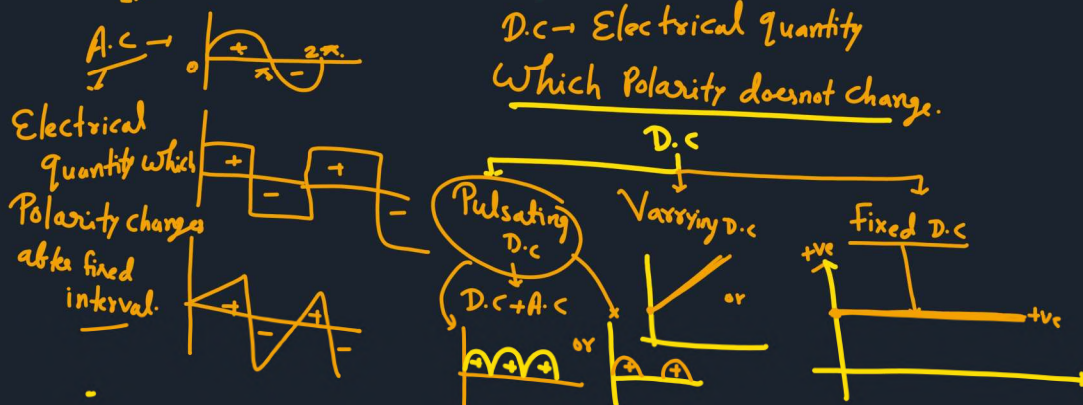





Independent Voltage Sources are further Classified into two Categories

1) Ideal Voltage Source:- No loss

2) Practical Voltage Source  
↳ few loss

## TECHNICAL CLASSES

\* Ideal Voltage Source:-


A device which gives all generated Voltage across its terminals is known as Ideal Voltage Source.


There is no loss in Ideal Voltage Source.

The internal resistance of device (Ideal Voltage Source) is connected in series and represented as  $R_s$ .

The Value of  $R_s$  is Zero in Ideal Voltage Source.


Ckt of Ideal Voltage Source

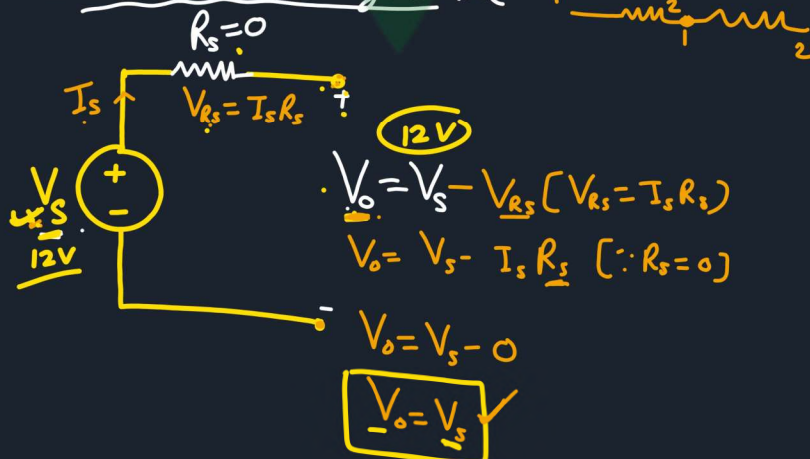

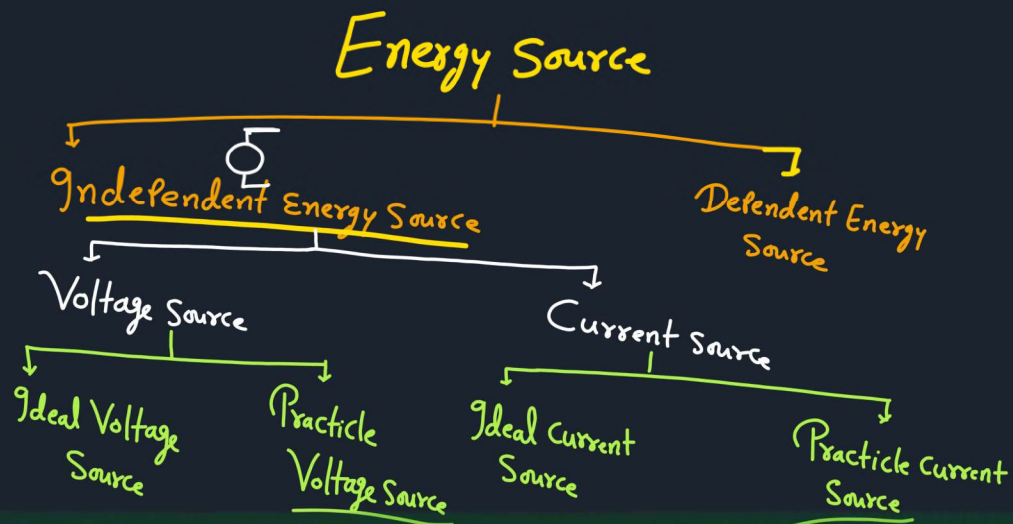

TECHNICAL CLASSES

## Voltage Source: →

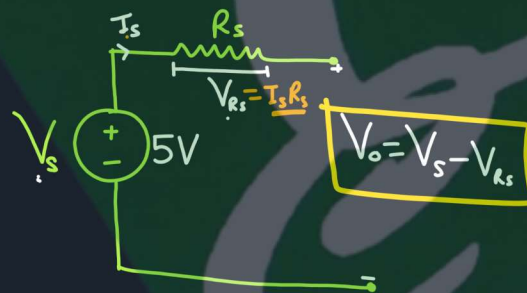


## Ideal Voltage Source

A device which gives all generated Voltage across it's terminals is called Ideal Voltage Source.

There is No loss in Ideal Voltage Source.  
Because it's Internal Resistance is Zero.

$$\underline{R_s = 0}$$

Ideal Voltage Source is shown below:-

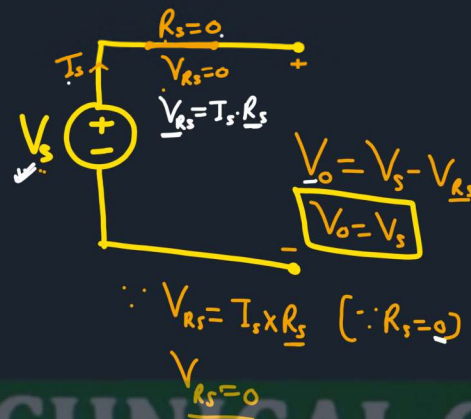


TECHNICAL CLASSES

### \* Practicle Voltage Source:-

A device which give less Voltage than generated Voltage across it's terminals.


It has few loss due to internal Resistance  $R_s$ .

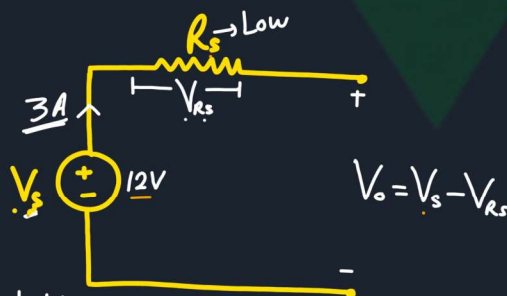The Value of internal Resistance  $R_s$  should be as low as possible.



Example  $\rightarrow$  Let be  $V_s = 12V$   
 $I_s = 3A$

$R_s = 3\Omega$	$R_s = 1\Omega$	$R_s = 0.5\Omega$	$R_s = 0.1\Omega$
$V_{R_s} = I_s R_s$	$V_{R_s} = I_s R_s$	$V_{R_s} = I_s R_s$	$V_{R_s} = I_s R_s$
$V_{R_s} = 3 \times 3 = 9V$	$V_{R_s} = 3 \times 1 = 3V$	$V_{R_s} = 3 \times \frac{0.5}{10} = 1.5V$	$V_{R_s} = 3 \times 0.1 = 0.3V$
$V_o = V_s - V_{R_s}$	$V_o = V_s - V_{R_s}$	$V_o = 12V - 1.5V$	$V_o = 12V - 0.3V$
$V_o = 12V - 9V = 3V$	$V_o = 12V - 3V = 9V$	$V_o = 10.5V$	$V_o = 11.7V$

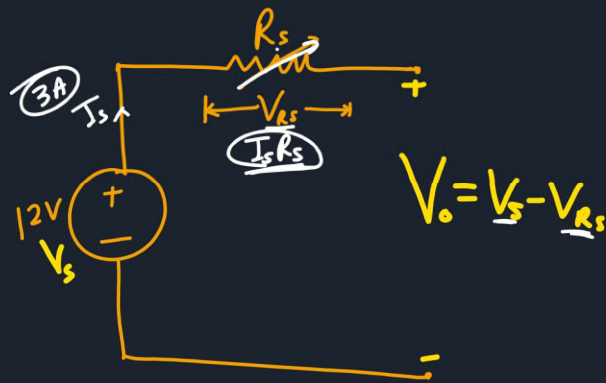

## TECHNICAL CLASSES

### Current Source

An Energy Source Which Produces current through its terminals is known as Current Source.

Current Source is shown below:-



There are two types of Current Sources:-


- ① Ideal Current Source  $\rightarrow$  No loss
- ② Practicle Current Source  $\rightarrow$  few loss


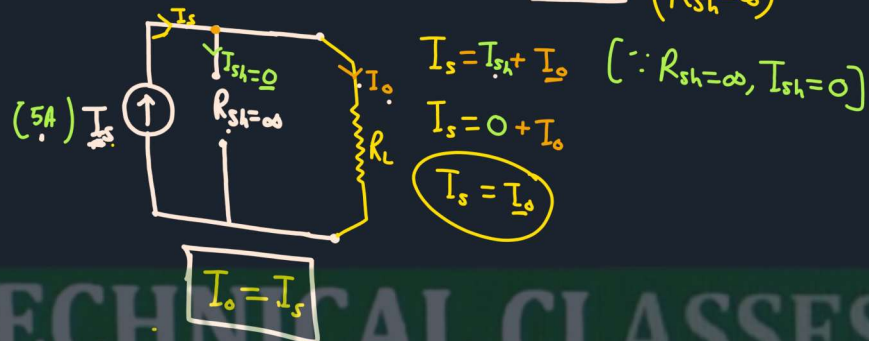
## Ideal Current Source:-

→ A Current Source which has no loss, is ideal c.s.


It's internal Resistance is infinite ( $R_{sh} = \infty$ )


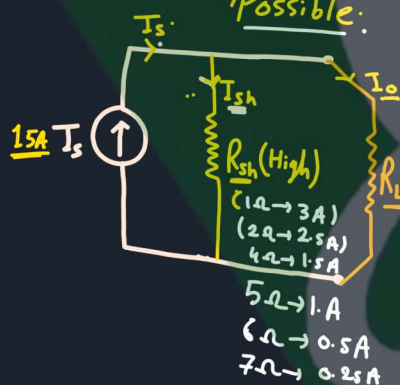
## Practical C.S

→ Few loss ✓

→ internal Resistance  $R_{sh}$  Should be as high as Possible:



Concept

$$I_s = I_{sh} + I_o$$

$$I_o = I_s - I_{sh}$$

$$I_s = 15A$$

$R_{sh}$	$I_{sh}$	$I_o$
1Ω	3A	12A
2Ω	2.5A	12.5A
4Ω	1.5A	13.5A
5Ω	1A	14A
6Ω	0.5A	14.5A
7Ω	0.25A	14.75A

Electric ckt

\* Voltage

\* Current

\* Current density

\* Electric field intensity


\* Energy Source

Tarun Sir


Anindh Sir



## Current Source

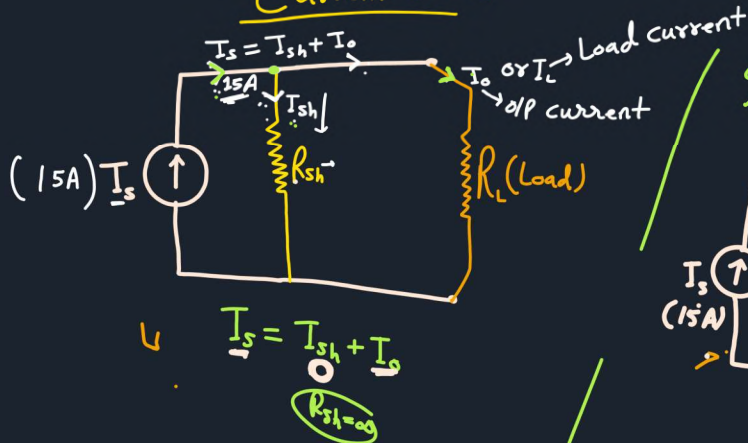


## ideal current source.

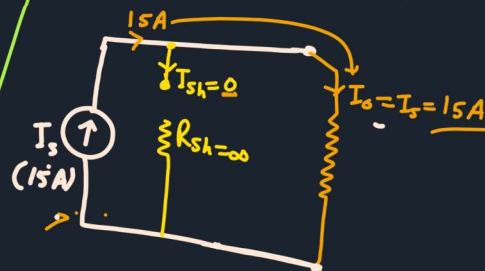


# TECHNICAL CLASSES


## Energy Source

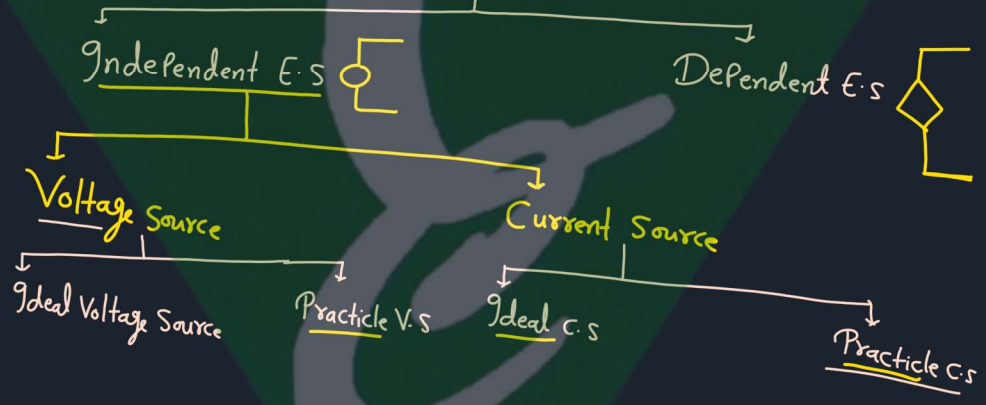


## Voltage Source

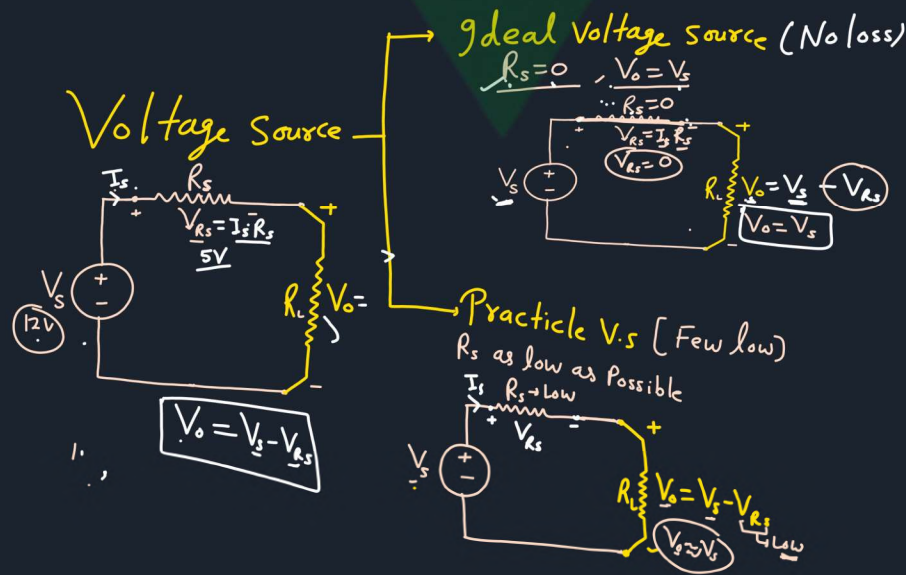

## ideal voltage source (No loss)

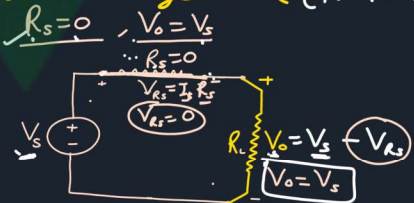


## Practicle V.s [ Few low]

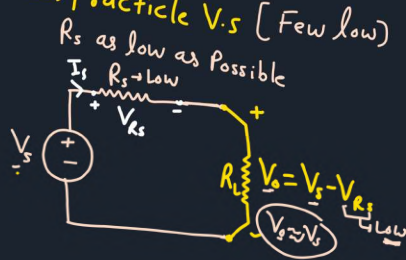





## Current Source

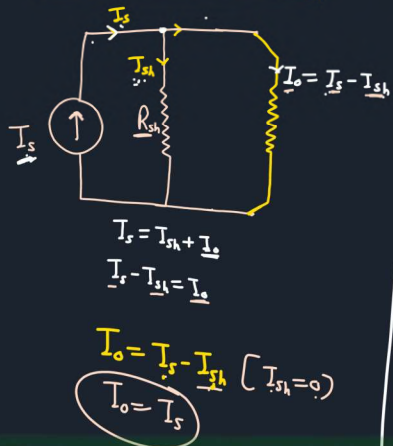
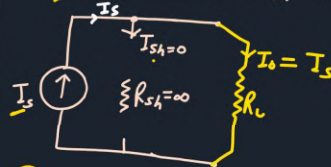
## Ideal C.S $\left[ \frac{\text{No Loss}}{R_{sh} = \infty} \right]$



## Practicle C.S

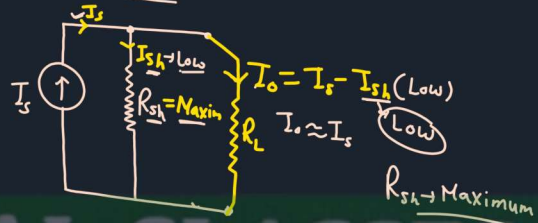


TECHNICAL CLASSES


$$V = IR \quad \leftarrow C.S \rightarrow V.S$$


$$I = \frac{V}{R} \quad \leftarrow V.S \rightarrow C.S$$

## Conversion from V.S to C.S


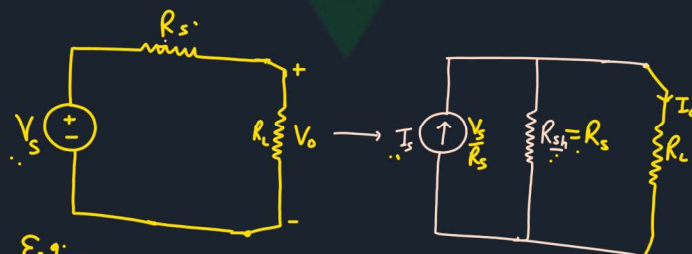


E.g:-

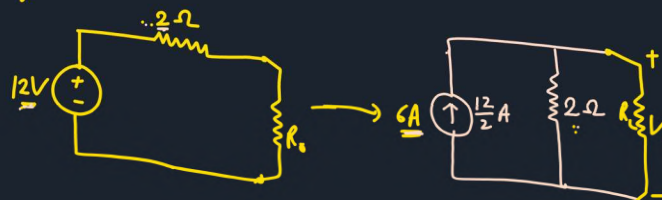

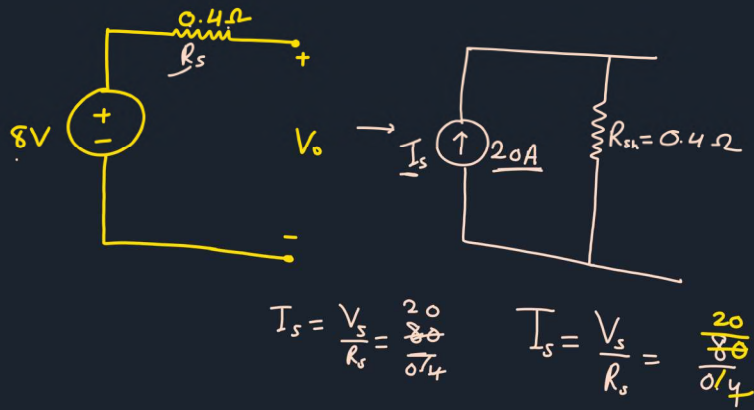

TECHNICAL CLASSES

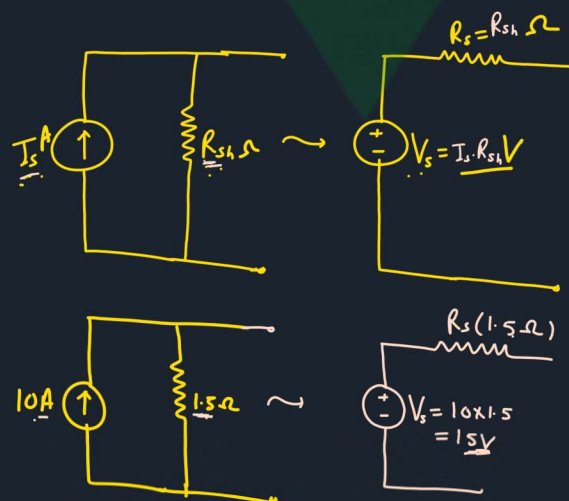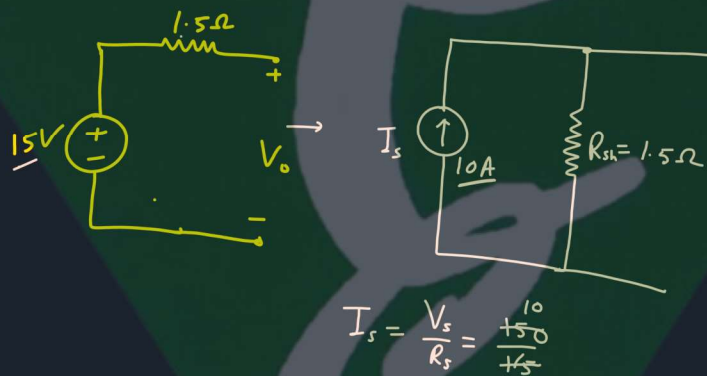





## Element of Electrical Circuit:-

### A) Active Element:-

Element which gives Energy to the Circuit is called active Element.

Eg:- Energy Source, Vacuum tube, Semiconductor devices

Except Diode

Energy Source

Transistor  $\begin{cases} \text{BJT} \\ \text{FET} \end{cases}$   
OP-Amp.

TECHNICAL CLASSES

### B) Passive Element

→ Passive Element does not give Energy to the Circuit.

While Passive Elements converts Energy into following:-

- ① Heat :- Resistor has ability to convert Electrical Energy into heat. So Resistor is a Passive Element.
- ② Electric field :- Capacitor has ability to store Energy in Electric field as Voltage. So Capacitor is also a Passive Element.
- ③ Magnetic field :- Inductor has ability to store Energy in magnetic field as Current. So Inductor is also a Passive Element.

Concept:-

Resistor

Power → Rate of doing work.

$$\text{Power} = \frac{\text{Work}}{\text{time}}$$

$$\text{Work} = \text{Power} \times \text{time}$$

$$\text{Heat} = I^2 R \times t$$


$$H = I^2 R t$$

$P = VI$      $V = IR$   
 $P = IR \times I = I^2 R$   
 $P = I^2 R$

Resistor Produces heat So Resistor is a Passive Element.



## Capacitor

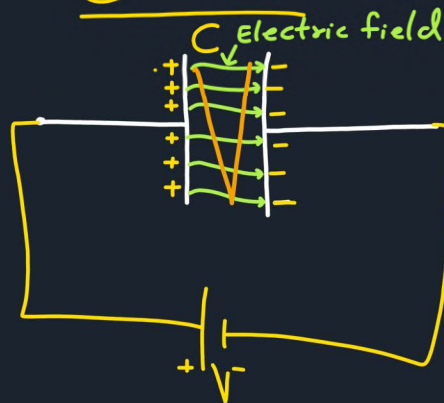

$$Q \propto V$$


$$Q = C \cdot V$$

C is Capacitance

$$C = \frac{Q}{V}$$

# TECHNICAL CLASSES

## Inductor

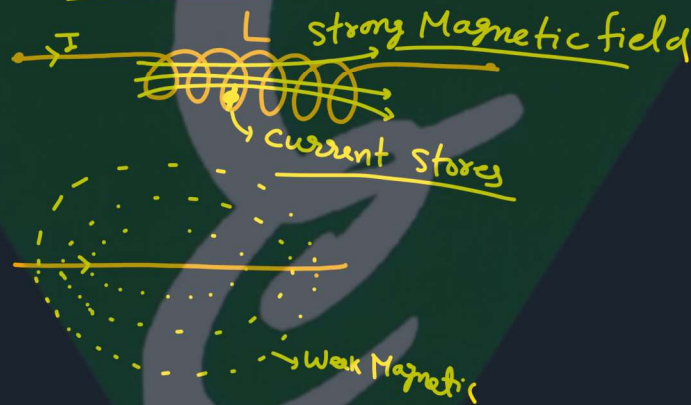

## Resistor

Resistor is a Passive two terminals Electrical Component that implements electrical Resistance as Circuit Element.

In Electronic circuits, resistors are used to reduce Current flow, adjust signal level, and divide Voltage.

We can design a Voltage divider Ckt by Resistors.





There are two types of Resistors:-

1) Fixed Resistor

→ Resistor which resistance does not change is known as fixed Resistor.

Symbol:-

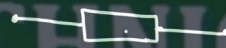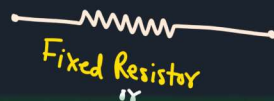


2) Variable Resistor

→ Resistor which resistance changes is known as Variable Resistor.

Symbol



Variable Resistor

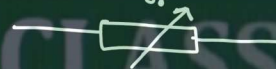

## Resistance

→ The property of material due to which it opposes a flow of current through it is called Resistance.

→ It depends upon length, Cross sectional Area and nature of material.

It is denoted by R.

Mathematically:-


$$R = \rho \frac{l}{A}$$

where

$\rho$  → Resistivity (Specific Resistance)

$l$  → length of Conductor

$A$  → Cross sectional Area

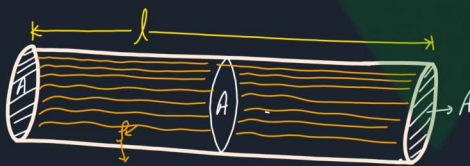

$\rho$  → Resistivity or Specific Resistance  
Depends on Material.

$$R \propto l \text{ --- (1)}$$

$$R \propto \frac{1}{A} \text{ --- (2)}$$

Combining eq<sup>n</sup> ① & ②, we have:-

$$R \propto \frac{l}{A} \text{ or } R = \rho \frac{l}{A}$$

\* Unit of Resistance is Ohm 'Ω'





→ Resistance is the ratio of Potential Difference across two end of a Conductor to the Current flowing through them.

$$\text{i.e. } R = \frac{V}{I}$$



$$\frac{V_{AB}}{I} = \text{Resistance}$$

$$V = IR$$

$$\frac{V}{I} = R$$

## TECHNICAL CLASSES

### Resistivity or Specific Resistance

It is the resistance of the material of Unit length and Unit area of Cross section.

It is denoted by  $\rho$

$$\rho = \frac{R \cdot A}{l} \quad \text{If } A = 1 \text{ m}^2 \text{ and } l = 1 \text{ m}$$

Unit of Resistivity ( $\rho$ ) is ohm-meter  $\Omega\text{-m}$   
Resistivity is independent of length of material and Area of Cross section  
But It depends on Nature of material.

Resistor → Device 

↳ which opposes the flow of current

$$R = \rho \frac{l}{A}$$

$$\frac{R \cdot A}{l} = \rho$$

$$R = \rho \frac{l}{A} \rightarrow \frac{1 \text{ m}}{1 \text{ m}^2}$$

$$R_{\text{resistor}} = \rho \left( \frac{l}{A} \right)$$

$$R_{\text{specific}} = \rho$$

Resistance is Property of material which opposes the flow of current.

$$[R = \rho \frac{l}{A}]$$

ohm ( $\Omega$ )

Specific Resistance  
or  
Resistivity ( $\rho$ )

$\Omega\text{-m}$

$$l = 1 \text{ m}, A = 1 \text{ m}^2$$

$$R = \rho \times \frac{1}{1}$$

$$R_{\text{specific}} = \rho$$






- Resistance can be measured by measuring instrument like Ohmmeter, Ratio Meter, Megger and Multimeter.
- Resistance can be Calculated by Colour Code.

## TECHNICAL CLASSES
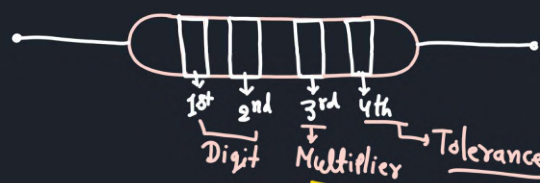
### Colour Code

- Colour code is a technique which helps us to Calculate Resistance and tolerance of Resistor.
- Colour code is also known as Resistance Calculator.

- Resistor has different colour band which help us to determine Resistance of Resistor.  
Generally we are 4 band Resistor.





B B R O Y lived in G r e a t B r i t a i n  
had V e r y G o o d W i f e

B → Black  
B → Brown  
R → Red  
O → Orange  
Y → Yellow  
G → Green  
Bl → Blue  
V → Violet  
Gr → Gray  
W → White

TECHNICAL CLASSES

Colour	1st & 2nd Band Digit	3rd Band Multiplier	Tolerance
Black	0	$\times 10^0 = 1$	
Brown	1	$\times 10^1 = 10$	
Red	2	$\times 10^2 = 100$	
Orange	3	$\times 10^3 = 1000$	
Yellow	4	$\times 10^4$	
Green	5	$\times 10^5$	
Blue	6	$\times 10^6$	
Violet	7	$\times 10^7$	
Gray	8	$\times 10^8$	
White	9	$\times 10^9$	
Gold	—		$\pm 5\%$
Silver	—		$\pm 10\%$

Gold →  $\pm 5\%$   
Silver →  $\pm 10\%$   
None →  $\pm 20\%$



B-0  
B-1  
R-2  
O-3  
Y-4

$$R = 23 \times 10^4 \Omega \pm 10\%$$


$$23 \times 10 \times 10^3 \Omega \pm 10\%$$

$$230 \times 10^3 \Omega \pm 10\%$$

$$230 \text{ k}\Omega \pm 10\%$$

$$R = 230 \text{ k}\Omega \pm 10\%$$
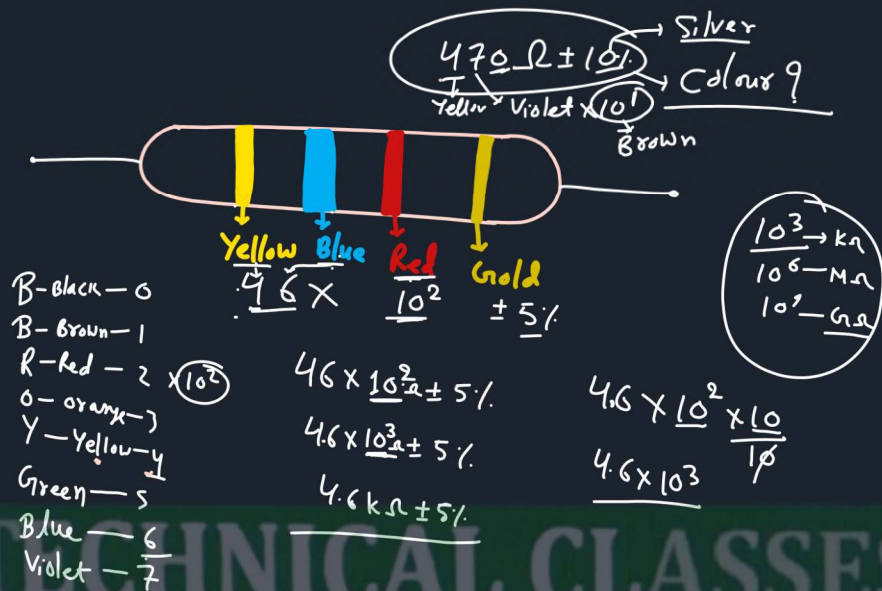
$$\begin{array}{l} 230 \text{ k}\Omega \\ - 23 \text{ k}\Omega \\ \hline 207 \text{ k}\Omega \end{array} \text{ to } \begin{array}{l} 230 \text{ k}\Omega \\ + 23 \text{ k}\Omega \\ \hline 253 \text{ k}\Omega \end{array}$$



## Colour Coding

- Colour coding is a technique which helps us to calculate resistance and tolerance of Resistor.
- Colour coding is also known as Resistance Calculator

BB ROY lived in Great Britain had Very Good Wife.

Digit Multiplier

B	Black	0	→ × 10 <sup>0</sup>
B	Brown	1	→ × 10 <sup>1</sup>
R	Red	2	→ × 10 <sup>2</sup>
O	Orange	3	→ × 10 <sup>3</sup>
Y	Yellow	4	→ × 10 <sup>4</sup>
G	Green	5	→ × 10 <sup>5</sup>
B	Blue	6	→ × 10 <sup>6</sup>
V	Violet	7	→ × 10 <sup>7</sup>
G	Gray	8	→ × 10 <sup>8</sup>
W	White	9	→ × 10 <sup>9</sup>

## Tolerance

Gold → ± 5%


Silver → ± 10%

None → ± 20%





We are taking 4 band Resistor.

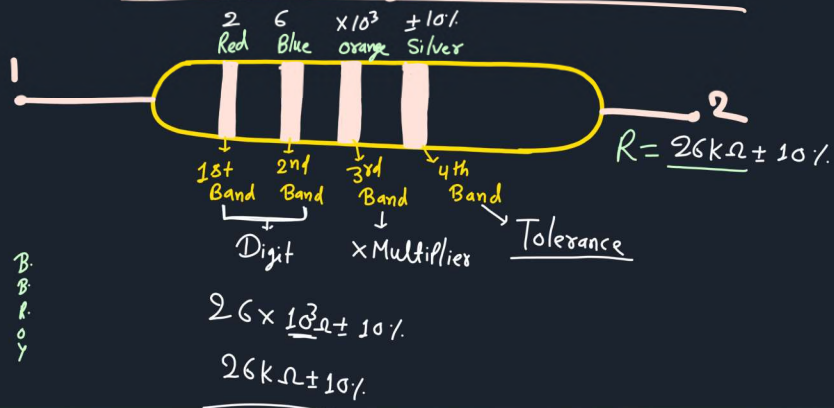

TECHNICAL CLASSES

Calculate the Value of Resistance for 4 Band Resistor

Q:- Red, Yellow, Green and Gold

$2 \quad 4 \times 10^5 \pm 5\%$

$24 \times 10^5 \Omega \pm 5\%$

$2.4 \times 10^5 \times \frac{10}{10} \Omega \pm 5\%$

$2.4 \times 10^6 \Omega \pm 5\%$

$2.4 \text{ M}\Omega \pm 5\%$

$\frac{10^3 \Omega}{10^6 \Omega} = 1k\Omega$   
 $\frac{10^6 \Omega}{10^6 \Omega} = 1M\Omega$

$24 \times 10^5 \Omega (\pm 5\%)$   
 $24 \times 10^5 \times \frac{10}{10} \Omega$   
 $\frac{24 \times 10^6}{10} = 2.4 \times 10^6 \Omega$   
 $= 2.4 \text{ M}\Omega$

Q 430  $\Omega \pm 10\%$

43  $\times 10^1 \pm 10\%$   
 Yellow Orange Brown Silver

B  
B





(1):- Red, Brown, Yellow, None

(2):- Blue, Red, Green, Gold

(3):- Violet, White, Red, Silver

(4):- Gray, Yellow, Orange, Gold

(5):- Orange, Red, Blue, None

## TECHNICAL CLASSES

Find the colour

Q  $470 \Omega \pm 5\%$

Q  $230 k\Omega \pm 10\%$

Q  $230 \Omega \pm 5\%$

Q  $470 k\Omega \pm 10\%$

Q  $5.2 k\Omega \pm 20\%$

### Combination of Resistors

→ Connection/Combination of resistors is a technique to join two or more Resistor together.

• There are 2 Ways of Connection of Resistor.

1) Series Connection

2) Parallel Connection



## \* Series Connection

→ When one terminal of Resistor is connected with terminal of new resistor.

This is shown below:-




## TECHNICAL CLASSES

Calculation of equivalent Resistance of Series Resistor.
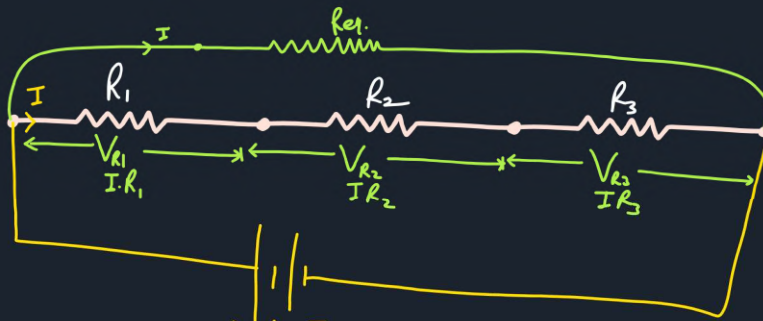
## Series Connection

In a Series Connection, all resistors are connected end to end and forming a single path for current flow.

→ Same amount of current flow through each resistor in series connection but voltage is distributed




$$+ \quad V = V_{R1} + V_{R2} + V_{R3}$$

$$I R_{eq} = I R_1 + I R_2 + I R_3$$


$$I R_{eq} = I (R_1 + R_2 + R_3)$$

$$R_{eq} = R_1 + R_2 + R_3$$

TECHNICAL CLASSES

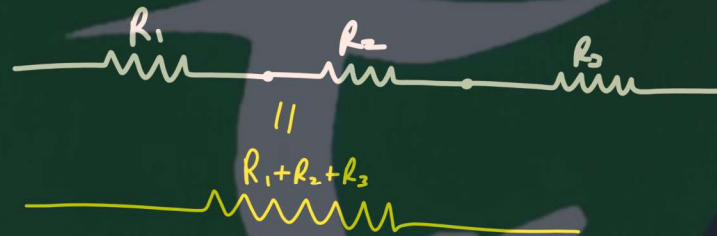

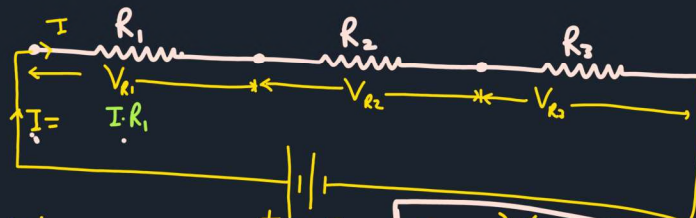Derivation of Voltage across each resistor



$$V = I \cdot R_{eq}$$

$$V = I (R_1 + R_2 + R_3)$$


$$I = \frac{V}{R_1 + R_2 + R_3}$$

$$I = \frac{V}{R_1 + R_2 + R_3}$$

$$V_{R1} = I \cdot R_1 = \frac{V}{R_1 + R_2 + R_3} \times R_1$$

$$V_{R2} = I \cdot R_2 = \frac{V}{R_1 + R_2 + R_3} \times R_2$$
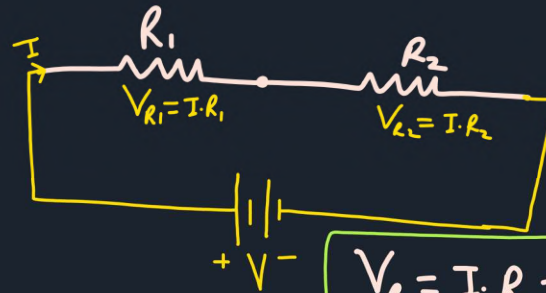
$$V_{R3} = I \cdot R_3 = \frac{V}{R_1 + R_2 + R_3} \times R_3$$



$$V = I \cdot R_{eq}$$

$$V = I \cdot (R_1 + R_2)$$


$$I = \frac{V}{R_1 + R_2}$$

$$V_{R_1} = I \cdot R_1 = \frac{V}{R_1 + R_2} \times R_1$$

$$V_{R_2} = I \cdot R_2 = \frac{V}{R_1 + R_2} \times R_2$$


TECHNICAL CLASSES

### Voltage Division Rule (VDR)

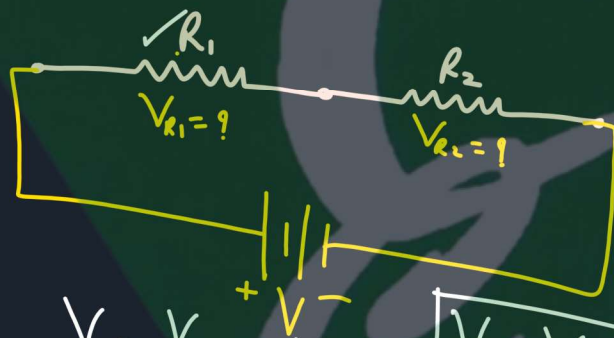

$$V_{R_1} = \frac{V}{R_1 + R_2} \times R_1$$
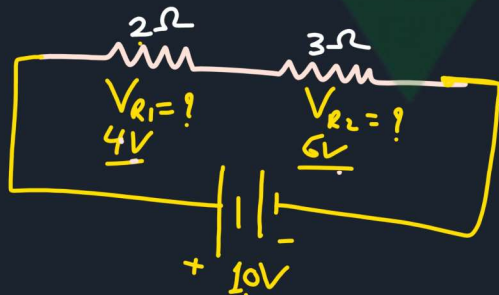
$$V_{R_2} = \frac{V}{R_1 + R_2} \times R_2$$



$$V_{R_1} = \frac{10}{2+3} \times 2 = \frac{10}{5} \times 2 = 4V$$

$$V_{R_2} = \frac{10}{2+3} \times 3 = \frac{10}{5} \times 3 = 6V$$






## Parallel Connection of Resistor

→ In Parallel Connection, all resistors are

Connected across each other, forming Exactly two sets of electrically common Point.


→ In Parallel connection Voltage across each resistor is Same but Current is divided.

This is shown below:-

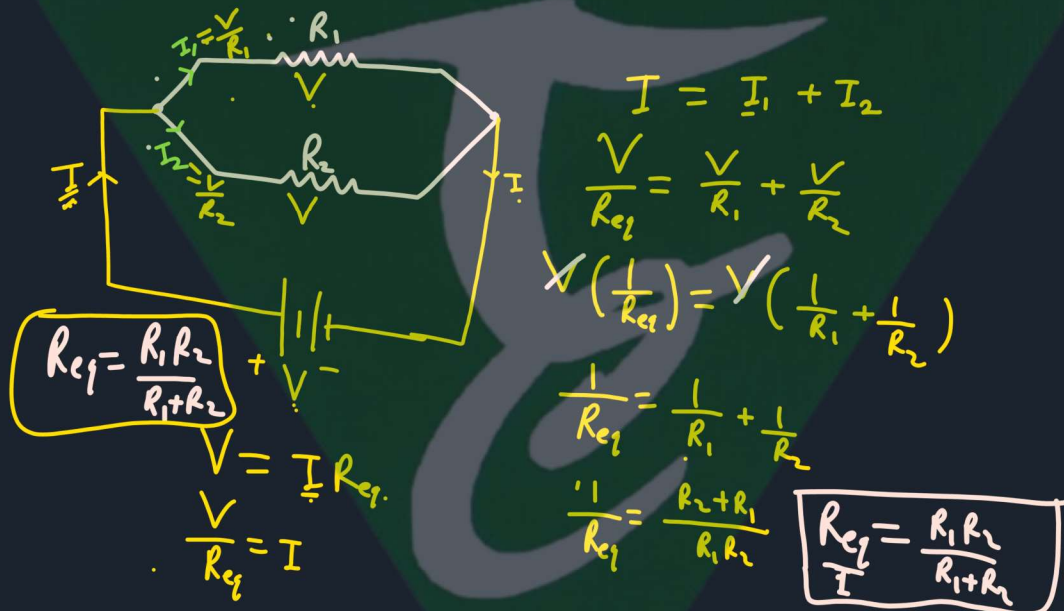

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$



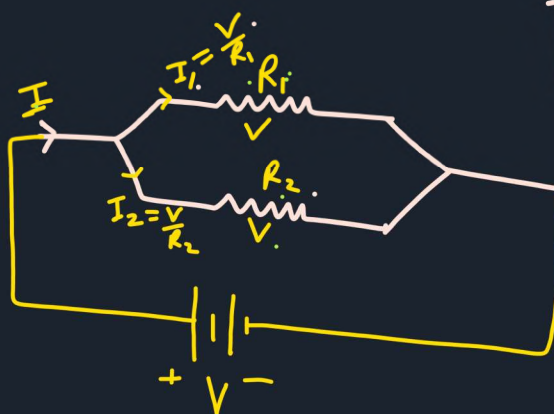

$$V = I \cdot \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I_1 = \frac{V}{R_1}$$

$$I_1 = \frac{1}{R_1} \times V = \frac{1}{R_1} \times I \times \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{I}{R_1 + R_2} \times R_2$$

$$\therefore V = I \cdot R_{eq} = I \cdot \frac{R_1 R_2}{R_1 + R_2}$$


TECHNICAL CLASSES

$$I_2 = \frac{V}{R_2}$$

$$I_2 = \frac{1}{R_2} \times V$$

$$I_2 = \frac{1}{R_2} \times I \times \frac{R_1 R_2}{R_1 + R_2}$$

$$I_2 = \frac{I}{R_1 + R_2} \times R_1$$

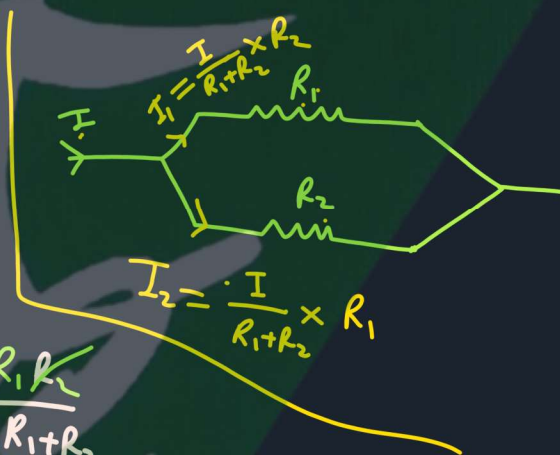

$$I_2 = \frac{I}{R_1 + R_2} \times R_1$$

C.D.R



$$I_1 = \frac{I}{R_1 + R_2} \times R_2 = \frac{10}{3+2} \times 2 = \frac{10}{5} \times 2 = 4A$$

$$I_2 = \frac{I}{R_1 + R_2} \times R_1 = \frac{10}{3+2} \times 3 = \frac{10}{5} \times 3 = 6A$$





# Inductor

Inductor is a passive device. It has ability to Store Energy in magnetic field as Current.

or  
Inductor is a passive device, that Stores Electrical Energy in magnetic field When Current Pass through it.

TECHNICAL CLASSES

Inductor is Shown in fig given below:→

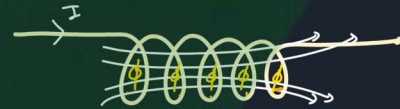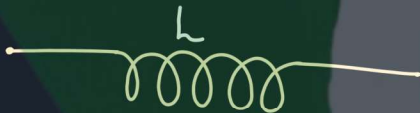

If there are  $N$  turns

Concept:- When Current flow in a Conductor then a magnetic field is extreined.

$$\text{Flux linkage } \Psi = N \cdot \phi$$



Weak magnetic field



Number of turns =  $n$   
Strong Magnetic field.

## Faraday's Law of Electro Magnetic Induction.

1) Faraday's 1<sup>st</sup> law:-

When Conductor Cuts magnetic line of force then  $\epsilon.m.f$  is induced in that conductor.

- ① Magnetic field
- ② Conductor
- ③ Relative Motion

$\epsilon.m.f$  is induced in  
Electro Motive force



2) Faraday's 2<sup>nd</sup> law:-

The induced  $\epsilon.m.f$  is directly Proportional to the rate of change of flux.


$$i.e. \epsilon \propto \frac{d\phi}{dt}$$

$$\epsilon = -N \cdot \frac{d\phi}{dt}$$

$$\boxed{\epsilon = -N \cdot \frac{d\phi}{dt}}$$



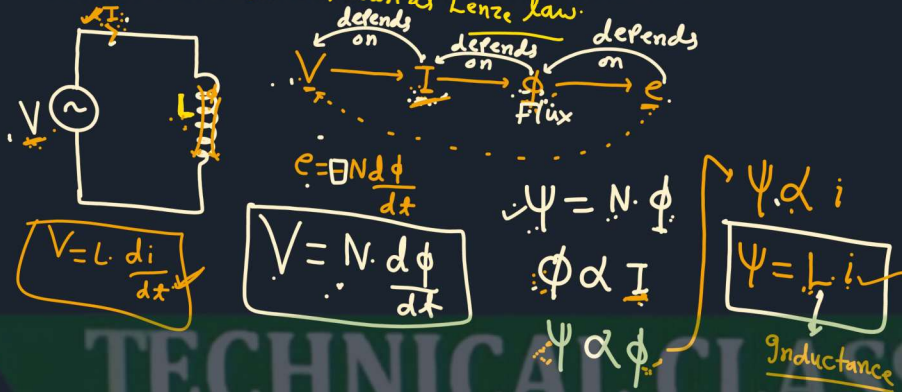Where -ve Sign indicates Voltage opposes its Cause of Expression. It is Explained by Lenz's law. So it is known as Lenz's law.



$$V = N \cdot \frac{d\Phi}{dt}$$

$$V = \frac{d(N\Phi)}{dt}$$

$$V = \frac{d\Psi}{dt}$$

$$V = \frac{d(L \cdot i)}{dt}$$

$$V = L \cdot \frac{di}{dt}$$

$$V = L \cdot \frac{di}{dt}$$


$$V \cdot dt = L \cdot di$$

$$\frac{V}{L} dt = di \text{ - integrating on both sides}$$

$$\int \frac{V}{L} dt = \int di$$

$$\frac{1}{L} \int V dt = i$$

$$i = \frac{1}{L} \int V dt$$

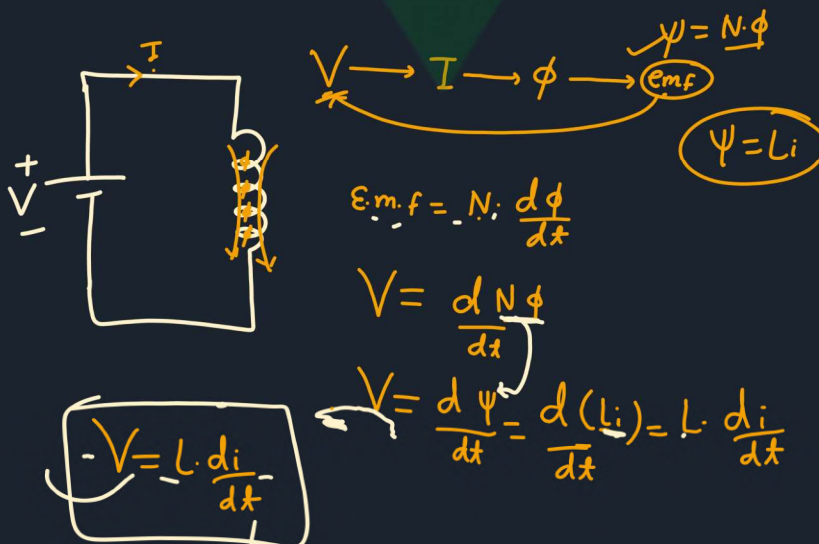

$$E.m.f. = -N \cdot \frac{d\Phi}{dt}$$

$$V = \frac{d(N\Phi)}{dt}$$

$$V = \frac{d\Psi}{dt} = \frac{d(L \cdot i)}{dt} = L \cdot \frac{di}{dt}$$

$$-V = L \cdot \frac{di}{dt}$$





$$V = L \cdot \frac{di}{dt}$$

$$i = \frac{1}{L} \int V dt$$

याद करो

# TECHNICAL CLASSES

## Inductor

Inductor is a passive device that stores Energy in magnetic field When current pass through it.




If there are  $N$  turns.

$$\text{flux linkage } \Psi = N \cdot \Phi$$

$$\mathcal{E} \propto \frac{d\Phi}{dt}$$

$$\mathcal{E} = -N \frac{d\Phi}{dt}$$

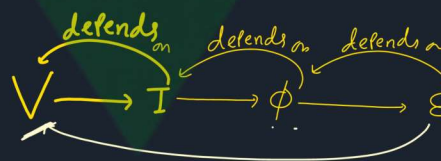

Current depends on Voltage

flux depends on current

EMF depends on flux.

$$\Phi \propto I$$

$$\Psi \propto \Phi$$

$$\Psi \propto I$$

$$\Psi = L \cdot I$$



$$V = N \cdot \frac{d\Phi}{dt}$$

$$V = \frac{d(N\Phi)}{dt}$$

$$V = \frac{d\Psi}{dt}$$

$$V = \frac{d(LI)}{dt}$$

$$V = L \frac{dI}{dt}$$

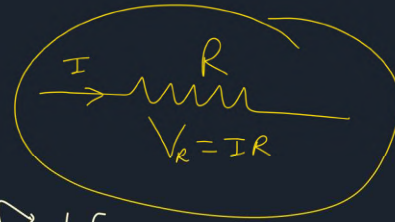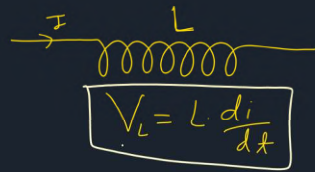

$$V = L \cdot \frac{di}{dt}$$

$$\frac{V}{L} \cdot dt = di \rightarrow \text{Integrating on both sides}$$

$$\int \frac{V}{L} \cdot dt = \int di$$

$$\frac{1}{L} \int V \cdot dt = I$$

$$I = \frac{1}{L} \int V \cdot dt$$


TECHNICAL CLASSES

$$V_L = L \frac{di}{dt}$$

$$I = \frac{1}{L} \int V \cdot dt$$

### Series Connection of Inductor

- ↳ Current same
- ↳ Voltage divide

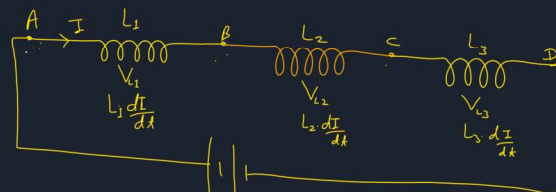

$$V = V_1 + V_2 + V_3$$

$$V_{AD} = V_{A0} + V_{0C} + V_{CD}$$

$$L_{eq} \frac{dI}{dt} = L_1 \frac{dI}{dt} + L_2 \frac{dI}{dt} + L_3 \frac{dI}{dt}$$


$$L_{eq} \frac{dI}{dt} = \frac{dI}{dt} (L_1 + L_2 + L_3)$$

$$L_{eq} = L_1 + L_2 + L_3$$



## Parallel Connection of Inductor

↳ Voltage Same & Current distribute.

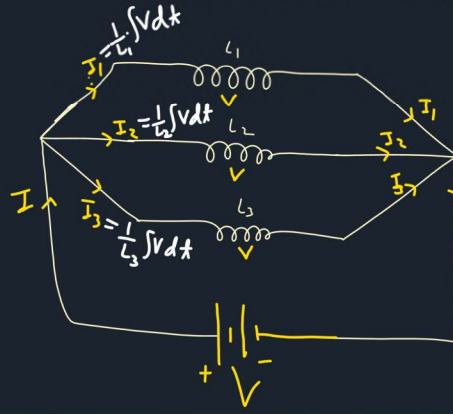

$$I = I_1 + I_2 + I_3$$

$$\frac{1}{L_1} \int V dt = \frac{1}{L_1} \int V dt + \frac{1}{L_2} \int V dt + \frac{1}{L_3} \int V dt$$

$$\frac{1}{L_1} \int V dt = \int V dt \left[ \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} \right]$$

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$


# TECHNICAL CLASSES

## Capacitor

Capacitor is a passive device.

It has ability to store energy in electric field as Voltage.

The symbol of Capacitor is shown below:→

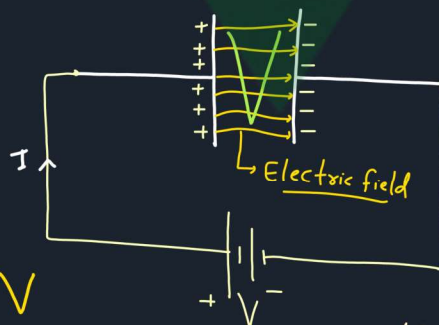

$$10^{-6} F = 1 \mu F$$

μF is mostly used as a Unit.

$$Q \propto V$$

$$Q = C \cdot V \quad \text{--- (1)}$$

where Q is the Charge  
C is Capacitance  
V is Voltage

$$C = \frac{Q}{V}$$

Unit of Capacitance is Farad.  
Farad is the larger Unit.



from eqn ①

$$Q = C \cdot V$$

Differentiating w.r.to time

$$\frac{dQ}{dt} = \frac{d(C \cdot V)}{dt}$$

$$\underline{i = C \cdot \frac{dV}{dt}} \quad \text{②}$$

$$\therefore i = C \cdot \frac{dV}{dt}$$

$$\frac{i}{C} dt = dV$$


Integrating on both sides, -

$$\int \frac{i}{C} dt = \int dV$$

$$\frac{1}{C} \int i dt = V$$

$$\underline{V = \frac{1}{C} \int i dt} \quad \text{③}$$

Series Connection of Capacitor

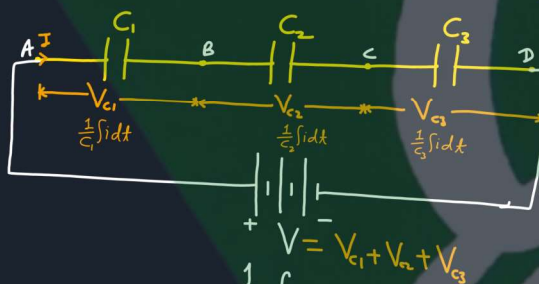


$$\frac{1}{C_{eq}} \int i dt = \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt + \frac{1}{C_3} \int i dt$$

$$\frac{1}{C_{eq}} \int i dt = \int i dt \left[ \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right]$$

$$\underline{\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$\frac{1}{C_{eq}} \int i dt = \frac{1}{C_1} \int i dt + \frac{1}{C_2} \int i dt + \frac{1}{C_3} \int i dt$$

Parallel Connection

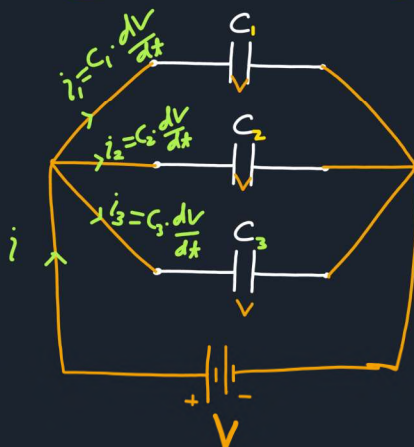

$$i = i_1 + i_2 + i_3$$

$$C_{eq} \cdot \frac{dV}{dt} = C_1 \frac{dV}{dt} + C_2 \frac{dV}{dt} + C_3 \cdot \frac{dV}{dt}$$

$$C_{eq} \cdot \frac{dV}{dt} = \frac{dV}{dt} [C_1 + C_2 + C_3]$$

$$\underline{C_{eq} = C_1 + C_2 + C_3}$$



## Capacitive Reactance

→ It is the property of Capacitor which opposes the flow of Current. It is denoted by  $X_c$ .

$$X_c = \frac{1}{2\pi fC}$$

Unit of  $X_c$  is ohm.

TECHNICAL CLASSES

for A.C

$$f = 50 \text{ Hz}$$

$$X_c = \frac{1}{2 \times 3.14 \times 50 \times C} = \frac{1}{314C} \text{ low}$$

Due to low reactance Capacitor allows to pass A.C.

for D.C

$$f = 0 \text{ Hz}$$

$$X_c = \frac{1}{2 \times 3.14 \times 0 \times C} = \frac{1}{0} = \infty \text{ (High)}$$

Due to high reactance Capacitor blocks the D.C.

## Energy stored by Capacitor

As we know that Capacitor is a passive device.


It has ability to store energy in electric field as Voltage.

$$\therefore Q \propto V$$

$$Q = C \cdot V$$

$$\boxed{\frac{Q}{V} = C}$$

$$\boxed{V = \frac{Q}{C}}$$

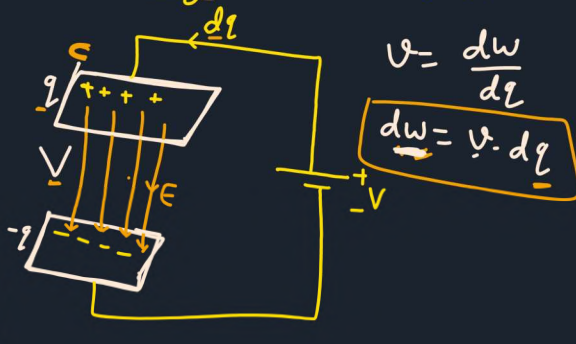



$$dW = V \cdot dq$$

Integrating on both side with suitable limit

$$\int dW = \int_0^Q V \cdot dq \quad [\because V = \frac{Q}{C}]$$

$$W = \int_0^Q \frac{Q}{C} \cdot dq$$

$$\int x^n dx = \frac{x^{n+1}}{n+1}$$

$$W = \frac{1}{C} \int_0^Q Q \cdot dq$$

$$W = \frac{1}{2} \cdot \frac{Q^2}{C} = \frac{1}{2} \times \frac{(CV)^2}{C}$$

$$W = \frac{1}{C} \left[ \frac{Q^2}{2} \right]_0^Q = \frac{1}{C} \left( \frac{Q^2}{2} - 0 \right)$$

$$W = \frac{1}{2} \times \frac{C^2 \times V^2}{C}$$

$$W = \frac{Q^2}{2C}$$

$$W = \frac{1}{2} CV^2$$

$$W = \frac{1}{2} C \cdot V^2$$

$$W = \frac{1}{2} \frac{Q^2}{C}$$

$$W = \frac{1}{2} \times C \times \left( \frac{Q}{C} \right)^2$$

$$W = \frac{1}{2} CV^2$$

$$W = \frac{1}{2} \times \epsilon \times \frac{Q^2}{C^2}$$

Energy Stored by Capacitor is

$$W = \frac{1}{2} \cdot \frac{Q^2}{C}$$

$$\frac{1}{2} CV^2 \text{ or } \frac{1}{2} \times \frac{Q^2}{C}$$

Rough

In Capacitor

$$Q = CV$$

$$V = \frac{Q}{C}$$

$$dW = V \cdot dq$$

$$dW = \frac{Q}{C} \cdot dq$$

$$\int dW = \int_0^Q \frac{Q}{C} \cdot dq$$

$$W = \frac{1}{C} \left[ \frac{Q^2}{2} \right]_0^Q$$

$$W = \frac{1}{2C} \times (Q^2 - 0)$$

$$W = \frac{1}{2C} \times Q^2$$

$$W = \frac{1}{2C} \times [CV]^2$$


$$W = \frac{1}{2C} \times C^2 V^2$$

$$W = \frac{1}{2} CV^2$$

Energy Stored by Parallel Plate Capacitor is  $\frac{1}{2} CV^2$



## \* Magnetic Energy in Inductor

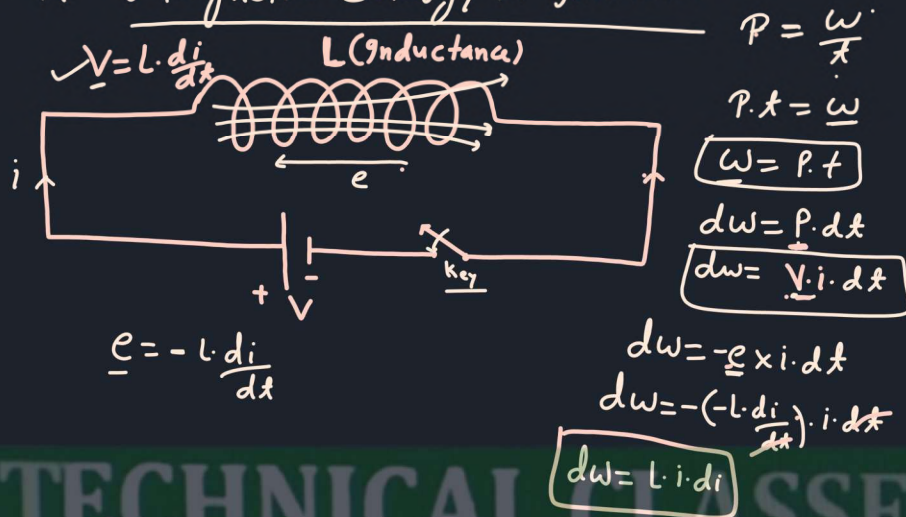

$$dW = L \cdot i \cdot di$$

Integrating on both sides with suitable limit.

$$\int dW = \int_0^I L \cdot i \cdot di$$

$$\int x^n dx = \frac{x^{n+1}}{n+1}$$

$$W = L \cdot \int_0^I i \cdot di$$

$$W = L \cdot \left[ \frac{i^2}{2} \right]_0^I$$

$$W = \frac{L}{2} [I^2 - 0]$$

$$W = \frac{L}{2} I^2$$

$$W = \frac{1}{2} L I^2$$

Magnetic Energy in Inductor is  $\frac{1}{2} L I^2$

In Capacitor

$$\frac{1}{2} C V^2$$

Capacitance

In Inductor

$$\frac{1}{2} L I^2$$

Inductance





## Active Element:-

Element which gives energy to the circuit or controls the flow of signal is called Active element.

There are different types of Active Elements:-

- ① Energy Source - { A) Voltage Source  
B) Current Source
- ② Tube device - { A) Vacuum tube  
B) Gas Filled tube.
- ③ Semiconductor device (Except Diode)  
like BJT, FET, OP-Amp etc.

## Passive Element

An Element which does not generate energy is called Passive Element.

Passive element absorbs energy and then converted into different form like heat, Electric field & Magnetic field.

like:- Resistor, Capacitor, Inductor & Transformer

## Linear Element

The element whose parameters are constant with respect to (Variation) change of Current or Voltage.

$$\begin{array}{l} V \propto I \\ V = RI \end{array}$$

Mathematically

If the relation between Current & Voltage contains a constant co-efficient then element is linear.

E.g:-  $V = RI$  (R is the constant co-efficient)

$$\frac{V}{I} = R$$





$V = \underline{L} \cdot \frac{di}{dt}$  , Here  $L$  is the Constant Co-efficient.

$V = \frac{1}{\underline{C}} \int i dt$  , Here  $\frac{1}{C}$  is the Constant Co-efficient.

TECHNICAL CLASSES



Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24



Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams


Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24



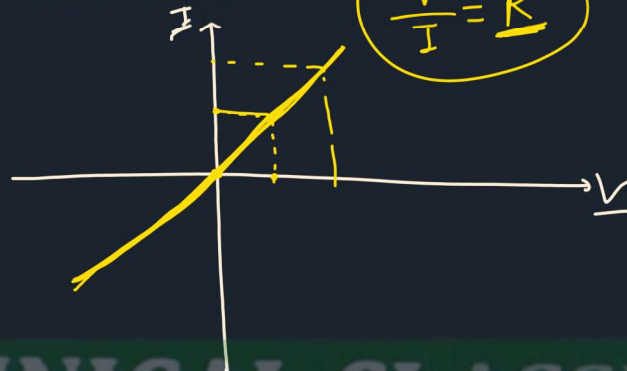The graphical representation of  
linear Element:




TECHNICAL CLASSES

Non Linear Element

The elements whose parameter is not constant w.r. to Voltage and Current are called non-linear elements.

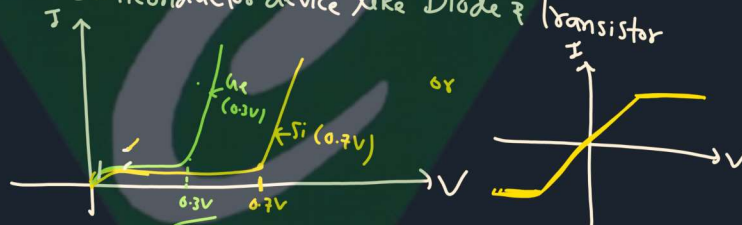Example :- Semiconductor device like Diode & Transistor




Unilateral Element

→ When elements property and characteristics depend upon the direction of current, then elements are unilateral.

→ These elements have different law of current & Voltage for different direction of current.

Eg:- Semiconductor Device like Diode.



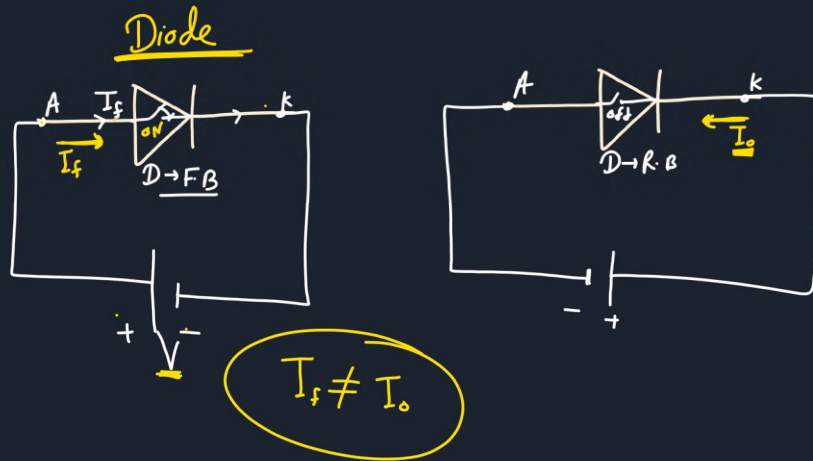

## TECHNICAL CLASSES

### Bilateral Element

Bilateral Elements have same relationship between Voltage & Current for current flowing in any direction.  
like Resistor



Active & Passive


Linear & Nonlinear

Unilateral & Bilateral


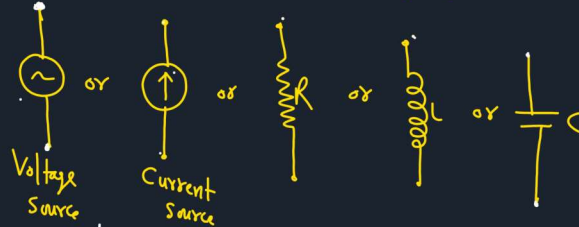
## Important terms:-


\* Branch:- A branch represents a single element such as Voltage Source, Current Source, Resistor, Inductor and Capacitor.



We can say that branch is two terminals of an element


How many branches in this N/W:-

N/W → Network

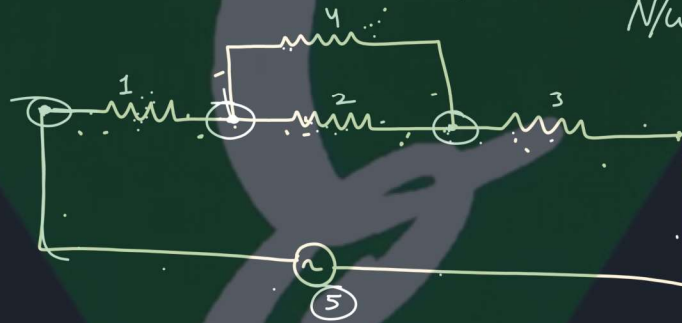

Node:- The node is a point in a network where two or more branches meet.

E.g.:-

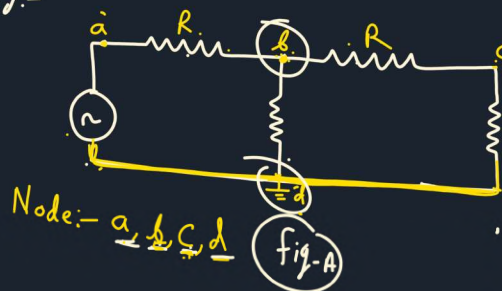

There are 3 types of Nodes:-

- ① Simple Node  $a, b, c$
- ② Datum Node (d)
- ③ Super Node.

Node:-  $a, b, c, d$

Fig-A



Junction:- Junction is a point where three or more branches meet together.


from fig (A)

b and d are junction.

★ Note:- All Junctions are nodes, but all nodes are not necessary to be a junction.
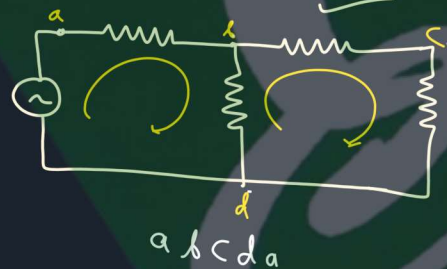
## TECHNICAL CLASSES

Loop :- A close path of a circuit in which another close path is present inside it is called loop.



## Ohm's law

\* Current Density → Current flow per unit area is called Current density.

It is denoted by J.  $J = \frac{I}{A}$

\* Electric field intensity:- Voltage developed per unit length is called Electric field intensity.

$$E = \frac{V}{l}$$

## Ohm's law

At Constant temperature and Pressure Current density is directly proportional to Electric field Intensity.

i.e.  $J \propto E$

$$J = \sigma E$$

$$\frac{I}{A} = \sigma \frac{V}{l}$$

$$\frac{l}{A} = \sigma \frac{V}{I}$$

$$\left(\frac{1}{\sigma}\right) \frac{l}{A} = \frac{V}{I}$$

$$\rho \frac{l}{A} = \frac{V}{I}$$

$$R = \frac{V}{I}$$

$$V = RI$$

TECHNICAL CLASSES

→ Ohm's law is applicable for lumped and distributed Element

## Kirchoff's law

To Solve Electrical Circuit Kirchoff's Proposed two Statements which are known as Kirchoff's Law.

- ① Kirchoff's current Law (K.C.L)
- ② Kirchoff's Voltage Law (K.V.L)



# Kirchoff's Current Law

Kirchoff's Current law states that algebraic Sum of Current at any node is Zero.

Here Incoming Current is taken +ve E.g.:-  
While outgoing Current is taken -ve.



$$I_1 + I_2 + (-I_3) + (-I_4) + (-I_5) = 0$$

$$I_1 + I_2 - I_3 - I_4 - I_5 = 0$$


$$I_1 + I_2 = I_3 + I_4 + I_5 \quad \text{--- (1)}$$

from eq<sup>n</sup> (1) it is clear that

Total Incoming Current = Total out going current  
or

Sum of Incoming Current = Sum of Outgoing Current.

E.g.:-

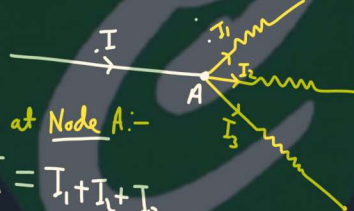

Apply KCL at Node A:-

$$I = I_1 + I_2 + I_3$$

$$\therefore I = I_1 + I_2 + I_3$$

$$I t = (I_1 + I_2 + I_3) t$$

$$I t = I_1 t + I_2 t + I_3 t$$

$$\underline{Q = Q_1 + Q_2 + Q_3}$$

$$I = \frac{Q}{t}$$

$$\underline{I t = Q}$$

from above expression it is Very Clear that KCL Explains  
Conservation of Charge



## ② Kirchhoff's Voltage Law


In any lumped network, algebraic sum of Voltage in a close loop is zero.

Sign Scheme:-




TECHNICAL CLASSES

E.g. → Apply KVL in loop a-b-c-d-a

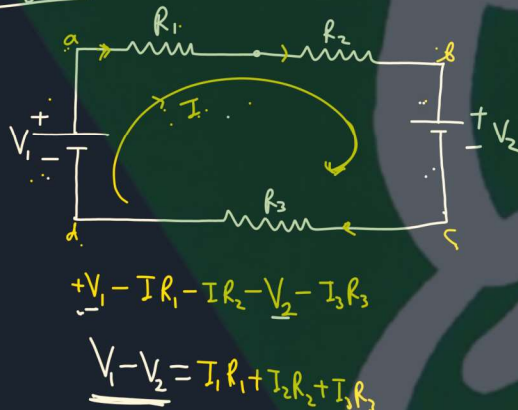

E.g. - 2

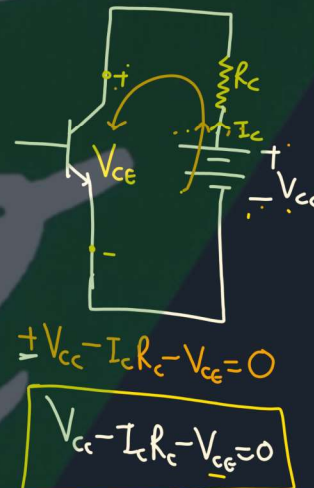

## Node Analysis

- Node analysis is a technique in which we apply K.C.L to find Voltage at Particular Node.
- Node analysis is based on K.C.L
- It is applicable on such circuit which consists several current sources. If a circuit consists voltage source then Voltage Source is converted into Current Source. After that we apply node Analysis.



Node Analysis is also applicable in that circuit in which number of nodes are less than number of Mesh.

In Node Analysis we use following steps:


Step-1) Identify the number of node given in a circuit and assign their name, such as 1, 2, 3, -- etc.

Step-2) Assume one of the node as reference node.

Step-3) Assume different branch current as we like.

Step-4) Write down the KCL according to circuit.

Step-5) Solving the given equation.


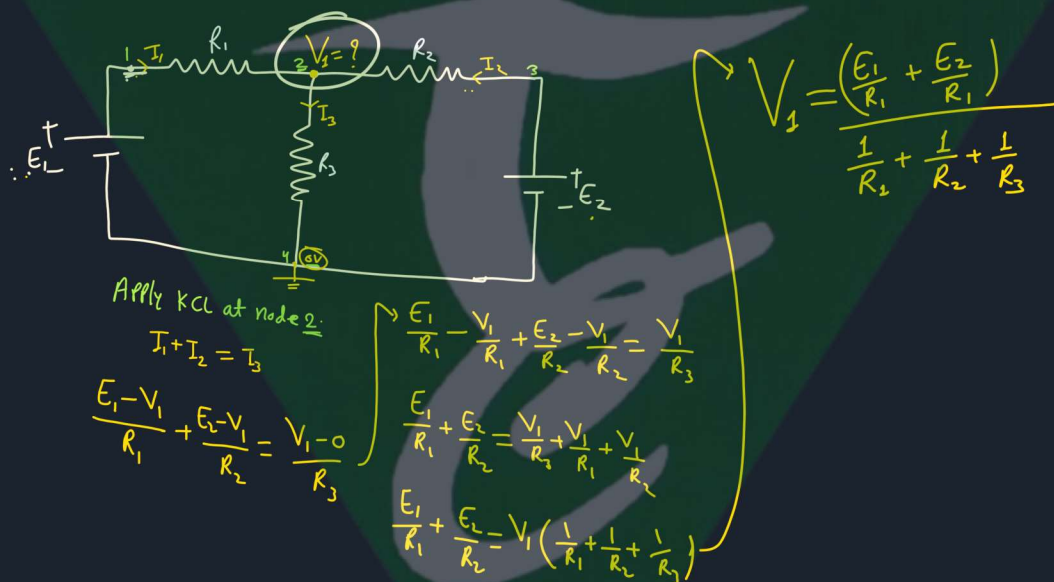


## A. C - Alternative Current

If the Value of Current or Voltage changes Continuously or Periodically with respect to time is known as A.C.

In A.C, Polarity is changed after fixed period.

Such as:-

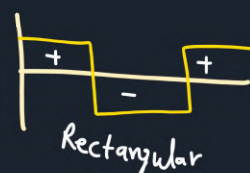
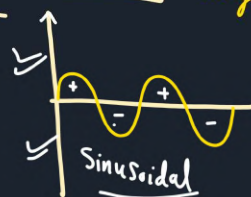






Sinusoidal AC is mostly preferred because

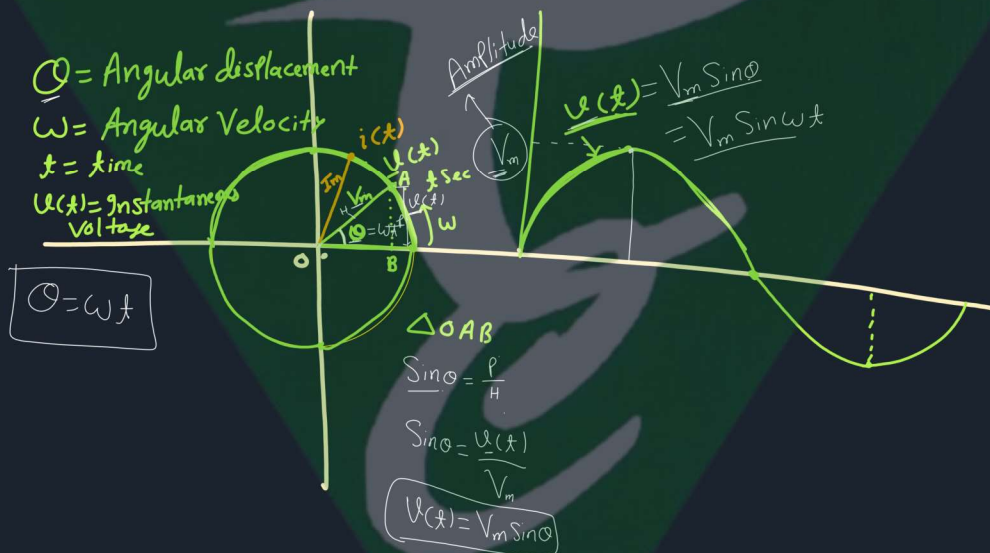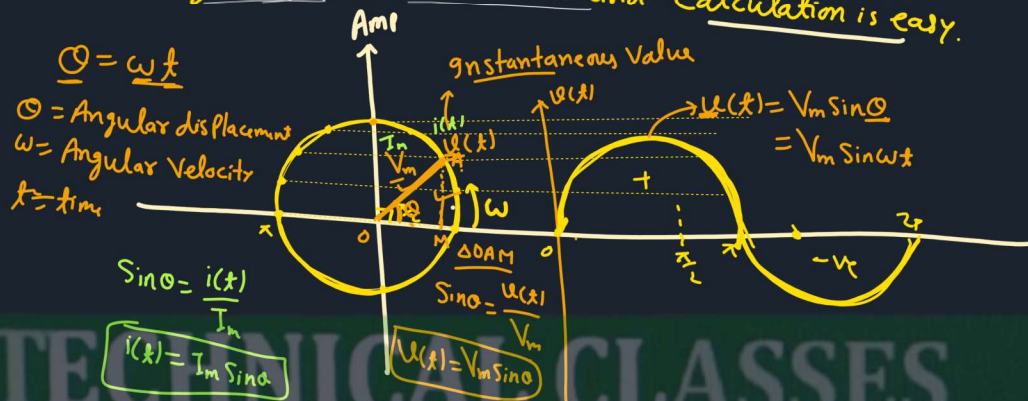it's generation, Transmission and Calculation is easy.



General equation of AC Voltage is

$$v(t) = V_m \sin \theta$$


or  
 $V_m \sin \omega t$



General equation for AC Current

$$i(t) = I_m \sin \theta$$

or  
 $I_m \sin \omega t$

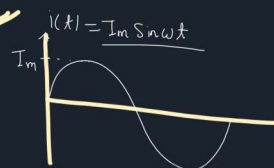



\* Cycle




\* Time Period:- The duration in second to complete one rotation is called time period. It is denoted by 'T'. It's unit is Second.

\* Frequency:- The No. of cycle completed in a second is called frequency. It is denoted by 'f'. It's unit is Hz.

$$f = \frac{1}{T}$$

$$T = \frac{1}{f}$$

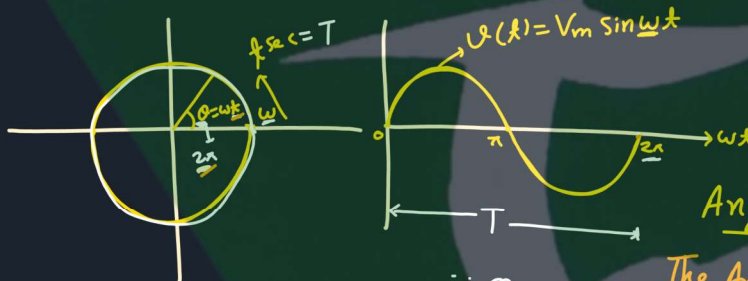

$\omega$  is the angular velocity  
If  $\theta = 2\pi$   
 $t = T$

$$\theta = \omega t$$

$$2\pi = \omega T$$

$$\omega = \frac{2\pi}{T}$$

$$\omega = \frac{2\pi}{T}$$

Angular frequency or Velocity

The Angular Velocity of Sinusoidal Signal is defined as the ratio of Variation of angle in one cycle to the time taken to complete one cycle.


Phase

The Phase of an Alternating quantity of any instant is the time interval that has elapsed from 0 to that instant. It is denoted by ' $\phi$ '






In Phase  $\rightarrow$

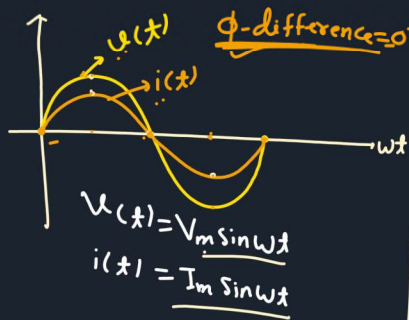

out of phase  
or

Phase Reversal

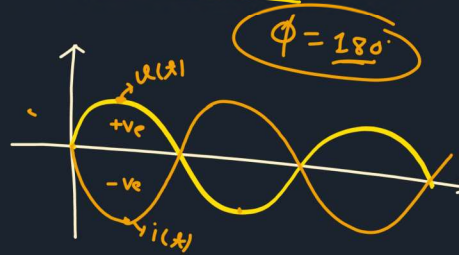

Average Value  $\Rightarrow$

The average Value of A.C is expressed by that Steady current which transfer the same amount of charge as transfer in D.C for same condition.

It is represented as  $V_{avg}$  or  $I_{avg}$ .

$$V_{avg} = \frac{2V_m}{\pi} = 0.63(V_m)$$

$$I_{avg} = \frac{2I_m}{\pi} = 0.63(I_m)$$

R.M.S Value

R.M.S Value stands of Root Means Square Value.

The R.M.S Value of A.C is that Value of Steady Current which produces same amount of heat as produce D.C in same condition.

It is denoted by  $V_{r.m.s}$  or  $I_{r.m.s}$

$$\left( \begin{aligned} I_{r.m.s} &= \frac{I_m}{\sqrt{2}} = 0.707 I_m \\ V_{r.m.s} &= \frac{V_m}{\sqrt{2}} = 0.707 V_m \end{aligned} \right)$$





Maximum Value =  $V_m$  or  $I_m$

R.M.S Value =  $V_{r.m.s}$  or  $I_{r.m.s}$

Average Value =  $V_{avg}$  or  $I_{avg}$

$\frac{V_m}{V_{r.m.s}}$  = Peak factor, Crest factor  
or  
Amplitude factor

$\frac{V_{r.m.s}}{V_{avg}} = \frac{I_{r.m.s}}{I_{avg}}$  = form factor

Peak factor =  $\frac{\text{Max. Value}}{\text{R.M.S Value}}$

Form factor =  $\frac{\text{R.M.S Value}}{\text{Average Value}}$

Peak factor:- It is defined as the ratio of Maximum Value to the r.m.s Value.

It is denoted by  $K_p$ .

$$K_p = \frac{\text{Max. Value}}{\text{R.M.S Value}} = \frac{V_m}{\frac{V_m}{\sqrt{2}}} = \frac{V_m}{V_m} \times \sqrt{2} = \sqrt{2} = 1.414$$

$K_p = 1.414$  → for sinusoidal signal

Form factor:- It is defined as the ratio of R.M.S Value to the average Value.

It is denoted by  $K_f$ .

$$K_f = \frac{\text{R.M.S Value}}{\text{Average Value}} = \frac{\frac{V_m}{\sqrt{2}}}{\frac{2 V_m}{\pi}} = \frac{V_m}{\sqrt{2}} \times \frac{\pi}{2 V_m} = \frac{\pi}{2\sqrt{2}} = 1.11$$

$K_f = 1.11$  → for sinusoidal signal




# Phashors

A Phashor is a Vector rotating at constant angular Velocity ( $\omega$ ).

The Sinusoidal Voltage or Current can be represented by Phashor diagram. This Phashor diagram is shown below:-
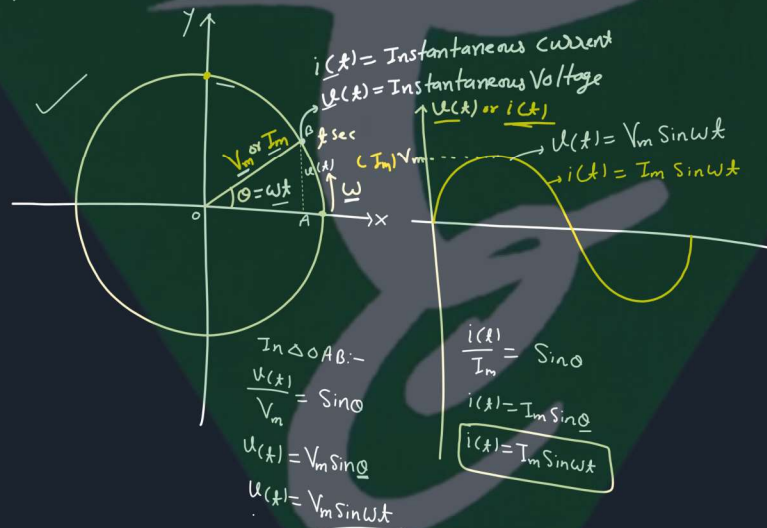
## TECHNICAL CLASSES

Here Phashor rotates in Counter Clock Wise:-



A Phashor is a Vector that represents alternating quantities like Voltage and current.

Phashors are used to analyze the A.C Circuit and determine the Phase relationship.




For Mathematical Calculation of alternating Quantities we draw Phasor diagram

i.e.  $V = V_m \sin \omega t$  ,  $I = I_m \sin \omega t$

There are 3 types of Phasor representation:-

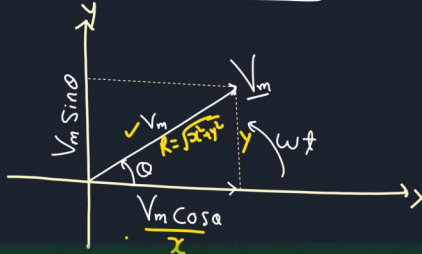- ① Polar Form
- ② Rectangular Form
- ③ Trigonometrical form



Representation of different Phasor

$$V = V_m \sin \omega t + \phi$$

Polar form

$$V = R \angle \phi$$

✓  $R = V_m$ ,  $\phi$  is Angle.

$$R = \sqrt{x^2 + y^2}$$

$$= \sqrt{(V_m \cos \phi)^2 + (V_m \sin \phi)^2}$$

$$R = \sqrt{V_m^2 \cos^2 \phi + V_m^2 \sin^2 \phi} = \sqrt{V_m^2 (\cos^2 \phi + \sin^2 \phi)}$$

$$\boxed{R = V_m}$$

Rectangular form

$$V = x + jy$$

or

$$\boxed{V = X + jy}$$

$$X = V_m \cos \phi$$


$$Y = V_m \sin \phi$$

$$\boxed{V = V_m \cos \phi + j V_m \sin \phi}$$

or

$$V_m \cos \phi - j V_m \sin \phi$$

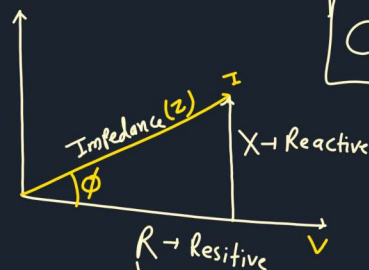\* Power factor:- Power factor of A.C circuit is  $\cos \phi$



$$\boxed{\cos \phi = \frac{R}{Z}}$$





Ex. 1:-  $V(t) = 10 \sin 314t$

- ① Amplitude or Maximum Voltage (10)
- ② Angular Velocity (314)
- ③ frequency (50Hz)
- ④ R.M.S Value =  $0.707 V_m = 0.707 \times 10 = 7.07$
- ⑤ Average Value =  $0.636 V_m = 0.636 \times 10 = 6.36$

TECHNICAL CLASSES

A. Given  $\Rightarrow V(t) = 10 \sin 314t$  — ①

Standard equation is

$$V(t) = V_m \sin \omega t \text{ — ②}$$

Compare eqn ① & ②, we have:-

$$V_m = 10 \text{ (Maximum Voltage } V_m = 10)$$

$$\omega t = 314t$$

$$\boxed{\omega = 314} \text{ (Angular Velocity } = 314)$$

$$\omega = 2\pi f = 314$$

$$f = \frac{314}{2 \times \pi} = \frac{314 \times 50}{2 \times 314} = 50 \text{ Hz}$$

The End

Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24



Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24



## Magnet



The materials which have ability to attract small pieces of iron, Cobalt and Nickel. It has ability to point North-South direction.

Magnetism:- The attractive and directive property of magnet is called magnetism.



## Important terms:-

\* Pole:- Point of magnet at which magnetic strength is maximum is called Pole.

There are two Poles in each magnet.  
i.e. North Pole & South Pole.

Both Poles Can't be Separated.




## Magnetic Axis $\Rightarrow$

A Straight line which passes through both Poles of magnets is called Magnetic Axis.

Law of Magnetic force:-

→ Like Poles repel each-other, but unlike Poles attract each-other.

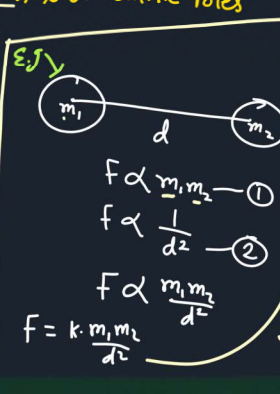→ The force between two magnetic material is directly proportional to the product of their magnetic strength and inversely proportional to the square of distance between them.



$k = \frac{1}{4\pi\mu_0\mu_r}$   
 $F = \frac{1}{4\pi\mu_0\mu_r} \times \frac{m_1 m_2}{r^2}$   
 $F \propto \frac{m_1 m_2}{d^2}$  — ①  
 $F \propto \frac{1}{d^2}$  — ②  
 $F \propto \frac{m_1 m_2}{d^2}$   
 $F = k \frac{m_1 m_2}{d^2}$   
 $\mu_0 \rightarrow$  Absolute Permeability  
 $\mu_r \rightarrow$  Relative Permeability  
 $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$

→ Permeability


The property of material by virtue which it allows itself to magnetise is called permeability. It is denoted by  $\mu$ .

$$\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$$

Absolute Permeability

Magnetic field:-

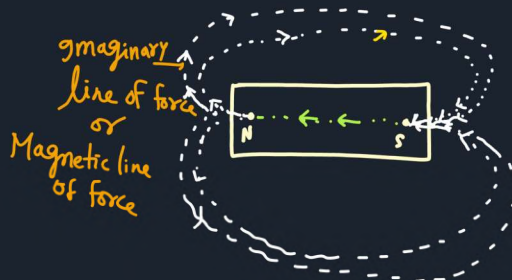The Space or field in which magnetic pole experiences force is called magnetic field.




The magnetic field around the magnet is represented by imaginary lines of forces, These line forces are magnetic line of forces.



- Magnetic lines of force are parallel to each-other. They never intercept.
- Magnetic line of forces create a close loop.  
Externally The direction of magnetic line of force is from North to South  
While internally it moves from South to North.

TECHNICAL CLASSES

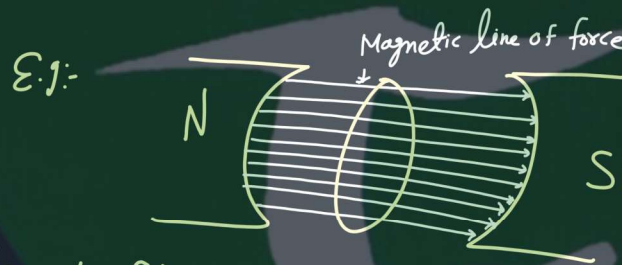

→ Magnetic flux:-

Magnetic flux represents the Strength of magnetic line of force produced by magnet.

or  
The number of magnetic line of forces set up by magnetic circuit is called magnetic flux. It is denoted by ' $\phi$ '. Its unit is Weber.

Flux density:- It is the amount of flux per unit area.

It is denoted by  $B$ .

$$B = \frac{\phi}{A}$$

$$\phi = B \cdot A$$





## Magnetic flux

The magnetic flux represents the quantity of magnetic line of force set up in a magnetic circuit.

It is denoted by ' $\phi$ '

Its unit is Weber.



## TECHNICAL CLASSES

## Flux density

It is defined as the amount of flux per unit Area.

It is denoted by ' $B$ '

$$B = \frac{\phi}{A}$$

Its unit is Weber/m<sup>2</sup>

## Magnetic motive force (m.m.f)

It is the magnetic pressure which sets up or tends to setup magnetic flux in magnetic circuit.

or

The work done in moving a unit magnetic pole round the magnetic circuit is called m.m.f

Mathematically M.M.F is the product of current and number of turns in coil. i.e.  $m.m.f = N \cdot I$

Its unit is Ampere-turns (A.T)





## Reluctance:-

Resistance in Electrical ckt

The opposition that the magnetic circuit offers to magnetic flux is called reluctance.


It is denoted by 'S'.

It's Unit is AT/Wb.

Permeance:- It is the reciprocal of Reluctance and measure of the ease which magnetic flux can pass through the material.

Permeance =  $\frac{1}{\text{Reluctance}}$  It's Unit is Wb/AT

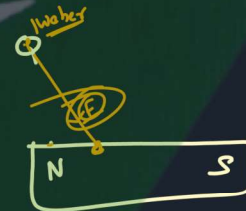Magnetic field Strength  
or  
Magnetic field Intensity  
or  
Magnetic force



It is a force which a Unit North Pole of 1 Weber strength experience at a Particular Point in the magnetic field.

It is denoted by H.

It's Unit is N/W.

## Magnetic field

① The region around the magnet where its pole shows the force of attraction or repulsion.

It is denoted by F.

②  $F = q \times V \times B$

q = Amount of Electric Charge

V = Velocity of Charge

B = flux density

③ It's Unit is Tesla

## Magnetic flux

→ It is the quantity of magnetic line of forces setup in the magnetic circuit.

It is denoted by  $\phi$

②  $\phi = B \times A$

B is flux density


A is Area.

③ It's Unit is Wb.




## Comparison b/w Electric circuit & Magnetic Circuit

### Electric ckt

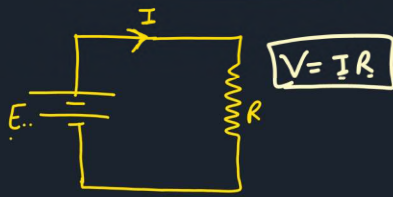

- The close path for electric current is called Electric Circuit.
- Current  $(I) = \frac{\text{E.M.F}}{\text{Resistance}} = \frac{E}{R}$
- Unit of E.M.F is Volt
- Current density  $(J) = \frac{I}{A}$

### Magnetic ckt

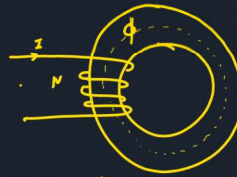

$$\text{M.M.F} = \phi \cdot \frac{S}{I}$$

Reluctance


- The close path for magnetic flux is called magnetic circuit
- Magnetic flux  $\phi = \frac{\text{m.m.f}}{\text{Reluctance}}$
- Unit of m.m.f is ampere-turn
- Flux density  $(B) = \frac{\phi}{A}$

## Magnetic hysteresis

↳ Lagging

The phenomenon of lagging of magnetic flux density (B) behind the magnetising force (H) in a magnetic material is called magnetic hysteresis.

## Hysteresis loop [B-H Curve]

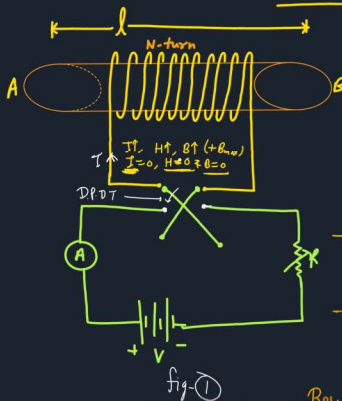

Consider as an Unmagnetised iron bar AB, Wound with coils of N-turn. As shown in fig-1

The magnetising force (H) produced by this Solenoid Can be changed by Varying the Coil Current.


- When Current in Solenoid is zero, then magnetising force  $(H=0)$  is zero and flux density  $(B=0)$  is also zero.
- As Current is increased, then magnetising force is also increased and same time flux density is also increase upto  $B_{max}$  i.e. Saturated point. Beyond this point flux density is not increased however we increased magnetising force.





→ If now H is gradually reduced (by solenoid current)

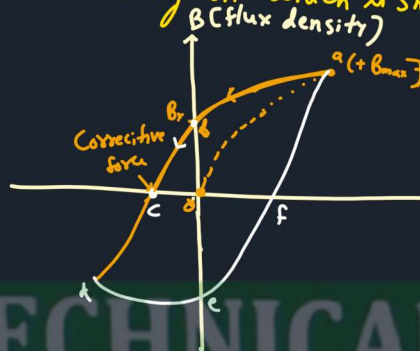It is found that magnetic flux density is not decreased along OA. Which is shown in fig.



from the fig. it is clear that when magnetising force is reduced till zero then flux density (B) is also have some value  $B_r$ . That means material has residual magnetism.

With the help (D.P.D.T) Double Pole double throat Switch we reverse the flow of current.

and at particular value of magnetising force, residual magnetism of material is removed and flux density becomes zero.


Force at which flux density becomes zero is known as Coersive force. After reducing the magnetising force flux density reaches at  $-B_{max}$  (-ve saturation)

from the loop it is clear that B lags behind H. This phenomenon is magnetic hysteresis. and a loop is traced. This loop (a, b, c, d, e, f, a) is known as Hysteresis loop or B-H curve.



B → flux density =  $\frac{\Phi}{A}$

H → Magnetising force

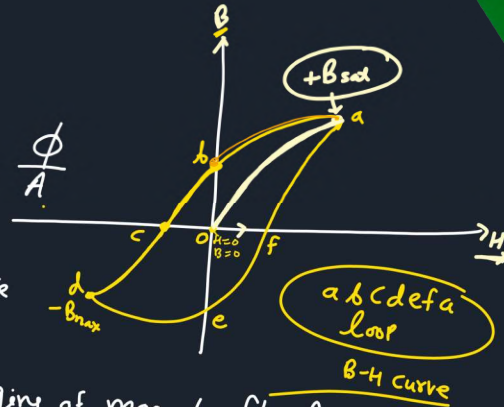

Phenomenon of lagging of magnetic flux density (B) behind the magnetising force (H)

## TECHNICAL CLASSES

### Concept

$\mathcal{E}.m.f \propto \frac{d\phi}{dt}$

$\phi \propto I$

$\phi = L \cdot I$

$\frac{d\phi}{dt} = \mathcal{E}.m.f = V$

$V = \frac{d\phi}{dt} = \frac{d(L \cdot I)}{dt}$

$V = L \cdot \frac{dI}{dt}$

Self Inductance

$L = \frac{V}{\frac{dI}{dt}}$

$V = L \cdot \frac{dI}{dt}$

$\frac{V}{\frac{dI}{dt}} = L$

$\% \frac{dI}{dt} = 1$

$L = \frac{V}{1}$

$\phi \propto I$   
 $\phi = L \cdot I$

$\frac{d\phi}{dt} = \mathcal{E}.m.f = V$   
 $V = \frac{d\phi}{dt} = \frac{d(L \cdot I)}{dt}$

## Inductance

It is the property of coil that opposes change in a current by means of energy stored in the form of magnetic field.

There are two types of inductance:-

- ① Self Inductance
- ② Mutual Inductance




## Self Inductance

Self Inductance is defined as the inductance of a Voltage in a Current Carrying Conductor (Wire) When the Current in the coil itself is Changing.

In the case of Self inductance the magnetic field is created by a changing current in the ckt itself induced Voltage in the same circuit.

Concept:-

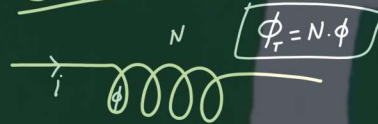

$$i \uparrow, \phi \uparrow, B \uparrow$$

$$\phi \propto i$$

$$\phi_r \propto i$$

$$\phi_r = L i$$

$$N \cdot \phi = L \cdot i$$

$$L = \frac{N \cdot \phi}{i}$$

Self Inductance is denoted by  $L$ .

$$L = \frac{N \cdot \phi}{i}$$

Where  $L$  is Self Inductance

$N$  is the number of turns

$\phi$  is the flux

$i$  is the current.



$$\phi \propto i$$

$$\phi = L i$$

As we know that

$$e.m.f \propto \frac{d\phi}{dt}$$

$$e.m.f = -N \frac{d\phi}{dt} \quad (\because N=1)$$

$$V = - \frac{d\phi}{dt}$$

$$V = - \frac{d\phi}{dt} \quad \star$$

$$V = - \frac{d(L \cdot i)}{dt}$$

$$|V| = \left| L \cdot \frac{di}{dt} \right|$$

$$L = \frac{|V|}{\left| \frac{di}{dt} \right|}$$


$$\text{If } \frac{di}{dt} = 1$$

$$L = V$$

Self Inductance may be defined as the amount of induced Voltage When the rate of Change of Current is Unity.



## Mutual Inductance $\Rightarrow$

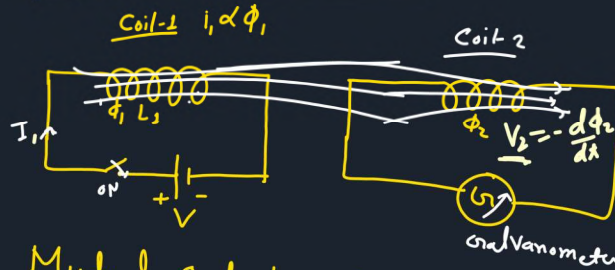

$$\Phi_2 \propto i_1$$

$$\Phi_2 = M \cdot i_1$$

Mutual inductance between two coils is defined as the property of the coil due to which it opposes the changes of current in the other coil or neighbouring coil.

TECHNICAL CLASSES

$$\Phi_2 \propto i_1$$

$\Phi_2 = M i_1$ , where  $M$  is the coefficient of mutual inductance.

Induced e.m.f in Coil-2 is:

$$V_2 = -\frac{d(\Phi_2)}{dt}$$

$$V_2 = -\frac{d(M i_1)}{dt}$$

$$|V_2| = M \left| \frac{di_1}{dt} \right|$$

$$M = \frac{|V_2|}{\left| \frac{di_1}{dt} \right|} \quad \because \frac{di_1}{dt} = 1$$

$$M = V_2$$

Mutual inductance of two coil is induced e.m.f of any coil when  $\frac{di_1}{dt}$  is unity for other coil.

## Faraday's Law of Electromagnetic Induction

Faraday's 1st law of Electromagnetic Induction:-

When a conductor cuts magnetic line of force an e.m.f. is induced in that conductor.

or  
Whenever magnetic flux linked with a circuit changes, induced e.m.f. is produced.





## Faraday's Second law of Electromagnetic Induction:-

Faraday's Second law of Electromagnetic Induction States that the amount of induced emf is directly Proportional to the rate of Change of flux.

$$\underline{\text{E.m.f}} \propto \frac{d\phi}{dt}$$

$$\underline{\text{E.m.f}} = -N \frac{d\phi}{dt} \quad \text{-ve Sign is explained in Lenz's law.}$$

This law tells about the magnitude of E.m.f

## → Lenz's law:-

This law helps us to determine the direction of emf.

According to Lenz's law the Polarity of the induced e.m.f is such that it opposes the Change in the magnetic flux responsible for its Production.



E.g:-



Fleming's Right hand Rule → Generator  
Fleming's Left hand Rule → Motor


## Fleming's Right hand Rule

Fleming's Right hand Rule is also known as generator Rule.

It helps to determine the direction

of induced current in a conductor moving within a magnetic field.

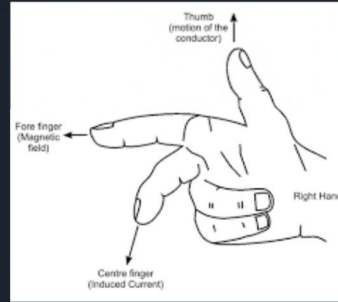It states that, if we extend our Right hand in such a way that Thumb, <sup>(Index)</sup> fore finger and middle finger perpendicular with each other.



Thumb:- Motion of Conductor

Index finger:- Points the direction of magnetic field.

Middle finger:- Points the direction of Current Induced in Conductor


## Fleming's Left hand Rule [Motor]

Fleming's Left hand rule helps to determine the direction of force of a Current carrying Conductor Placed in magnetic field.

→ Thumb:- Motion

✓ Index finger:- Direction of Magnetic field

✓ Middle finger:- Direction of Current

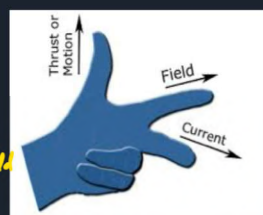





① Faraday's law

② Lenz's law

③ Fleming Right hand Rule

④ Fleming Left hand Rule


⑤ Ampere's law

The End

① Magnetic field

② Conductor

③ Relative Motion

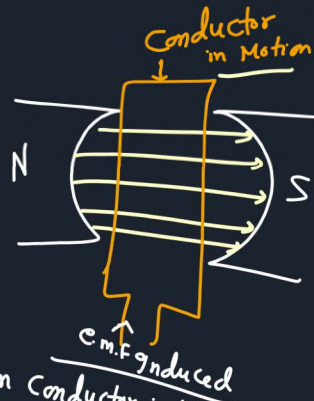

When current carrying conductor placed in magnetic field then a force is experienced in conductor

① When conductor in Motion, then e.m.f. is Produced. [F.R.H. → Direction of induced e.m.f. or current]

## Ampere's law

According to Ampere's law, magnetic fields are related to the electric current produced in them.

The law specifies the magnetic field that is associated with a given current or Vice-versa.



Mathematically


$$\nabla \times \underline{H} = \frac{\partial \underline{D}}{\partial t} + \underline{J}$$

Curl of magnetic field

Current Density



## Numerical

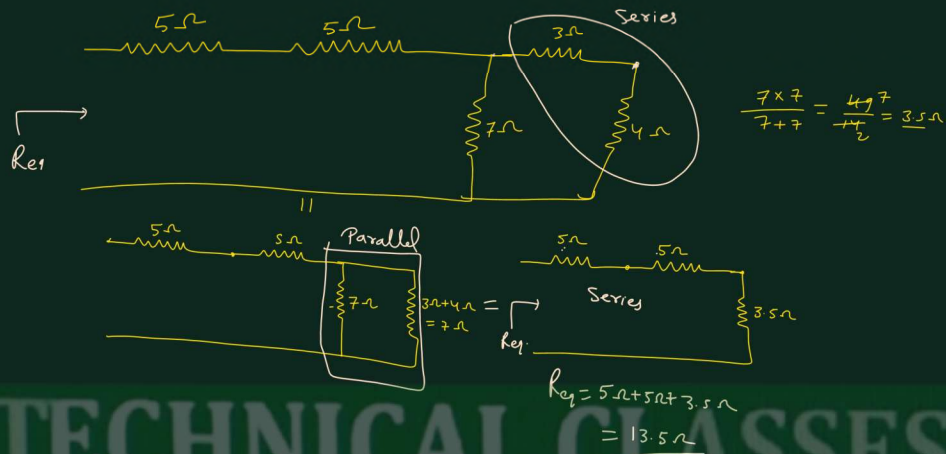

TECHNICAL CLASSES

# The End

Roushan Sir  
Aashutosh Sir  
Nitesh Sir

→ Main Teacher



flow of electrons is Current

or

flow of Charges per unit time is called Current

$$J = \frac{Q}{t}$$

\* Current density ( $J$ ) = Current flows per Unit Area is called Current density

$$J = \frac{I}{A}$$

\* Electric field intensity ( $E$ ) → Voltage developed per unit length.

$$E = \frac{V}{d}$$



A/c to Ohm's law:- At constant Temp. & Pressure  
current density is directly  
proportional to Electric field  
intensity.

$$J \propto E$$

$$V = RI$$

$$V \propto I$$


$$J = \sigma E$$

$$\frac{I}{A} = \sigma \frac{V}{l}$$

$$\left(\frac{1}{\sigma}\right) \cdot \frac{l}{A} = \frac{V}{I}$$

$$\left(\frac{1}{\sigma}\right) \cdot \frac{l}{A} = \frac{V}{I}$$

$$R = \frac{V}{I}$$

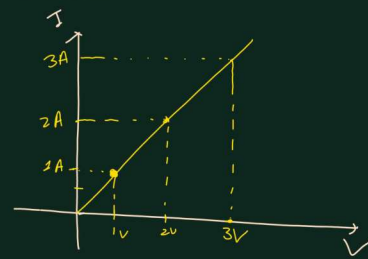

TECHNICAL CLASSES



Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24



Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24



## Unit:-4

### Basic Electronics Components

#### Semi Conductor

Substances which resistivity lies between Conductor and Insulator are known as Semiconductor.

It's resistivity lies between  $10^{-4} \Omega\text{-m}$  to  $0.5 \Omega\text{-m}$

## TECHNICAL CLASSES

Semiconductors are magical material


Which resistance can be Varried by adding impurity.

So, Semiconductor material is the back bone of Electronics device.

→ Resistivity of Semiconductor can also be changed by applied electric field (Connect the cell or battery).

Example of Semiconductor materials:-  
Silicon, Ge


### Classification of Semiconductor

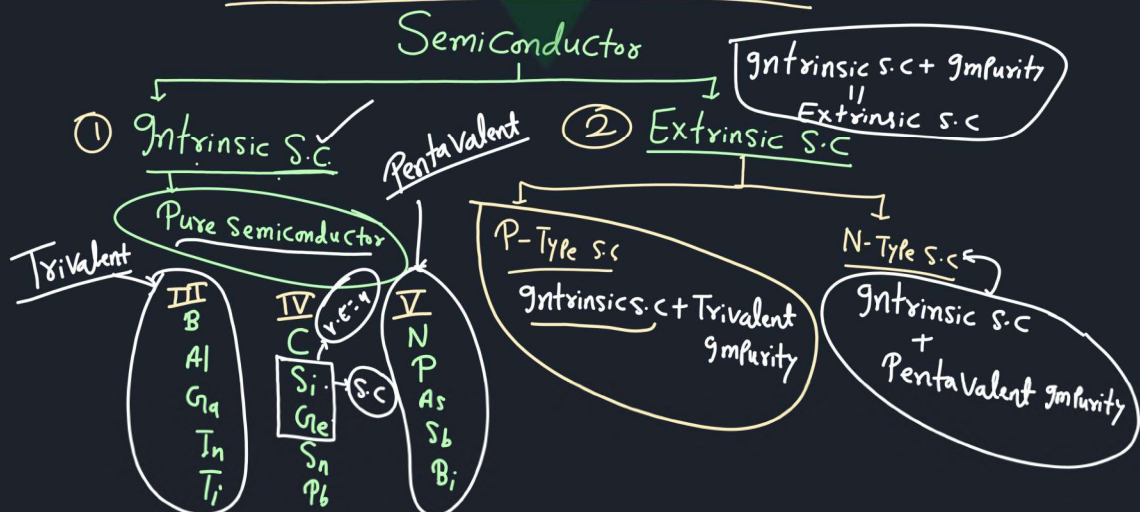



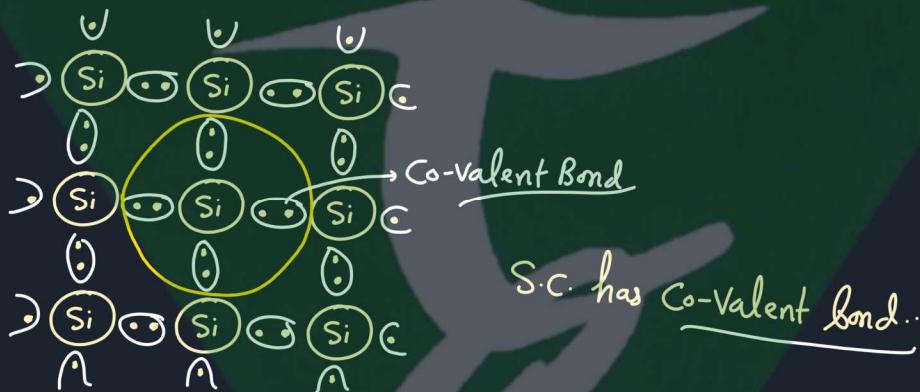
# Intrinsic Semiconductor

- Purest form of Semiconductor is known as Intrinsic Semiconductor.  
E.g:- Pure Si & Ge
- It's conductivity is Very Poor. So, Extrinsic S.C is required.
- Intrinsic S.C has 4 Valance electrons.  
The Str. of Intrinsic S.C is shown below:-




## Energy band diagram of Intrinsic S.C

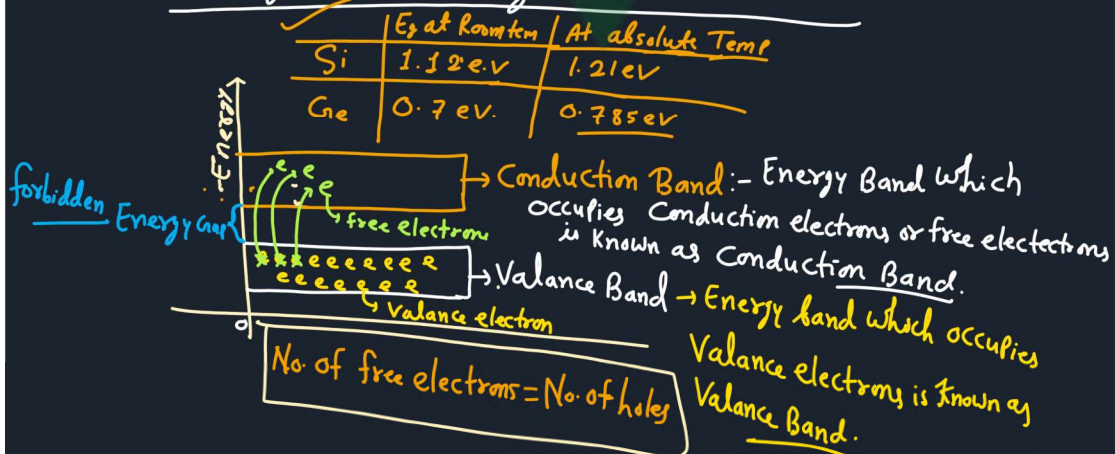



9/6 Temperature is increased, Conductivity is also increased.  
Resistivity is decreased.

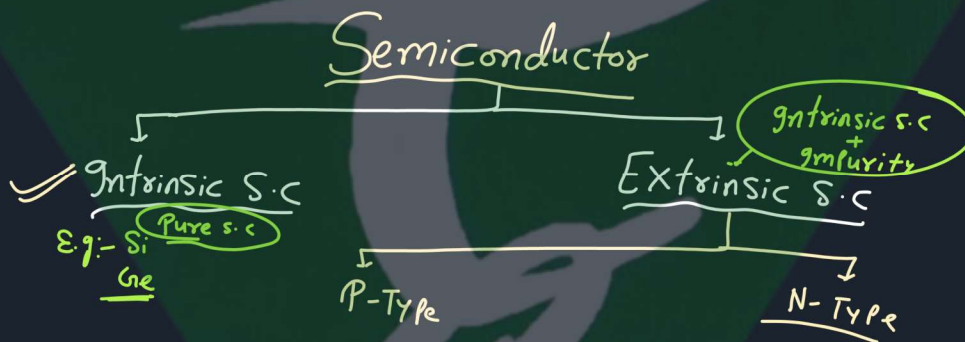$T \uparrow R \downarrow$   $\star$  S.C. has -ve temperature Co-efficient of Resistance  
 $T \downarrow R \uparrow$   $\star$  At Absolute temperature S.C. behaves as an Insulator.



## Extrinsic S.C

→ Extrinsic S.C is the Combination of Intrinsic S.C and Impurity.

→ Impurity is also known as Doppend.

There are two types of doppend (Impurity).

- ① Trivalent impurity (III<sup>rd</sup>) (B, Al, Ga, In, Ti)
- ② Penta Valent impurity (V<sup>th</sup>) (N, P, As, Sb, Bi)



→ Intrinsic S.C + Trivalent Impurity = P-Type S.C  
(B, Al, Ga, In, Tl)

→ Intrinsic S.C + Pentavalent Impurity = N-Type S.C  
(N, P, As, Sb, Bi)

i.e. There are two types of Extrinsic S.C ⇒

① P-Type S.C →

② N-Type

TECHNICAL CLASSES

Doping ⇒ The Process of adding  
Impurity is called doping.  
or

→ The Process of adding suitable impurity in proper manner  
to increase conductivity is called Doping.

P-Type S.C



## P-Type S.C

P-Type S.C is the Combination of Intrinsic S.C and Trivalent Impurity. [Trivalent Impurity is known as Acceptor]

Str. of P-Type S.C is Shown below:→



From the Str. it is clear that in P-Type S.C holes are created so,

Number of holes is larger than no. of free electrons



P Type S.C

Holes - Majority  
free electrons - Minority

→ P-Type S.C is also electrically Neutral.

P-Type = Intrinsic S.C + Trivalent Imp.



P-Type S.C




## N-Type S.C

N-Type S.C is the Combination of Intrinsic S.C and

PentaValent Impurity. [Donor]


The Str. of N-Type S.C is Shown below:-

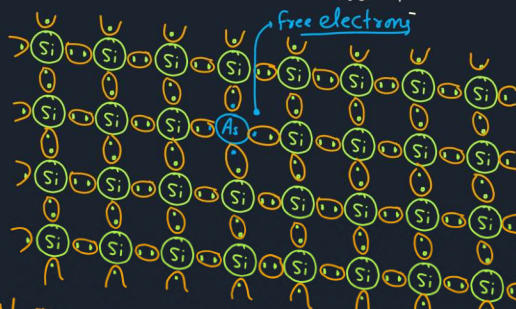

N-Type S.C is also electrically Neutral.

From the Str. it is Clear that Number of free electrons are larger than no. of holes.

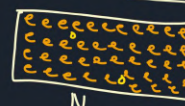Majority → free electrons  
Minority → Holes.




N



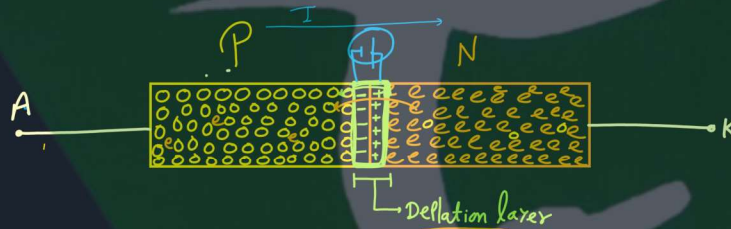
## P-N Junction Diode

When a P Type material brings near to N-Type material, then a boundary or interface is created between both materials. This is known as P-N Junction. P-N Junction has two terminals Anode and Cathode so It is named as P-N Junction Diode.

The Schematic diagram of P-N Junction is shown below:-



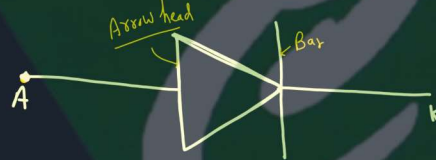Symbol of P-N Junction diode is shown below:⇒



→ Due to Different Concentration gradient Current flows in P-N Junction diode, This Current is known as diffusion Current.

→ But Main Current of diode is Drift Current.

Drift Current generates in diode due to applied Electric field

Apply Electric field means Connection of Cell or Battery

→ Connection of Cell or Battery is known as Biasing.



P-N Junction is operated in two different Biasing modes.

① Forward Biasing


② Reverse Biasing

→ Biasing:- Biasing is a technique to establish electric field across terminals of diode for proper operation.

## TECHNICAL CLASSES
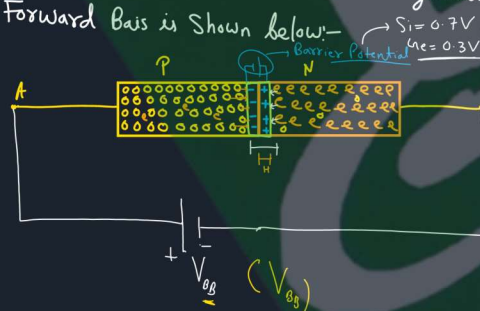
### Forward Biasing

When +ve terminal of cell is connected with P-Type material & -ve terminal of cell is connected with N-Type material, Then P-N Junction is forward biased. The arrangement of Forward Bias is shown below:-




In F.B P-N Junction diode,

Width of depletion layer is reduced.


So Resistance is also reduced.

Resistance is 'few ohm'

& Diode act as ON Switch

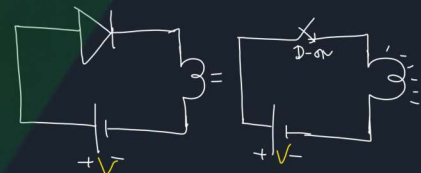
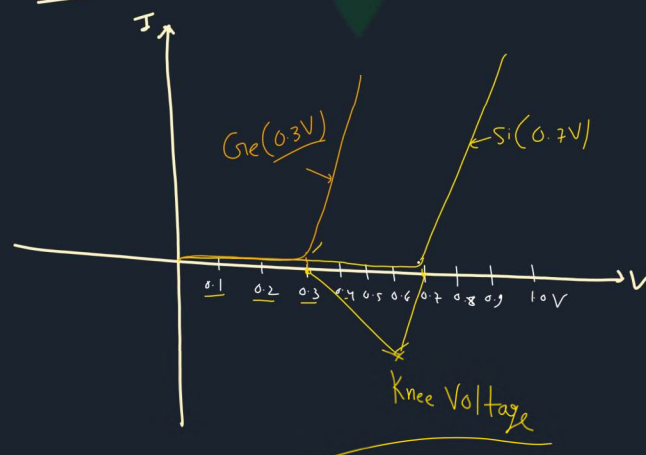
### V-I Characteristics of forward Bias P-N Junction





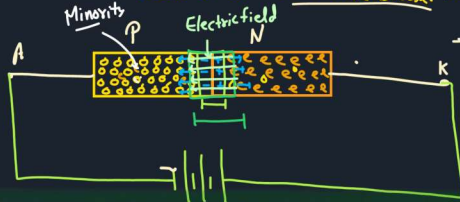
## Reverse Biasing




When +ve terminal of battery is connected with N-Type Material and -ve terminal of battery is connected with P-Type material, then PN Junction diode is said to be in Reverse Bias. This is shown below:-




- The width of Depletion layer is increased in R.B
- Resistance is also increased (in  $M\Omega$ )
- Due to flow of minority charge leakage current flows. Leakage current is also known as Reverse saturation current.

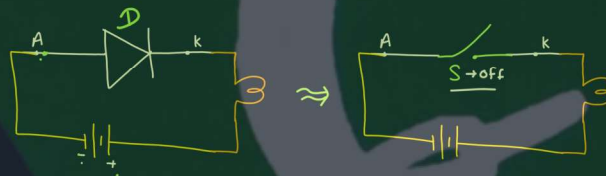→ Diode act as off switch in Reverse Bias.



Note:- Diode is a Unidirectional Switch.  
 In F.B Diode acts as ON Switch  
 & In R.B Diode acts as off Switch.

## V-I Characteristic of Diode in R.B

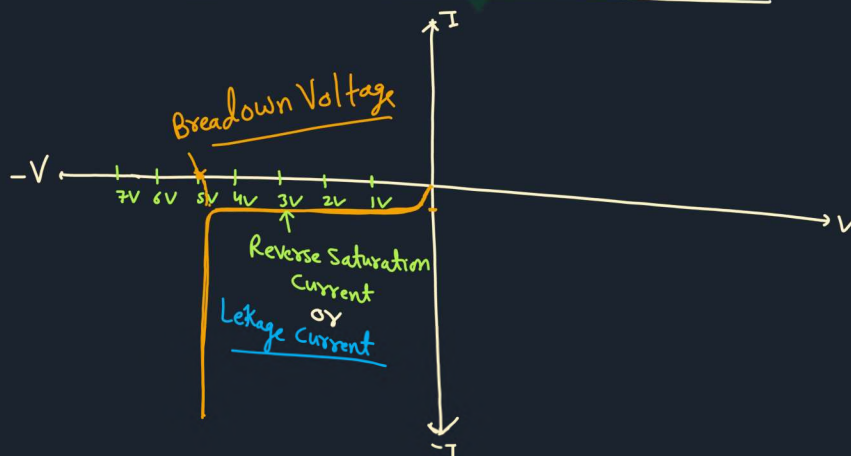



# Transistor

## Transfer of Resistor

Amplifier: - Ackt that increases the strength of input signal.

## Transistor


→ Transistor is a Solid State Electronics device in which electrical signal transfers either from low Resistance to high Resistance or high Resistance to low Resistance.

or

Transistor is a Solid State Electronic device which act as a Switch or Amplifier.
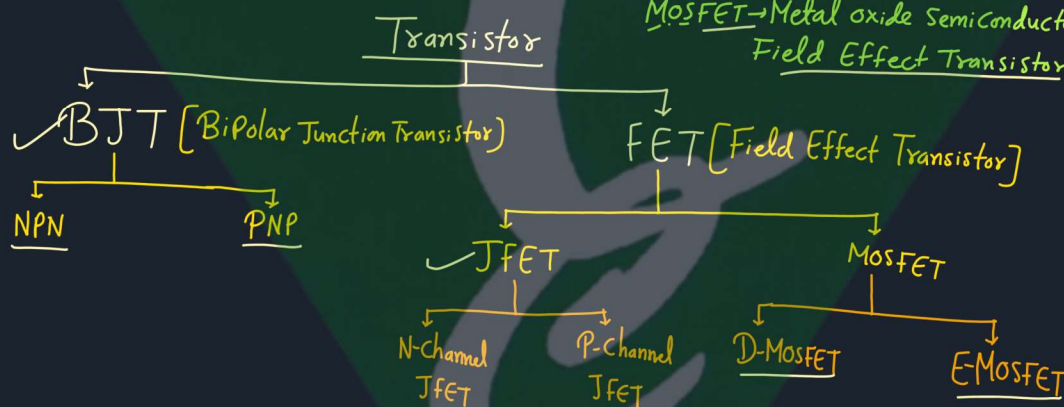
## Classification of Transistor

JFET → Junction Field Effect Transistor  
MOSFET → Metal oxide Semiconductor Field Effect Transistor



## BJT

- BJT Stands for BiPolar Junction Transistor.
- When a different type of Extrinsic Semiconductor is Sandwiched between two similar Extrinsic Semiconductor. then a BJT is formed.

- ① NPN Transistor
  - ② PNP Transistor
- Both are the type of BJT.



→ BJT is a three terminal semiconductor device.  
It has 3 layers and 2 Junctions.

→ These layers are:-


① Emitter:- Emitter is heavily doped and moderately in size.

② Base:- Base is lightly doped and smallest in size.


③ Collector:- Collector is moderately doped and the largest in size.

A/c to Doping:  $E > C > B$  / A/c to Size:  $C > E > B$

Schematic diagram of NPN Transistor

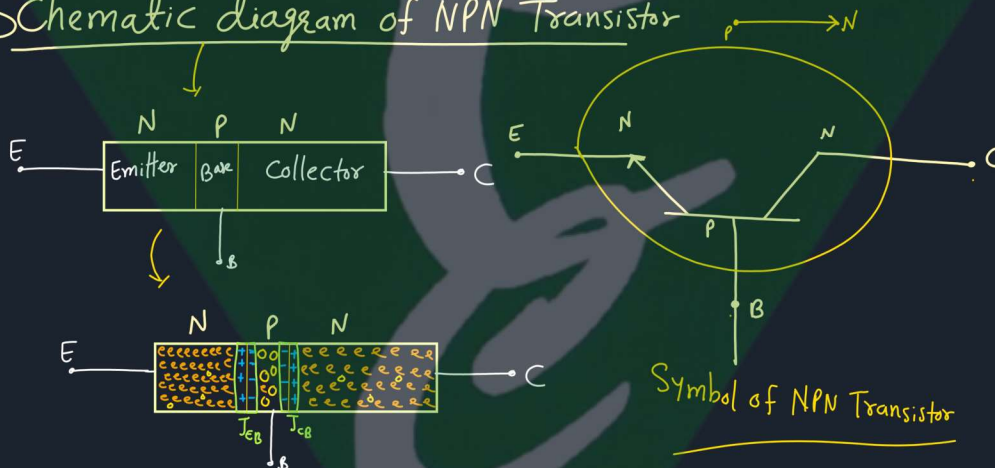

Schematic diagram and symbol of PNP

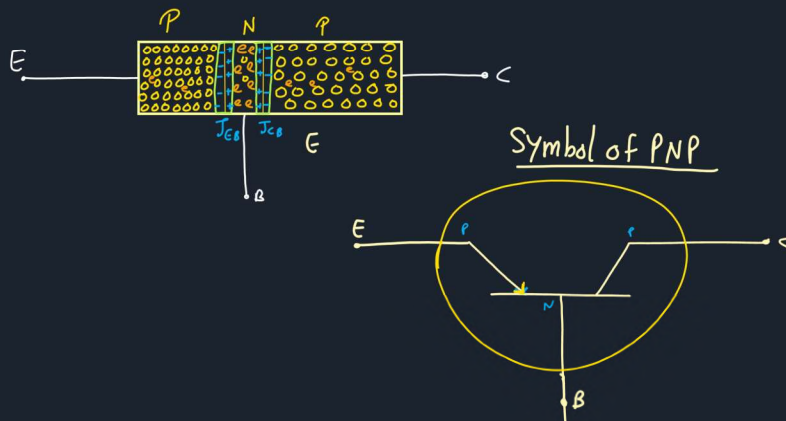






## Operation of NPN Transistor

→ NPN is a type of BJT, which is formed when a P-type material is sandwiched between two N-type material.

Generally NPN transistor is operated in Active or Normal mode. In this mode transistor acts as an amplifier.

For Active mode Input Junction is forward biased, and output Junction is Reverse biased.

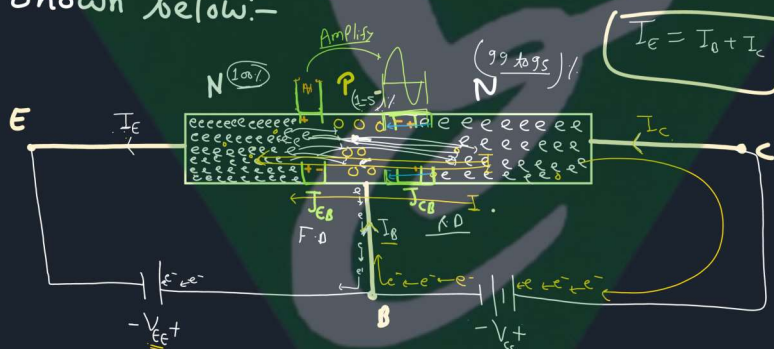The arrangement of Schematic diagram in active mode is shown below:-



→ We apply forward Voltage  $V_{EE}$  across ( $J_{EB}$ )

Emitter Base Junction, This Electric field ( $V_{EE}$ )

breaks the Junction and due to  $V_{EE}$  Electrons of

Emitter is energized to move into P-type materials.

When energized electron enter into P-type material then 1 to 5%

Electrons are neutralized with holes of P-type materials.



Now  $J_{CB}$  is Reverse bias with the  $V_{CC}$ , then an Electric field developed across the Junction  $J_B$  and Width of depletion is increased so Resistance is also increased.

→ This Electric field supports the flow of electrons from Base to Collector side, but due to resistive effect Junction is heat up and at a Particular Voltage Junction breaks and 99 to 95% electrons are collected in collector region so, Current flows from Collector to Emitter layer.

$$I_E = I_B + I_C$$

$$I_E \rightarrow mA$$

$$I_B \rightarrow \mu A$$

$$I_C \rightarrow mA$$

→ Smallest

Transistor

Transfer of Resistor

Transistor

Amplifier:- Ackt that increases the strength of input signal.


→ Transistor is a Solid State Electronics device in which electrical signal transfers either from low Resistance to high Resistance or high Resistance to low Resistance.

or

Transistor is a Solid State Electronic device which act as a Switch or Amplifier.



# Classification of Transistor

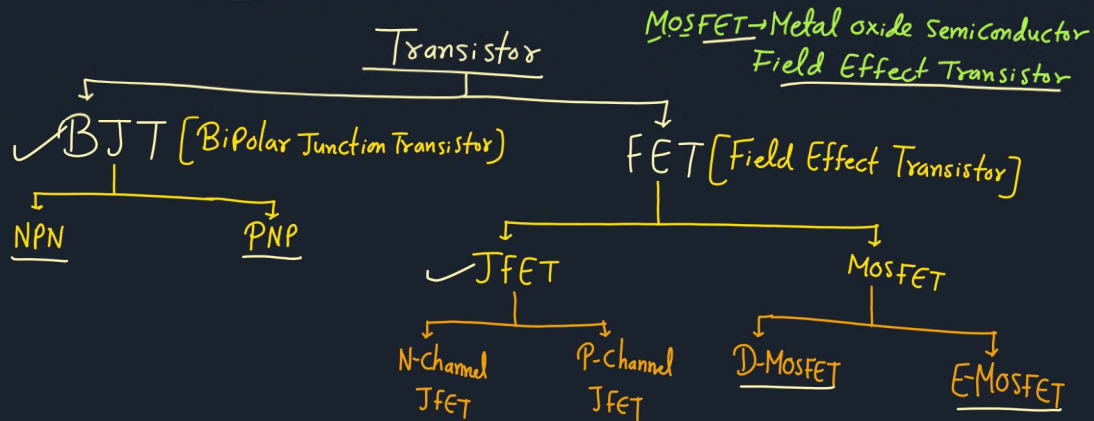

## TECHNICAL CLASSES

### BJT

- BJT Stands for Bipolar Junction Transistor.
- When a different type of Extrinsic Semiconductor is Sandwiched between two similar Extrinsic Semiconductor, then a BJT is formed.

- ① NPN Transistor
  - ② PNP Transistor
- Both are the type of BJT.

- BJT is a three terminal Semiconductor device.
- It has 3 layers and 2 Junctions.


→ These layers are:-

- ① Emitter:- Emitter is heavily doped and moderately in size.
  - ② Base:- Base is lightly doped and smallest in size.
  - ③ Collector:- Collector is moderately doped and the largest in size.
- |                              |                            |
|------------------------------|----------------------------|
| A/c to Doping<br>$E > C > B$ | A/c to Size<br>$C > E > B$ |
|------------------------------|----------------------------|






## Schematic diagram of NPN Transistor

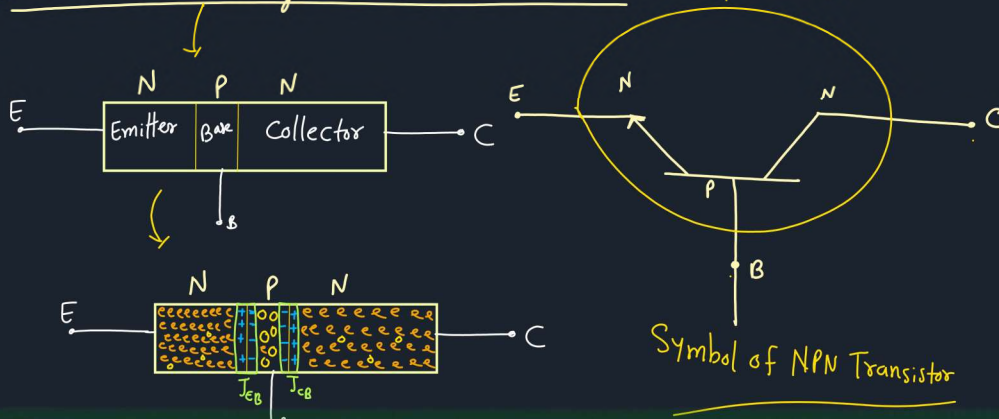

TECHNICAL CLASSES

## Schematic diagram and symbol of PNP

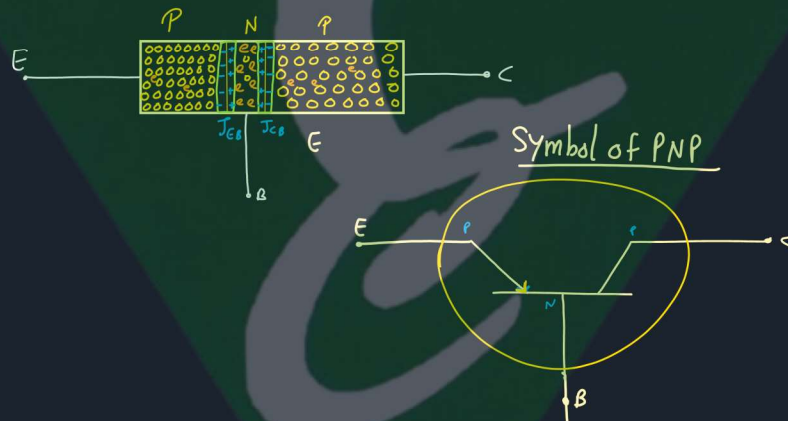


Operation:-

$\frac{I_E}{J_{EB}}$	$\frac{I_C}{J_{CB}}$	Mode	Work as
F.B	F.B	Saturation Mode	ON Switch
R.B	R.B	Cut off Mode	Off Switch
✓ <u>F.B</u>	<u>R.B</u>	Active Mode or Normal Mode.	Amplifier



## Operation of NPN Transistor

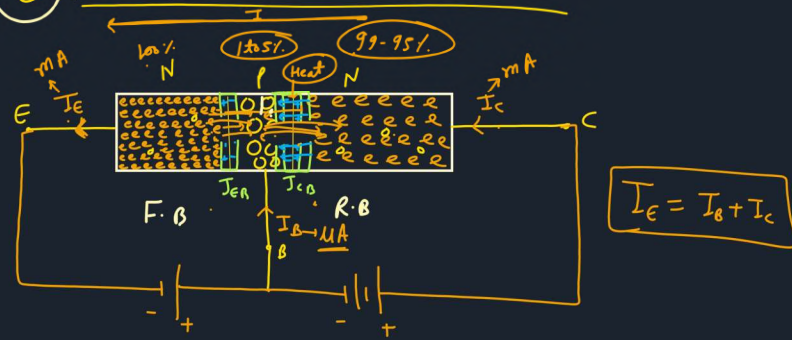

$$\frac{I_E}{\sigma/R} = I_B + \underbrace{I_C}_{I/R}$$


## \* Configuration of BJT

I/P  $\rightarrow$  Base  
O/P  $\rightarrow$  collector

There are 3 type of Configuration

- ① Common Base [C.B]
- ② Common Emitter [C.E]
- ③ Common Collector.


## Common Base

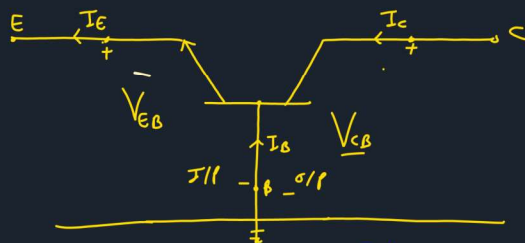

Input Current =  $I_E$   
Input Voltage =  $V_{E\beta}$

Output Current =  $I_c$   
Output Voltage  $V_{c0}$


## Common Emitter connection

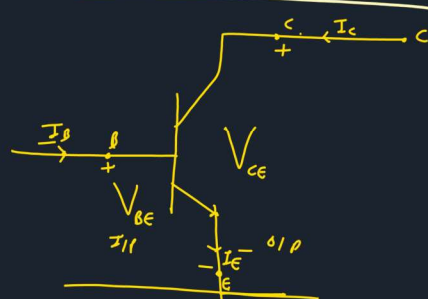

Input current = $I_0$	output current = $I_c$
Input Voltage = $V_{EB}$	output Voltage = $V_{CE}$



## Common Collector

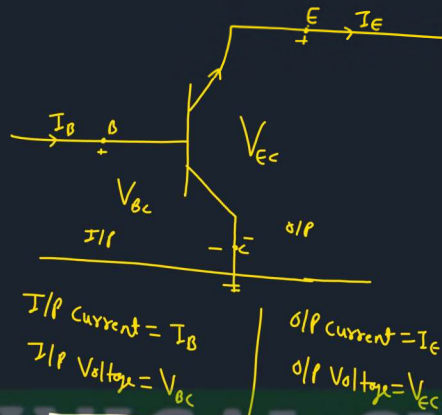

JFET

## Configuration of BJT

$I/P \rightarrow \text{Base}$   
 $O/P \rightarrow \text{Collector}$

Parameter	C.B	C.E	C.C
Ckt	<p> <math>I/P \text{ Current} = I_E</math>  <math>I/P \text{ Voltage} = V_{EB}</math>  <math>O/P \text{ Current} = I_C</math>  <math>O/P \text{ Voltage} = V_{EC}</math> </p>	<p> <math>I/P \text{ Current} = I_B</math>  <math>I/P \text{ Voltage} = V_{EB}</math>  <math>O/P \text{ Current} = I_C</math>  <math>O/P \text{ Voltage} = V_{CE}</math> </p>	<p> <math>I/P \text{ Current} = I_B</math>  <math>I/P \text{ Voltage} = V_{BE}</math>  <math>O/P \text{ Current} = I_E</math>  <math>O/P \text{ Voltage} = V_{EC}</math> </p>

## JFET


JFET stands for Junction Field Effect Transistor.

- It is a three terminal Semiconductor device.  
It's terminals are Source, Gate & Drain.
- It is device in which current conducts only due to majority charge. So JFET is unipolar.
- JFET is a Voltage Controlled device.
- JFET has high Input Impedance.
- JFET is a Voltage Controlled Current Source device.




## Construction details of JFET

① n-channel JFET

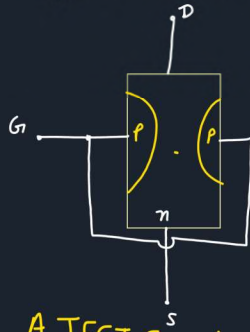


② P-Channel JFET

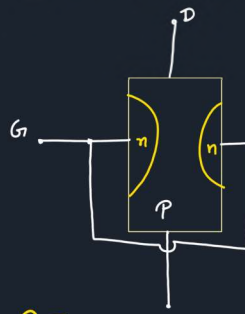


A JFET consists of N-Type or P-Type Si-Bar containing two P-N Junction at side. The bar forms the conducting channel for the charge carrier.  
If bar of N-Type then n-channel JFET & P-Type then P-channel JFET.
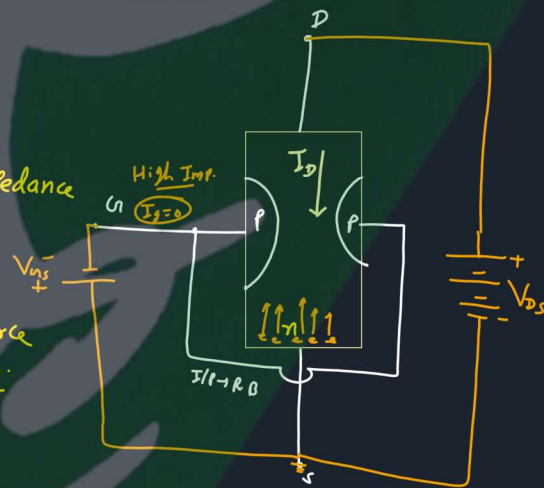
## JFET Polarities

- ① The input circuit of JFET is Reverse Biased. So Input Impedance of JFET is high.
- ② The Drain is so Biased with Source that drain current can be flow.
- ③ If  $I_a = 0$ ,  $I_s = I_D$



## FET

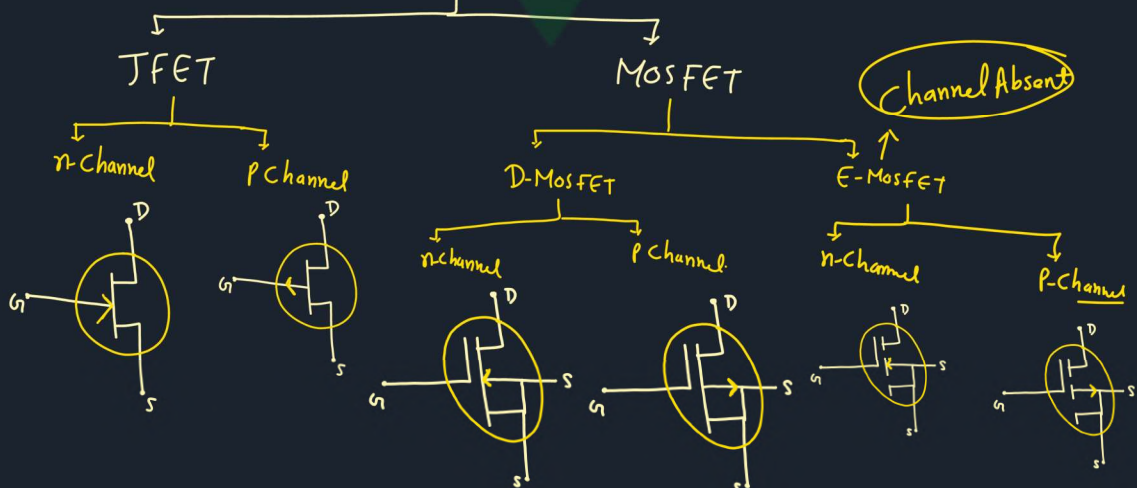

Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24



Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24





## Number System

A System in which Set of Symbols or digits is used is known as number system.

There are two types of number system:-

- ① Non - Positional Number System
- ② Positional Number system

## TECHNICAL CLASSES

### \* Non Positional Number System

It is a System in which digits of it's any number have no any Place Value.

E.g:- Roman Number,

i  
ii  
iii  
iv  
v  
vi  
vii

### \* Positional Number system

It is a System in which digits of it's any number have Place Value or Weight.

E.g:- Decimal No. System

2 4 5  
Hundred Tens ones

$(d_{n-1} \dots d_2 d_1 d_0)_x$   
 $\downarrow \quad \downarrow \quad \downarrow \quad \downarrow$   
 $x^{n-1} \dots x^2 x^1 x^0 \leftarrow \text{Place Value.}$

It is denoted as  $(d_{n-1} \dots d_2 d_1 d_0)_x$

Here x is base

? The Value of x is equal to the number of digits used in system.

$x \rightarrow 2 \text{ to } 36$



$r$	Symbol
✓ 2	0, 1 → Binary Number System
3	0, 1, 2
4	0, 1, 2, 3
...	
✓ 8	0, 1, 2, 3, 4, 5, 6, 7 → Octal No. System
✓ 10	0, 1, 2, 3, 4, 5, 6, 7, 8, 9 → Decimal No. System
...	
✓ 16	0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F <sub>10 11 12 13 14 15</sub>

## I) Conversion of any Number to Decimal Number & Vice-Versa

$$\rightarrow \left( \begin{matrix} d_3 & d_2 & d_1 & d_0 \\ \times r^3 & \times r^2 & \times r^1 & \times r^0 \end{matrix} \right)_r \rightarrow ( \quad )_{10}$$

$$x_3 + x_2 + x_1 + x_0 = \text{Result}$$

E.g:-  $(327)_8 \rightarrow (215)_{10}$

$$\begin{aligned} 7 \times 8^0 &= 7 \times 1 = 7 \\ 2 \times 8^1 &= 2 \times 8 = 16 \\ 3 \times 8^2 &= 3 \times 64 = 192 \\ \hline &215 \end{aligned}$$

$$\begin{array}{r|rr|r} 8 & 215 & & 7 \\ \hline 8 & 26 & & 2 \\ \hline & 3 & & \end{array}$$

$(327)_8$

$$\left( \begin{matrix} 2 & 1 & 3 \\ 6^2 & 6^1 & 6^0 \end{matrix} \right)_6 \rightarrow (81)_{10}$$



$$\begin{aligned} 3 \times 6^0 &= 3 \times 1 = 3 \\ 1 \times 6^1 &= 1 \times 6 = 6 \\ 2 \times 6^2 &= 2 \times 36 = 72 \\ \hline &81 \end{aligned}$$

$$\begin{array}{r|rr|r} 6 & 81 & & 3 \\ \hline 6 & 13 & & 1 \\ \hline & 2 & & \end{array}$$

$213$

$$(23A)_{16} \rightarrow (570)_{10}$$
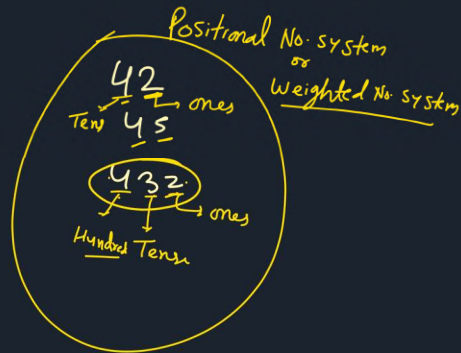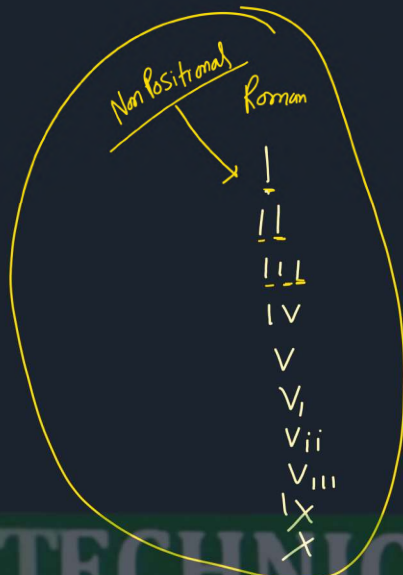
$$\begin{aligned} 10 \times 16^0 &= 10 \times 1 = 10 \\ 3 \times 16^1 &= 3 \times 16 = 48 \\ 2 \times 16^2 &= 2 \times 256 = 512 \\ \hline &570 \end{aligned}$$



## TECHNICAL CLASSES

### Conversion of Any No. system to Decimal Number

$$(d_{n-1} \dots d_2 d_1 d_0)_r \rightarrow ( \quad )_{10}$$

$$\begin{aligned} & \rightarrow d_0 \times r^0 = x_0 \\ & \rightarrow d_1 \times r^1 = x_1 \\ & \rightarrow d_2 \times r^2 = x_2 \\ & \vdots \\ & \rightarrow d_{n-1} \times r^{n-1} = x_{n-1} \end{aligned}$$

Add = Result

### ✓ A) Binary to Decimal.

$$(b_{n-1} \dots b_2 b_1 b_0)_2 \rightarrow ( \quad )_{10}$$

$$\begin{aligned} & \rightarrow b_0 \times 2^0 = x_0 \\ & \rightarrow b_1 \times 2^1 = x_1 \\ & \rightarrow b_2 \times 2^2 = x_2 \\ & \vdots \\ & \rightarrow b_{n-1} \times 2^{n-1} = x_{n-1} \end{aligned}$$

Add = Result





E.g. -  $(10110)_2 \rightarrow (22)_{10}$

$$\begin{aligned} &0 \times 2^0 = 0 = 0 \\ &1 \times 2^1 = 1 \times 2 = 2 \\ &1 \times 2^2 = 1 \times 4 = 4 \\ &0 \times 2^3 = 0 = 0 \\ &1 \times 2^4 = 1 \times 16 = 16 \end{aligned}$$

$$(110110)_2 \rightarrow (54)_{10}$$

$$32 + 16 + 4 + 2 = 54$$

$$(1111)_2 \rightarrow (15)_{10}$$

$$(100010)_2 \rightarrow (34)_{10}$$

## TECHNICAL CLASSES

### B) Octal to Decimal

$$(O_{n-1} \dots O_2 O_1 O_0)_8 \rightarrow ( )_{10}$$

$$\begin{aligned} &O_0 \times 8^0 = x_0 \\ &O_1 \times 8^1 = x_1 \\ &O_2 \times 8^2 = x_2 \\ &\vdots \\ &O_{n-1} \times 8^{n-1} = x_{n-1} \end{aligned}$$

$$\text{Add} = \text{Result}$$

E.g. -  $(217)_8 \rightarrow (143)_{10}$

$$\begin{aligned} &2 \times 8^2 = 2 \times 64 = 128 \\ &1 \times 8^1 = 1 \times 8 = 8 \\ &7 \times 8^0 = 7 \times 1 = 7 \\ &\hline &143 \end{aligned}$$

$$(145)_8 \rightarrow (101)_{10}$$

$$\begin{aligned} &1 \times 8^2 = 1 \times 64 = 64 \\ &4 \times 8^1 = 4 \times 8 = 32 \\ &5 \times 8^0 = 5 \times 1 = 5 \\ &\hline &101 \end{aligned}$$

### C) Hexadecimal to Decimal

$$(H_{n-1} \dots H_2 H_1 H_0)_{16} \rightarrow ( \quad )_{10}$$

$$\begin{aligned} H_0 \times 16^0 &= x_0 \\ H_1 \times 16^1 &= x_1 \\ H_2 \times 16^2 &= x_2 \\ &\vdots \\ H_{n-1} \times 16^{n-1} &= x_n \end{aligned}$$

$$\begin{array}{cccccc} A & B & C & D & E & F \\ 10 & 11 & 12 & 13 & 14 & 15 \end{array} \quad \text{Add} = \text{Result}$$

Ex:-

$$(25A)_{16} \rightarrow (602)_{10}$$

$$\begin{array}{r} 2 \quad 5 \quad A \\ \downarrow \quad \downarrow \quad \downarrow \\ 2 \times 16^2 = 2 \times 256 = 512 \\ 5 \times 16^1 = 5 \times 16 = 80 \\ 10 \times 16^0 = 10 \times 1 = 10 \\ \hline 602 \end{array}$$

## TECHNICAL CLASSES

### ★ Conversion from Decimal to Any Number

$$(d_{n-1} \dots d_2 d_1 d_0)_{10} \rightarrow ( \quad )_r$$

$r$	$d_{n-1} \dots d_2 d_1 d_0$	Rem.
$r$	$x_{n-1} \dots x_2 x_1 x_0$	$r_1$
$r$	$y_{n-1} \dots y_2 y_1 y_0$	
$\vdots$		
$r$		$r_{n-1}$

### \* Decimal to Binary

$$(22)_{10} \rightarrow (10110)_2$$

2	22	0
2	11	1
2	5	1
2	2	0
	1	

Trick:-

$$(22)_{10} \rightarrow ( \cancel{1} \frac{1}{16} \frac{0}{8} \frac{1}{4} \frac{1}{2} \frac{0}{1} )_2$$

$$\cancel{1} \frac{1}{16} \frac{0}{8} \frac{1}{4} \frac{1}{2} \frac{0}{1}$$

$$(15)_{10} \rightarrow (1111)_2$$

$$\frac{1}{8} \frac{1}{4} \frac{1}{2} \frac{1}{1}$$

$$(54)_{10} \rightarrow (110110)_2$$

$$\cancel{1} \frac{1}{32} \frac{1}{16} \frac{0}{8} \frac{1}{4} \frac{1}{2} \frac{0}{1}$$



## Decimal to Octal

$$(d_{n-1} \dots d_2 d_1 d_0)_{10} = ( \quad )_8$$

E.g:-  $(143)_{10} = (217)_8$  |  $(101)_{10} \rightarrow (145)_8$

8	143	7
8	17	1
	2	

8	101	5
8	12	4
	1	

TECHNICAL CLASSES

## Decimal to Hexadecimal

$$(602)_{10} \rightarrow (25A)_{16}$$

16	602	10(A)
16	37	5
	2	

16	602	37
48		
122		
112		
010		

## \* Conversion from Binary to Octal & Vice Versa

$$(b_{n-1} \dots b_5 b_4 b_3 b_2 b_1 b_0)_2 \rightarrow ( \quad )_8$$

3-group  
↓ Decimal  
Value

E.g:-  $(010110100100)_2 \rightarrow (2654)_8$

$(0010000001011010)_2 \rightarrow (140252)_8$





$$\begin{array}{c} \text{4 2 1} \quad \text{4 2 1} \quad \text{4 2 1} \quad \text{4 2 1} \\ (00 \mid 111 \mid 001 \mid 000 \mid 010)_2 \rightarrow (17102)_8 \\ \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \\ 1 \quad 7 \quad 1 \quad 0 \quad 2 \end{array}$$

$$\begin{array}{c} \text{4 2 1} \quad \text{4 2 1} \quad \text{4 2 1} \quad \text{4 2 1} \\ (00 \mid 010 \mid 010 \mid 110)_2 \rightarrow (1226)_8 \\ \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \\ 1 \quad 2 \quad 2 \quad 6 \end{array}$$

## TECHNICAL CLASSES

### Octal to Binary

$$\begin{array}{c} (1226)_8 \rightarrow (001010010110)_2 \\ \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \\ \begin{array}{cccc} \frac{0}{4} \frac{0}{2} \frac{1}{1} & \frac{0}{4} \frac{1}{2} \frac{0}{1} & \frac{0}{4} \frac{1}{2} \frac{0}{1} & \frac{1}{4} \frac{1}{2} \frac{0}{1} \end{array} \end{array}$$

$$\begin{array}{c} (17102)_8 \rightarrow (1111001000010)_2 \\ \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow \\ \begin{array}{ccccc} \frac{0}{4} \frac{0}{2} \frac{1}{1} & \frac{1}{4} \frac{1}{2} \frac{1}{1} & \frac{0}{4} \frac{0}{2} \frac{1}{1} & \frac{0}{4} \frac{0}{2} \frac{0}{1} & \frac{0}{4} \frac{1}{2} \frac{0}{1} \end{array} \end{array}$$

$$\begin{array}{c} \text{4 2 1} \quad \text{4 2 1} \quad \text{4 2 1} \\ (01 \mid 010 \mid 001)_2 \rightarrow (251)_8 \\ \downarrow \quad \downarrow \quad \downarrow \\ 2 \quad 5 \quad 1 \end{array}$$

$$\begin{array}{c} (257)_8 \rightarrow (1010111)_2 \\ \downarrow \quad \downarrow \quad \downarrow \\ 010 \mid 101 \mid 111 \end{array}$$

3	→	$\frac{0}{4}$	$\frac{1}{2}$	$\frac{1}{1}$
7	→	$\frac{1}{4}$	$\frac{1}{2}$	$\frac{1}{1}$
6	→	$\frac{1}{4}$	$\frac{1}{2}$	$\frac{0}{1}$

0	→	$\frac{0}{4}$	$\frac{0}{2}$	$\frac{0}{1}$
1	→	$\frac{0}{4}$	$\frac{0}{2}$	$\frac{1}{1}$
2	→	$\frac{0}{4}$	$\frac{1}{2}$	$\frac{0}{1}$
3	→	$\frac{0}{4}$	$\frac{1}{2}$	$\frac{1}{1}$
4	→	$\frac{1}{4}$	$\frac{0}{2}$	$\frac{0}{1}$
5	→	$\frac{1}{4}$	$\frac{0}{2}$	$\frac{1}{1}$
6	→	$\frac{1}{4}$	$\frac{1}{2}$	$\frac{0}{1}$
7	→	$\frac{1}{4}$	$\frac{1}{2}$	$\frac{1}{1}$



## Binary to Hexadecimal

$$(b_{n-1} \dots b_5 b_4 b_3 b_2 b_1 b_0)_2 \rightarrow (\quad)_{16}$$

4 bit

$$\begin{array}{c|c|c|c} \begin{smallmatrix} 2 & 1 \\ 0 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 0 & 1 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 0 & 0 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 1 & 1 & 0 \end{smallmatrix} \\ \hline 3 & 2 & 8 & 6 \end{array}_2 \rightarrow (3286)_{16}$$

10 - A  
11 - B  
12 - C  
13 - D  
14 - E  
15 - F

$$\begin{array}{c|c|c|c|c} \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 1 & 0 & 1 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 0 & 0 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 1 & 0 & 0 & 1 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 0 & 1 & 1 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 1 & 1 & 1 & 0 \end{smallmatrix} \\ \hline 5 & 1 & 9 & 3 & E \end{array}_2 \rightarrow (5193E)_{16}$$

TECHNICAL CLASSES

$$\begin{array}{c|c|c|c} \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 1 & 0 & 0 & 1 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 0 & 1 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 0 & 1 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 1 & 0 & 0 \end{smallmatrix} \\ \hline 1 & 9 & 2 & 4 \end{array}_2 \rightarrow (1924)_{16}$$

$$\begin{array}{c|c|c|c|c} \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 1 & 0 & 1 & 1 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 1 & 1 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 1 & 0 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 1 & 0 & 1 & 0 \end{smallmatrix} & \begin{smallmatrix} 5 & 4 & 2 & 1 \\ 0 & 0 & 1 & 1 \end{smallmatrix} \\ \hline 2 & E & 4 & A & 3 \end{array}_2 \rightarrow (2E4A3)_{16}$$

## Hexadecimal to Binary

0 → 0000  
1 → 0001  
2 → 0010  
3 → 0011  
4 → 0100  
5 → 0101  
6 → 0110  
7 → 0111  
8 → 1000  
9 → 1001  
A → 1010  
B → 1011  
C → 1100  
D → 1101  
E → 1110  
F → 1111

$$(3A2B)_{16} \rightarrow (11101000101011)_2$$

0011 1010 0010 1011

$$(57AC)_{16} \rightarrow (101011110101100)_2$$

1010 0111 1010 1100



## Hexadecimal to Octal

$$( \quad )_{16} \rightarrow ( \quad )_2 \rightarrow ( \quad )_8$$

$$(57AC)_{16} \rightarrow (0101\ 0111\ 1010\ 1100)_2 \rightarrow (53654)_8$$

$$(3A2B)_{16} \rightarrow (0011\ 1010\ 0010\ 1011)_2 \rightarrow (35053)_8$$

## TECHNICAL CLASSES

## Octal to Hexadecimal

$$( \quad )_8 \rightarrow ( \quad )_2 \rightarrow ( \quad )_{16}$$

$$(35053)_8 \rightarrow (3A2B)_{16}$$

$$(0011\ 1010\ 0010\ 1011)_2$$

$$(53654)_8 \rightarrow (57AC)_{16}$$

$$(0101\ 0111\ 1010\ 1100)_2$$

$$(67AB)_{16} \rightarrow (63653)_8$$

$$(0110\ 0111\ 1010\ 1011)_2$$





H.W

$$(73A8)_{16} \rightarrow ( )_8$$

$$(5763)_8 \rightarrow ( )_{16}$$

$$(2345)_8 \rightarrow ( )_{16}$$

$$(110010110)_2 \rightarrow ( )_8 = ( )_{16}$$

$$(111100010000)_2 \rightarrow ( )_8 = ( )_{16}$$

$$(217)_8 \rightarrow ( )_{10}$$

$$(275)_{10} \rightarrow ( )_2$$

$$(1010010)_2 \rightarrow ( )_{10}$$

TECHNICAL CLASSES

$$(27.75)_{10} \rightarrow (11011.11)_2$$

$$(27.25)_{10} \rightarrow (11011.01)_2$$

$$\times \frac{1}{k} \frac{1}{8} \frac{0}{4} \frac{1}{2} \frac{1}{1}$$

$$\begin{array}{r} .75 \\ \times 2 \\ \hline 1.50 \rightarrow 1 \\ \times 2 \\ \hline 1.00 \rightarrow 1 \end{array}$$

$$\begin{array}{r} .25 \\ \times 2 \\ \hline 0.50 \rightarrow 0 \\ \times 2 \\ \hline 1.00 \rightarrow 1 \end{array}$$

$$(15.625)_{10} \rightarrow (1111.101)_2$$

$$15 \rightarrow 1111$$

$$\begin{array}{r} .625 \\ \times 2 \\ \hline 1.250 \rightarrow 1 \\ \times 2 \\ \hline 0.500 \rightarrow 0 \\ \times 2 \\ \hline 1.000 \rightarrow 1 \end{array}$$

$$\begin{array}{r} .625 \\ \times 2 \\ \hline 1.250 \rightarrow 1 \\ \times 2 \\ \hline 0.500 \rightarrow 0 \\ \times 2 \\ \hline 1.000 \rightarrow 1 \end{array}$$

$$.625 \rightarrow .101$$



$$(735.42)_8 \rightarrow (1DD.88)_{16}$$

$$\begin{array}{ccccccc} 000 & | & 11 & 01 & | & 101 & . & 100 & 0 & | & 000 & 0 \\ \hline & & 1 & D & & D & . & 8 & & & 8 & \end{array}$$

$$(253.75)_8 \rightarrow (AB.F4)_{16}$$

$$\begin{array}{ccccccc} 000 & | & 10 & 10 & | & 101 & . & 111 & 1 & | & 010 & 0 \\ \hline & & 0 & A & & B & . & F & & & 4 & \end{array}$$

TECHNICAL CLASSES

$$(1DD.88)_{16} \rightarrow (735.42)_8$$

$$\begin{array}{ccccccc} 000 & | & 11 & 01 & | & 110 & 1 & . & 1000 & | & 1000 \\ \hline & & 7 & 3 & & 5 & . & 4 & & & 2 & \end{array}$$



## Q. Addition

0	10	20
1	11	21
2	12	22
3	13	23
4	14	
5	15	
6	16	
7	17	
8	18	
9	19	

$$(47)_{10} + (35)_{10} = (82)_{10} \checkmark$$

$$(57)_8 + (43)_8 = (122)_8$$

$$(101111)_2 + (100011)_2 = (1010010)_2$$

$$\begin{array}{r} 101111 \\ + 100011 \\ \hline 1010010 \end{array}$$

$$\begin{array}{r} 8 \overline{) 47} \overline{) 7} \\ \underline{5} \end{array}$$

$$\begin{array}{r} 8 \overline{) 35} \overline{) 3} \\ \underline{4} \end{array}$$

$$\begin{array}{r} 8 \overline{) 82} \overline{) 2} \\ \underline{10} \underline{2} \\ 1 \end{array}$$

0	10	20
1	11	21
2	12	22
3	13	
4	14	
5	15	
6	16	
7	17	

TECHNICAL CLASSES

$$(57)_8 + (43)_8 = (122)_8$$

$$\begin{array}{r} 101111 \\ + 100011 \\ \hline 001010010 \\ \underline{1} \quad \underline{2} \quad \underline{2} \end{array}$$

$$\frac{1}{2}$$

$$\begin{array}{r} 0 \\ + 0 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 0 \\ + 1 \\ \hline 1 \end{array}$$

$$\begin{array}{r} 1 \\ + 1 \\ \hline 1 \end{array}$$

$$\frac{1}{2} \rightarrow 10 \quad \frac{1}{3} \rightarrow 11$$

$$\begin{array}{r} 101001 \\ + 011011 \\ \hline 1010100 \end{array}$$

$$(1000110)_2 + (1001)_2 = (100111)_2$$

$$\begin{array}{r} 1000110 \\ + 1001 \\ \hline 1001111 \end{array}$$





$$(47)_8 + (32)_8 = (101)_8$$

$$\begin{array}{r} \begin{array}{cccc} 1 & 0 & 0 & 1 & 1 & 1 \\ + & 0 & 1 & 1 & 0 & 1 & 0 \\ \hline 1 & 0 & 0 & 0 & 0 & 1 & 1 \\ \hline 1 & 0 & 1 & & & & \end{array} \end{array}$$

$$(53)_8 + (35)_8 = (110)_8$$

$$\begin{array}{r} \begin{array}{cccc} 1 & 0 & 1 & 0 & 1 & 1 \\ + & 0 & 1 & 1 & 1 & 0 & 1 \\ \hline 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ \hline 1 & 1 & 0 & & & & \end{array} \end{array}$$

## TECHNICAL CLASSES

$$(3A)_{16} + (47)_{16} = (81)_{16}$$

$$\begin{array}{r} 3A \rightarrow \begin{array}{cccc} 0 & 0 & 1 & 1 & 1 & 0 & 1 & 0 \\ 47 \rightarrow + & 0 & 1 & 0 & 0 & 0 & 1 & 1 \\ \hline 1 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ \hline 8 & 1 & & & & & & \end{array} \end{array}$$

$$\begin{array}{r} (56)_{16} + (67)_{16} = (BD)_{16} \\ \begin{array}{cccc} 0 & 1 & 0 & 1 & 0 & 1 & 1 & 0 \\ + & 0 & 1 & 1 & 0 & 0 & 1 & 1 \\ \hline 1 & 0 & 1 & 1 & 1 & 0 & 1 & 1 \\ \hline B & D & & & & & & \end{array} \end{array}$$

Complements —  $\begin{cases} \rightarrow r\text{'s complement} \\ \rightarrow (r-1)\text{'s complement} \end{cases}$

E.g.:- for Binary ( $r=2$ ) —  $\begin{cases} \rightarrow 2\text{'s complement} \\ \rightarrow 1\text{'s complement} \end{cases}$

Complements are used only for Negative Number



Deciml	Sign Mg. Binary	1's Complement	2's Complement
+0	0000	0000	0000
+1	0001	0001	0001
+2	0010	0010	0010
+3	0011	0011	0011
+4	0100	0100	0100
+5	0101	0101	0101
+6	0110	0110	0110
+7	0111	0111	0111
-7	1111		
-6	1110		
-5	1101		

Rule:-

Given  $(100110)_2$   $\xrightarrow{1's}$   $011001$   $\xrightarrow{2's}$   $011010$  ✓

1's Complement:

$$\begin{array}{r} 111111 \\ - 100110 \\ \hline 011001 \\ \text{1's comp} \rightarrow \end{array}$$

2's Complement = 1's Complement + 1

$$\begin{array}{r} 011001 \\ + 1 \\ \hline 011010 \end{array}$$

Binary  $\xrightarrow{1's \text{ complement}}$

$$(101001)_2 \xrightarrow{1's \text{ comp}} 010110$$

$$(100110)_2 \xrightarrow{1's \text{ comp}} 011001$$

$$(11101)_2 \xrightarrow{1's \text{ complement}} 00010$$

$$\begin{array}{r} 111111 \\ - 101001 \\ \hline 010110 \end{array}$$

$1's + 1 = 2's \text{ comp}$

$$(101001)_2 \xrightarrow{2's} 010111$$

$$\begin{array}{r} 010110 \\ + 1 \\ \hline 010111 \end{array}$$

$$(101001)_2 \rightarrow 010111$$



$$(100100100)_2 \xrightarrow{2's \text{ comp}} 011011100$$

Q Express -45 in 8 bit's 2's complement

$$+45 \rightarrow 00101101$$

32 16 8 4 2 1

$$+45 \rightarrow 00101101 \xrightarrow{2's \text{ complement}} 11010011$$

## TECHNICAL CLASSES

Q Subtract 14 from 46 Using 8 bit 2's complement Arithmetic

$$\begin{array}{r} 46 \\ -14 \\ \hline +32 \end{array}$$

$$\begin{array}{r} 00101101 \\ + 11100100 \\ \hline 10010000 \end{array}$$

Carry MSB

Ignore the carry

$$+14 \rightarrow 00001110$$

↓ 2's

$$-14 = 1110010$$

MSB is 0 So Result is +ve

$$00100000 = +32$$

Q Add -75 to 26 using 8 bit 2's complement Arithmetic

$$\begin{array}{r} 26 \\ -75 \\ \hline -49 \end{array}$$

$$\begin{array}{r} 00011010 \\ + 10110101 \\ \hline 11001111 \end{array}$$

MSB

There is no carry & MSB is 1. So Result is -ve.

$$+75 \rightarrow 01001011$$

32 16 8 4 2 1

$$\downarrow 2's \text{ comp}$$

$$10110101$$

$$11001111 \xrightarrow{2's} 00110001$$

49

MSB → Most Significant bit

LSB → Least Significant bit





find 1's & 2's complement

$$* (100100)_2$$

$$* (111001001)_2$$

$$* (111111)_2$$

$$* (100000)_2$$

$$* (1010010)_2$$

## TECHNICAL CLASSES

### Logic Gate

Device which allows either pass signal or stop signal according to logic is known as logic gate.


or  
Devices which connects load [Bulb, Fan, T.V & Motor etc] to the Source according to proper logic are known as logic gate.

Logic Condition	I/P	O/P
[No] 0		Bulb off (No, Bulb is not glowing)
[Yes] 1		Bulb on (Yes, Bulb is glowing)

### Classification of Logic Gates:-



Concept:-

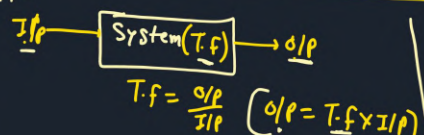

# ① NOT Gate

→ No. of I/P Pins = 1  
No. of o/p Pin = 1

→ Symbol of NOT



T.F of NOT gate is 1 → Complement


Boolean Expression  
 $Y = \bar{A}$   
or  
 $Y = A'$

Defination:- Gate which Produces inverted output is called NOT Gate.

Truth Table


I/P A	O/P Y = $\bar{A}$
0	1
1	0

Electrical ckt

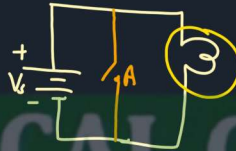

NOT Gate is also known as inverter.

% A = 0

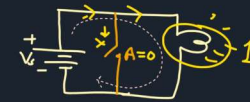

% A = 1



# AND Gate

→ No. of I/P Pins = 2 or More  
No. of o/p Pin = 1

Symbol of AND Gate



Boolean Expression  
 $Y = A \cdot B$


Defination:- A Gate which Produces high output (1) only when all inputs are high (1), otherwise low (0). is called AND Gate.

Truth Table




I/P	A	B	O/P Y = A · B
0	0	0	0
1	0	1	0
2	1	0	0
3	1	1	1

Total Probability of I/P =  $2^{\text{No. of I/P Pins}}$   
E.g.:- No. of I/P Pins = 2  
Total Prob =  $2^2 = 4$

Electrical equivalent ckt:-

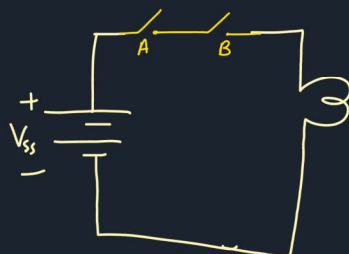

AND Gate acts as Series Switch

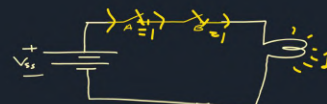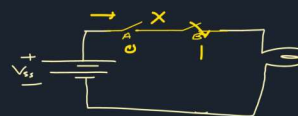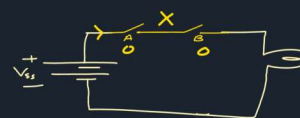

## OR Gate ✓

No. of I/P Pins = 2 or More

No. of o/p Pin = 1

Total Probability of I/P =  $2^{No. of I/P Pins}$

Symbol of OR Gate



$Y = A + B$  - Boolean Expression


Defination:- A Gate which o/p is high (1)

When at least one I/P is high (1)



Truth Table

I/P		O/P
A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

## Electrical equivalent circuit

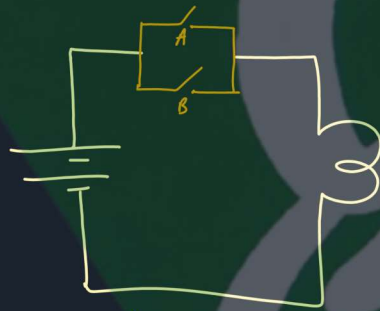

OR Gate acts as Parallel Switch

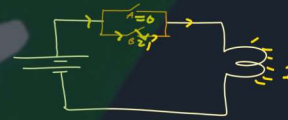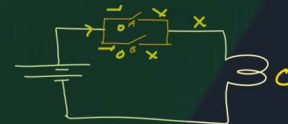



## NAND Gate

Negation of AND

No. of I/P Pins = 2 or More

No. of o/p Pin = 1 Pin

Symbol:-

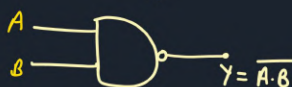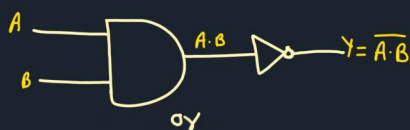

Defination:- A Gate Which o/p is high when at

least one I/P is low (0).




Truth Table

I/P		O/P
A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0





## Electrical Equivalent CKT

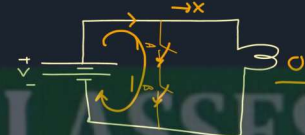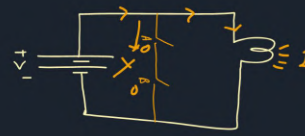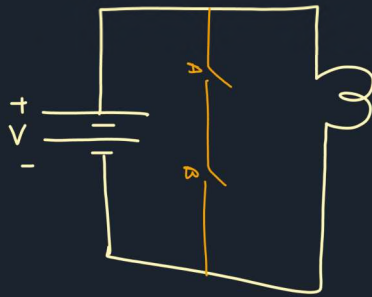

TECHNICAL CLASSES


## NOR Gate

Negation of OR Gate

No. of I/P pins = 2 or More

No. of o/p pin = 1

Symbol :-

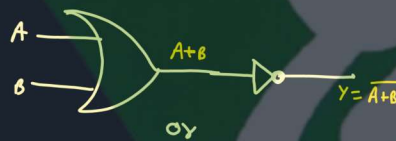


Defination:- A Gate which o/p is low(0) when at least one input is high(1).

Truth Table

I/P		O/P
A	B	$Y = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

## Electrical equivalent CKT

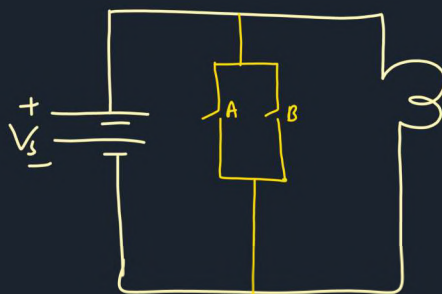



## EX-OR Gate

[Anti Coincident Gate]  
or

Equality Detector

No. of I/P Pins = 2

No. of o/p Pins = 1

Symbol



$$Y = A \oplus B$$

Defination:- A Gate whose o/p is high (1)

When both inputs are different.

Truth Table

I/P		O/P
A	B	$Y = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

## EX-NOR

No. of I/P Pins = 2

No. of o/p Pin = 1

Equality detector

Symbol



$$Y = A \odot B$$

Defination:- A Gate whose o/p is high (1)

When both inputs are same.

Truth Table


I/P		O/P
A	B	$Y = A \odot B$
0	0	1
0	1	0
1	0	0
1	1	1

## Boolean Algebra

- It is the algebra of binary Variables.
- It is also known as two Value algebra because binary Variable have only two Values [0 & 1]
- It is discovered by Jorge Boole in 1854
- It's law & theorem can be effectively used for simplification of Complex Boolean expression.

## 1) NOT Laws:-

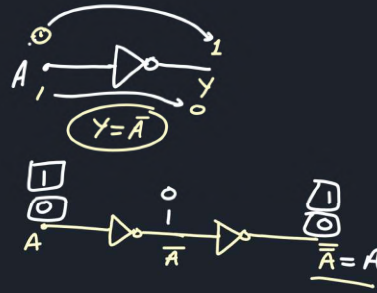
- A)  $\bar{0} = 1$
- B)  $\bar{1} = 0$
- C)  $\bar{\bar{A}} = A$  [ $\bar{\bar{x}} = x$ ]
- D) If  $A=0$ ,  $\bar{A}=1$
- E) If  $A=1$ ,  $\bar{A}=0$



# TECHNICAL CLASSES


## 2) AND Law:-

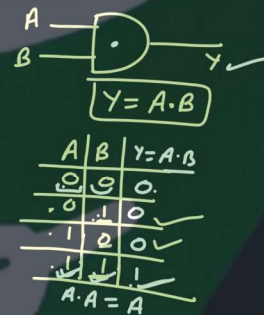- A)  $A \cdot 0 = 0$
- B)  $A \cdot 1 = A$
- C)  $A \cdot A = A$
- D)  $A \cdot \bar{A} = 0$  [ $x \cdot \bar{x} = 0$ ]
- If  $A=0$ ,  $\bar{A}=1$  [ $0 \cdot 1 = 0$ ]
- $A=1$ ,  $\bar{A}=0$  [ $1 \cdot 0 = 0$ ]



## OR Law:-

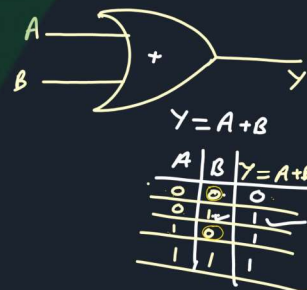- A)  $A + 0 = A$
- B)  $A + 1 = 1$
- C)  $A + A = A$
- $0 + 0 = 0$
- $1 + 1 = 1$
- D)  $A + \bar{A} = 1$  [ $x + \bar{x} = 1$ ]
- If  $A=0$ ,  $\bar{A}=1$
- $0 + 1 = 1$
- If  $A=1$ ,  $\bar{A}=0$
- $1 + 0 = 1$







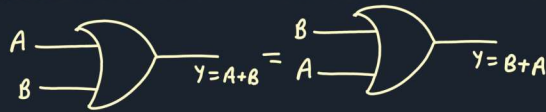
## Commutative Law:

Law:-1)  $A + B = B + A$  or  $A + B + C + D = D + C + A + B$



A	B	$Y = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

B	A	$Y = B + A$
0	0	0
0	1	1
1	0	1
1	1	1

TECHNICAL CLASSES

Law:-2)  $A \cdot B = B \cdot A$  or  $A \cdot B \cdot C = C \cdot A \cdot B$


A	B	$A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

B	A	$B \cdot A$
0	0	0
0	1	0
1	0	0
1	1	1

$[A \cdot B \cdot C \cdot D = B \cdot C \cdot D \cdot A]$

## Associative Law:

Law:-1)  $(A + B) + C = A + (B + C)$

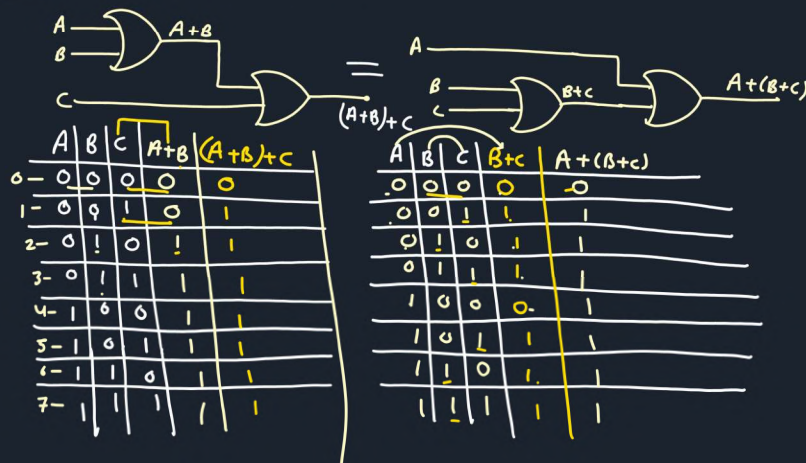

A	B	C	$A + B$	$(A + B) + C$
0	0	0	0	0
1	0	0	0	0
2	0	1	0	1
3	0	1	1	1
4	1	0	1	1
5	1	0	1	1
6	1	1	1	1
7	1	1	1	1

A	B	C	$B + C$	$A + (B + C)$
0	0	0	0	0
1	0	0	0	0
2	0	1	1	1
3	0	1	1	1
4	1	0	0	1
5	1	0	0	1
6	1	1	1	1
7	1	1	1	1



Law:-2

$$(A \cdot B) \cdot C = A \cdot (B \cdot C)$$

## TECHNICAL CLASSES

Distributive Law

Law:-1)  $A \cdot (B + C) = A \cdot B + A \cdot C$

Law:-2)  $A + (B \cdot C) = (A + B) \cdot (A + C)$

V.V.9 → Redundant Literal Rule (RLR)

Law:-1)  $A + \bar{A}B = A + B$   $[x + \bar{x}y = x + y]$

Prove:-  $(A + \bar{A}) \cdot (A + B)$

$1 \cdot (A + B) = A + B$

Law:-2)  $A \cdot (\bar{A} + B) = A \cdot B$

$A \cdot \bar{A} + A \cdot B$

$0 + A \cdot B = A \cdot B$

→ Involution Law:-

$\bar{\bar{A}} = A$

$[\bar{\bar{x}} = x] \quad (\bar{\bar{A} \cdot B} = A \cdot B)$

$\bar{\bar{A} + B} = A + B$

→ Idempotence Law:-

Law:-1)  $A + A + A + \dots = A$

Law:-2)  $A \cdot A \cdot A \cdot \dots = A$

Absorption Law:-

Law:-1)  $A + A \cdot B = A$

$A + A \cdot B + A \cdot B \cdot C + A \cdot B \cdot C \cdot D = A$

Prove:-  $A + A \cdot B$

$A(1 + B)$

$A \cdot 1 = A$



$$\underline{A \cdot (A+B) = A} \checkmark$$

$$\underline{A \cdot A} + A \cdot B$$

$$A + A \cdot B$$

$$A(1+B)$$

$$A \cdot 1 = \underline{A}$$

## TECHNICAL CLASSES

### DE-MORGAN'S THEOREM

This theorem is used to Convert Sum of Product (SOP) Expression into Product of Sum (POS) & Vice Versa.

Note:-  $f(A, B, C)$

$$Y = \underbrace{A \cdot B \cdot C}_{\text{Product term}} + \underbrace{A \cdot C}_{\text{Product term}} + \underbrace{B \cdot C}_{\text{Product term}} + \underbrace{A \cdot \bar{B} \cdot C}_{\text{Product term}} \rightarrow \text{Sum of Product (SOP)}$$

$$Y = \underbrace{(A+B+C)}_{\text{Sum term}} \cdot \underbrace{(B+C)}_{\text{Sum term}} \cdot \underbrace{(\bar{A}+B+C)}_{\text{Sum term}} \rightarrow \text{Product of Sum (POS)}$$

There are two Basic De Morgan's Theorem:-

Theorem:-1 > De Morgan's first theorem explain that

Complement of Sum is equal to Product of Complement.

$$\overline{A+B+C+D} = \bar{A} \cdot \bar{B} \cdot \bar{C} \cdot \bar{D}$$

Complement of Sum = Product of Complement

[Trick:- Breaking the line & Changing the Sign ( $\cdot \leftrightarrow +$ )


$$\overline{A+B+C} = \bar{A} \cdot \bar{B} \cdot \bar{C}$$

$$\overline{A+B+C} = \bar{A} \cdot \bar{B} \cdot \bar{C}$$





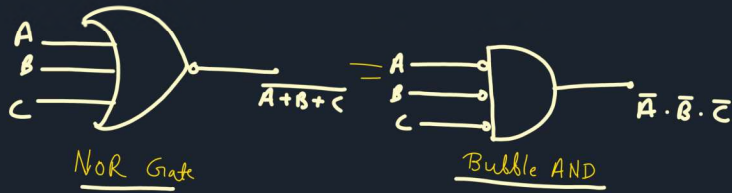
$$\overline{A+B+C} = \bar{A} \cdot \bar{B} \cdot \bar{C}$$


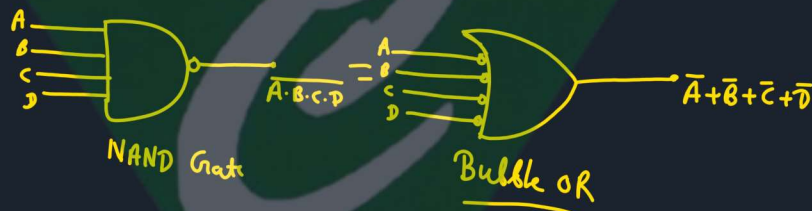
## TECHNICAL CLASSES

Theorem:-2 > De Morgan's 2<sup>nd</sup> theorem states that Complement of Product is equal to the Sum of Complement.

$$\overline{A \cdot B \cdot C \cdot D} = \bar{A} + \bar{B} + \bar{C} + \bar{D}$$



Q Using Basic laws & Theorems Simplify the following Expression.

Q:-  $Z = \overline{x+y} + \overline{x \cdot y} + \overline{x \cdot y}$

Sol:-  $Z = (\overline{x+y}) \cdot (\overline{x \cdot y}) \cdot (\overline{x \cdot y})$

$$Z = (\overline{x+y}) \cdot (\overline{x \cdot y}) \cdot (\overline{x \cdot y})$$

$$Z = (\overline{x+y} + \overline{x \cdot y}) \cdot (\overline{x \cdot y})$$

$$Z = (\overline{x+y} + \overline{x \cdot y}) \cdot (\overline{x \cdot y})$$

$$Z = \overline{x \cdot y} \cdot (\overline{x+y})$$

$$Z = \overline{x \cdot y} + \overline{x \cdot y} = \overline{x \cdot y} + 0 = \overline{x \cdot y}$$

$$\boxed{Z = \overline{x \cdot y}}$$

De Morgan's  
Breaking the line &  
changing the sign

$$\overline{\overline{A}} = A$$

$$[A \cdot A = A]$$

$$[A + A = A]$$

$$[A \cdot \overline{A} = 0]$$

$$[ABC + ABC = ABC]$$

$$\underline{A + A + A + \dots = A}$$

$$2) Z = \overline{B \cdot \overline{C} \cdot D} + \overline{\overline{A} \cdot C \cdot D}$$

$$\text{Sol}^n \rightarrow Z = (\overline{B \cdot \overline{C} \cdot D}) \cdot (\overline{\overline{A} \cdot C \cdot D})$$

$$Z = (\overline{B} + \overline{\overline{C}} + \overline{D}) \cdot (\overline{\overline{A}} + \overline{C} + \overline{D})$$

$$Z = (\overline{B} + \overline{C} + \overline{D}) \cdot (\overline{A} + C + D)$$

$$Z = \overline{A} \overline{B} C D + \overline{A} \overline{C} \overline{D} D \quad (x \cdot \overline{x} = 0)$$

$$Z = \overline{A} \overline{B} C D + 0$$

$$Z = \overline{A} \overline{B} C D$$

$$Z = (\overline{B \cdot \overline{C} \cdot D}) \cdot (\overline{\overline{A} \cdot C \cdot D})$$

$$Z = (\overline{B} + \overline{\overline{C}} + \overline{D}) \cdot (\overline{A} + C + D) \quad [\overline{\overline{x}} = x]$$

$$Z = (\overline{B} + \overline{C} + \overline{D}) \cdot (\overline{A} + C + D)$$

$$Z = \overline{A} \overline{B} C D + \overline{A} \overline{C} \overline{D} D \quad (x \cdot \overline{x} = 0)$$

$$Z = \overline{A} \overline{B} C D + 0$$

$$Z = \overline{A} \overline{B} C D$$

$$3) Z = (A + B) (\overline{A} + \overline{B})$$

$$Z = A \cdot (\overline{A} + \overline{B}) + B \cdot (\overline{A} + \overline{B})$$

$$Z = \underline{A \cdot \overline{A}} + A \cdot \overline{B} + \overline{A} B + \underline{B \cdot \overline{B}}$$

$$Z = 0 + A \cdot \overline{B} + \overline{A} B + 0$$

$$Z = \underline{\overline{A} B + A \overline{B}} = A \oplus B$$

$$4) Z = \overline{A} \cdot \overline{B} \cdot C + \underline{A B \overline{C}} + \underline{A B C}$$

$$Z = \overline{A} \cdot \overline{B} \cdot C + A B (\overline{C} + C) \quad (A + \overline{A} = 1)$$

$$Z = \overline{A} \cdot \overline{B} \cdot C + A B \cdot 1$$

$$Z = \overline{A} \overline{B} C + A B$$

$$x \oplus y = \overline{x} y + x \overline{y}$$

$$5) Z = \overline{A} \cdot \overline{B} \cdot C + \underline{A \cdot \overline{B} \cdot \overline{C}} + \underline{B \overline{D}}$$

$$Z = \overline{B} (\overline{A} C + A \overline{C}) + B \overline{D}$$

$$= \overline{B} (A \oplus C) + B \overline{D}$$

$$= \overline{B} (A \oplus C + \overline{D})$$



# NAND Gate & NOR Gate

Both are Universal Gate.

Because all Gates can be realized by using only NAND Gate or NOR Gate

## TECHNICAL CLASSES

### Application of NAND Gate


A	B	$Y = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

$$\overline{\overline{A}} = A$$

#### ① NOT Gate by Using NAND




#### ② AND Gate by Using NAND

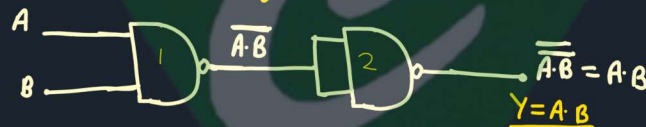


#### ③ OR Gate by Using NAND

Bubble NAND = OR Gate

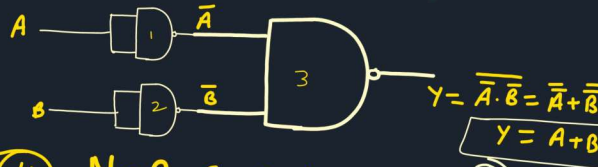

$$\overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A} + \overline{B}} = A + B$$


#### ④ NOR Gate by Using NAND

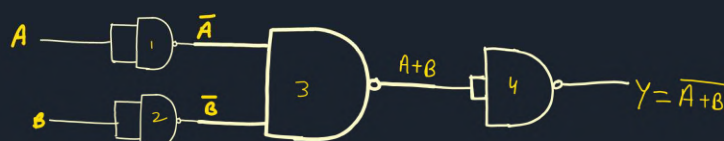







### 5) EX-OR Gate by Using NAND

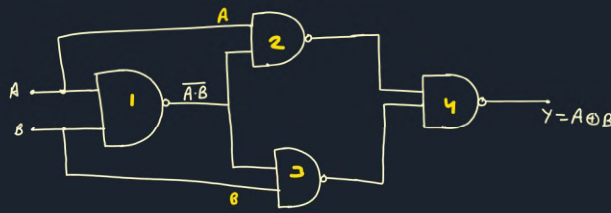

### 6) EX-NOR Gate by Using NAND

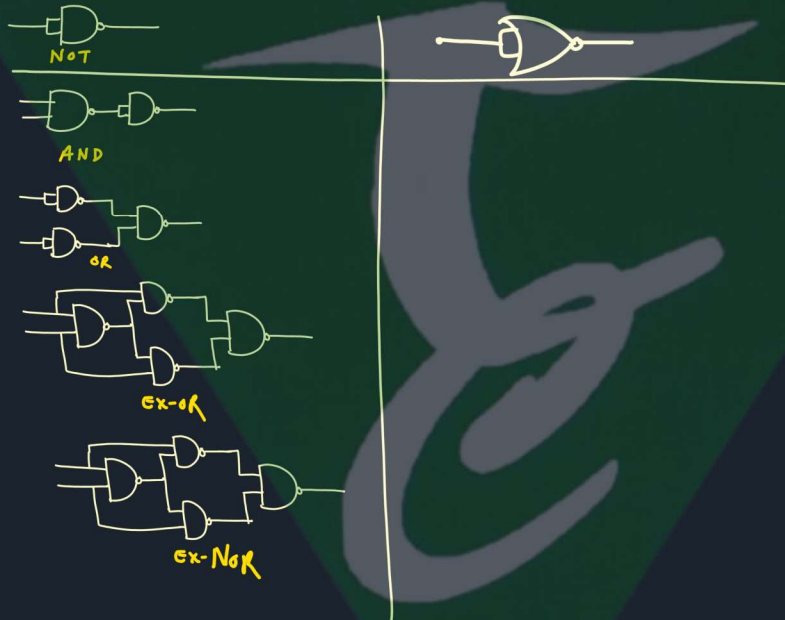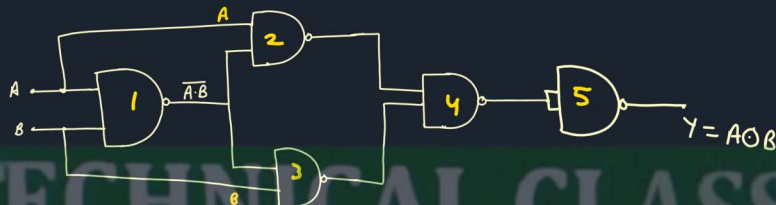


## Application of NOR Gate

### 1) NOT Gate by Using NOR




### 2) AND Gate by Using NOR

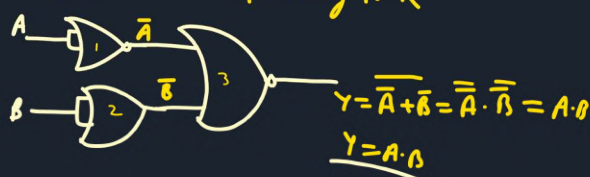

A	B	$Y = \overline{A+B}$
0	0	1 ✓
0	1	0
1	0	0
1	1	0 ✓

Bubble NOR = AND

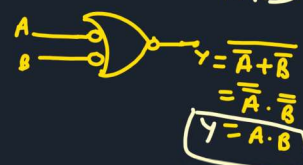




### 3) OR Gate by Using NOR



### 4) EX-OR Gate

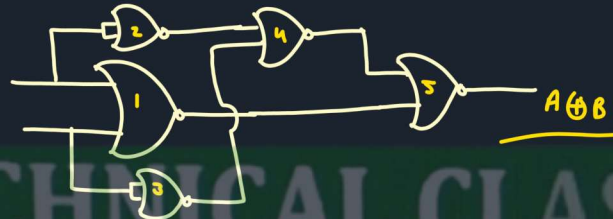

Logic Gate	No. of NAND	No. of NOR
Not	1	1
AND	2	3
OR	3	2
Ex-OR	4	5
Ex-NOR	5	4

V.V.9  
M.C.9

## Boolean function

The function of binary Variables is known as Boolean function or Boolean expression.

- There are two ways to express Boolean functions:→
- 1) Sum of Product (SOP)
  - 2) Product of Sum (POS)



## Sum of Product (SOP)

The Boolean expression in which Product terms are Sum together is known as SOP expression.

$$f(A, B, C) = \underbrace{A \cdot \bar{B} \cdot C}_{P.T} + \underbrace{A \cdot B}_{\bar{P.T}} + \underbrace{A \cdot \bar{C} + \bar{B} \cdot C}_{\bar{P.T}}$$

$$f(A, B, C) = A + B \cdot C + A \cdot \bar{C}$$

## TECHNICAL CLASSES

## Product of Sum (POS)

The Boolean expression in which Sum terms are multiplied together is known as Product of Sum.

$$f(A, B, C) = \underbrace{(A + \bar{B} + C)}_{S.T} \cdot \underbrace{(A + B)}_{\bar{S.T}} \cdot \underbrace{(B + C)}_{\bar{S.T}}$$

$$f(A, B, C) = \underbrace{(A + B)}_{\bar{S.T}} \cdot \underbrace{(\bar{A} + B + C)}_{\bar{S.T}} \cdot \underbrace{(A + \bar{B} + C)}_{\bar{S.T}}$$

$$\checkmark \underline{A \cdot B} + \underline{A \cdot \bar{B} \cdot C} + \underline{\bar{A} \cdot B \cdot C} \rightarrow \text{SOP}$$

$$\checkmark \underline{\bar{A} \cdot B} + \underline{A \cdot B \cdot C} + \underline{B \cdot \bar{C}} \rightarrow \text{SOP}$$

$$\checkmark \underline{(A + B + C)} \underline{(A + \bar{B} + C)} \underline{(\bar{A} + C)} \rightarrow \text{POS}$$





## Canonical Standard Product (Min term)

Standard Product or Min terms are those Which consists of all the binary variables either in normal form or

Complement form. The Value of min terms is logic '1'.  
It is denoted by  $m_i$ . Here  $i$  represents decimal equivalent value.  
If we have 3 binary variables (A, B, C) Then possible

Min terms are  $2^3 = \underline{8}$

i.e.  $f(A, B, C)$

Decimal No.	Binary Variables			Min terms ( $m_i$ )
	A	B	C	
0	0	0	0	$m_0 = \bar{A} \cdot \bar{B} \cdot \bar{C}$
1	0	0	1	$m_1 = \bar{A} \bar{B} C$
2	0	1	0	$m_2 = \bar{A} B \bar{C}$
3	0	1	1	$m_3 = \bar{A} B C$
4	1	0	0	$m_4 = A \bar{B} \bar{C}$
5	1	0	1	$m_5 = A \bar{B} C$
6	1	1	0	$m_6 = A B \bar{C}$
7	1	1	1	$m_7 = A B C$

## Canonical Standard SUM or Max term ( $M_i$ )

Standard Sum or Max terms are those that contains all variables either in normal form or in Complement form.

The Value of Max term is logic 0  $\left[ \begin{array}{l} 0 \rightarrow A \\ 1 \rightarrow \bar{A} \end{array} \right]$   $\begin{array}{l} \rightarrow \text{Normal} \\ \rightarrow \text{Complement} \end{array}$

Here Max term is represented as  $M_i$

If  $f(A, B, C)$  we have 3 variables:-



Decimal No	Binary Variables			Max term ( $M_i$ )
	A	B	C	
0	0	0	0	$M_0 = A+B+C$
1	0	0	1	$M_1 = A+B+\bar{C}$
2	0	1	0	$M_2 = A+\bar{B}+C$
3	0	1	1	$M_3 = A+\bar{B}+\bar{C}$
4	1	0	0	$M_4 = \bar{A}+B+C$
5	1	0	1	$M_5 = \bar{A}+B+\bar{C}$
6	1	1	0	$M_6 = \bar{A}+\bar{B}+C$
7	1	1	1	$M_7 = \bar{A}+\bar{B}+\bar{C}$

Conversion from SOP to Canonical SOP  
[ $x + \bar{x} = 1$ ]

$$\begin{aligned}
 ① \quad f(A, B, C) &= \underline{A} + \underline{B \cdot C} \\
 &= A \cdot (\underline{B + \bar{B}}) \cdot (\underline{C + \bar{C}}) + (A + \bar{A}) \cdot B \cdot C \\
 &= (A \cdot B + A \cdot \bar{B}) \cdot (C + \bar{C}) + A B C + \bar{A} B C \\
 &= \underline{A B C} + \underline{A \bar{B} C} + \underline{A B \bar{C}} + \underline{A \bar{B} \bar{C}} + \underline{A B C} + \underline{\bar{A} B C} \\
 &= m_7 + m_5 + m_6 + m_4 + m_3 + m_2 \\
 &= m_3 + m_4 + m_5 + m_6 + m_7 \\
 &= \sum m(3, 4, 5, 6, 7)
 \end{aligned}$$

$$2) \quad f(A, B, C) = \underline{A B} + \bar{A} B C$$

$$\begin{aligned}
 &= \underline{A B \cdot (C + \bar{C})} + \bar{A} B C \\
 &= \underline{A B C} + \underline{A B \bar{C}} + \bar{A} B C \\
 &\quad \begin{array}{ccc} \underline{111} & \underline{110} & \underline{011} \\ m_7 & m_6 & m_3 \end{array} \\
 &= m_3 + m_6 + m_7 \\
 &= \sum m(3, 6, 7)
 \end{aligned}$$



# Karnaugh's Map (K-Map)

The Simplification of Boolean expression Using Boolean algebra is an Unconditional Process. It doesn't follow any Specific Sequence. To overcome this Problem an alternative method is used. This alternative method is known as K-Map.

## TECHNICAL CLASSES

### Format of K-Map:-

A K-Map Consists of a number of Squares.

for  $n$ -Variables, Total number of Squares in map is  $2^n$ .

for example:-

2- Variables  $(A, B)$

No. of Squares  $= 2^2 = 4$

A \ B	0	1
	$\bar{A}\bar{B}$ $m_0$	$\bar{A}B$ $m_1$
0	$\bar{A}\bar{B}$ $m_0$	$\bar{A}B$ $m_1$
1	$A\bar{B}$ $m_2$	$AB$ $m_3$

for 3 Variables  $(A, B, C)$

No. of Squares  $= 2^3 = 8$ .

A \ BC	$\bar{B}\bar{C}$ $00$	$\bar{B}C$ $01$	$B\bar{C}$ $11$	$BC$ $10$
	$\bar{A}\bar{B}\bar{C}$ $m_0$	$\bar{A}\bar{B}C$ $m_1$	$\bar{A}B\bar{C}$ $m_2$	$\bar{A}BC$ $m_3$
0	$\bar{A}\bar{B}\bar{C}$ $m_0$	$\bar{A}\bar{B}C$ $m_1$	$\bar{A}B\bar{C}$ $m_2$	$\bar{A}BC$ $m_3$
1	$A\bar{B}\bar{C}$ $m_4$	$A\bar{B}C$ $m_5$	$AB\bar{C}$ $m_6$	$ABC$ $m_7$

### 3-Variables $f(A, B, C)$

A \ BC	$\bar{B}\bar{C}$ $00$	$\bar{B}C$ $01$	$B\bar{C}$ $11$	$BC$ $10$
	$\bar{A}\bar{B}\bar{C}$ $m_0$	$\bar{A}\bar{B}C$ $m_1$	$\bar{A}B\bar{C}$ $m_2$	$\bar{A}BC$ $m_3$
0	$\bar{A}\bar{B}\bar{C}$ $m_0$	$\bar{A}\bar{B}C$ $m_1$	$\bar{A}B\bar{C}$ $m_2$	$\bar{A}BC$ $m_3$
1	$A\bar{B}\bar{C}$ $m_4$	$A\bar{B}C$ $m_5$	$AB\bar{C}$ $m_6$	$ABC$ $m_7$







# Karnaugh's Map (K-Map)

The Simplification of Boolean expression Using Boolean algebra is an Unconditional process. It doesn't follow any specific sequence. To overcome this problem an alternative method is used. This alternative method is known as K-Map.

## TECHNICAL CLASSES

### Format of K-Map:-

A K-Map consists of a number of squares. For  $n$ -Variables, Total number of squares in map is  $2^n$ .

for example:-

2-Variables (A, B)

No. of squares =  $2^2 = 4$

A \ B	0	1
	$\bar{A}\bar{B}$ $m_0$	$\bar{A}B$ $m_1$
A 0	$\bar{A}\bar{B}$ $m_0$	$\bar{A}B$ $m_1$
A 1	$A\bar{B}$ $m_4$	$AB$ $m_5$

for 3 Variables (A, B, C)

No. of squares =  $2^3 = 8$

A \ BC	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$BC$ 11	$B\bar{C}$ 10
	$\bar{A}\bar{B}\bar{C}$ $m_0$	$\bar{A}\bar{B}C$ $m_1$	$\bar{A}B\bar{C}$ $m_2$	$\bar{A}BC$ $m_3$
A 0	$\bar{A}\bar{B}\bar{C}$ $m_0$	$\bar{A}\bar{B}C$ $m_1$	$\bar{A}B\bar{C}$ $m_2$	$\bar{A}BC$ $m_3$
A 1	$A\bar{B}\bar{C}$ $m_4$	$A\bar{B}C$ $m_5$	$AB\bar{C}$ $m_6$	$ABC$ $m_7$

### 3-Variables $f(A, B, C)$

A \ BC	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$BC$ 11	$B\bar{C}$ 10
	$\bar{A}\bar{B}\bar{C}$ $m_0$	$\bar{A}\bar{B}C$ $m_1$	$\bar{A}B\bar{C}$ $m_2$	$\bar{A}BC$ $m_3$
A 0	0 0 0 $\bar{A}\bar{B}\bar{C}$ $m_0$	0 0 1 $\bar{A}\bar{B}C$ $m_1$	0 1 1 $\bar{A}B\bar{C}$ $m_2$	0 1 0 $\bar{A}BC$ $m_3$
A 1	1 0 0 $A\bar{B}\bar{C}$ $m_4$	1 0 1 $A\bar{B}C$ $m_5$	1 1 1 $AB\bar{C}$ $m_6$	1 1 0 $ABC$ $m_7$



## 4- Variables $f(A, B, C, D)$

No. of square =  $2^4 = 16$

CD \ AB	$\bar{C}\bar{D}$		$\bar{C}D$		$C\bar{D}$		$CD$	
	00	01	11	10	00	01	11	10
00 $\bar{A}\bar{B}$	0000 $\bar{A}\bar{B}\bar{C}\bar{D}$ $m_0$	0001 $\bar{A}\bar{B}\bar{C}D$ $m_1$	0011 $\bar{A}\bar{B}C\bar{D}$ $m_2$	0010 $\bar{A}\bar{B}CD$ $m_3$	0100 $\bar{A}B\bar{C}\bar{D}$ $m_4$	0101 $\bar{A}B\bar{C}D$ $m_5$	0111 $\bar{A}BC\bar{D}$ $m_6$	0110 $\bar{A}BCD$ $m_7$
01 $\bar{A}B$	0100 $\bar{A}B\bar{C}\bar{D}$ $m_8$	0101 $\bar{A}B\bar{C}D$ $m_9$	0111 $\bar{A}BC\bar{D}$ $m_{10}$	0110 $\bar{A}BCD$ $m_{11}$	1100 $AB\bar{C}\bar{D}$ $m_{12}$	1101 $AB\bar{C}D$ $m_{13}$	1111 $ABC\bar{D}$ $m_{14}$	1110 $ABCD$ $m_{15}$
11 $AB$	1100 $AB\bar{C}\bar{D}$ $m_{12}$	1101 $AB\bar{C}D$ $m_{13}$	1111 $ABC\bar{D}$ $m_{14}$	1110 $ABCD$ $m_{15}$	1000 $A\bar{B}\bar{C}\bar{D}$ $m_{16}$	1001 $A\bar{B}\bar{C}D$ $m_{17}$	1011 $A\bar{B}C\bar{D}$ $m_{18}$	1010 $A\bar{B}CD$ $m_{19}$
10 $A\bar{B}$	1000 $A\bar{B}\bar{C}\bar{D}$ $m_{16}$	1001 $A\bar{B}\bar{C}D$ $m_{17}$	1011 $A\bar{B}C\bar{D}$ $m_{18}$	1010 $A\bar{B}CD$ $m_{19}$	0000 $\bar{A}\bar{B}\bar{C}\bar{D}$ $m_0$	0001 $\bar{A}\bar{B}\bar{C}D$ $m_1$	0011 $\bar{A}\bar{B}C\bar{D}$ $m_2$	0010 $\bar{A}\bar{B}CD$ $m_3$



## TECHNICAL CLASSES

### How to enter in k-map

→ Bring the given expression in Canonical SOP or POS in terms of minterms or maxterm respectively.

In Case of Canonical SOP expression, for each minterm is substituted by 1.

In Case of Canonical POS expression for each maxterm is substituted by 0.

### \* Draw k-map for given expression


Q:-  $f(A, B, C) = \bar{A}B + \bar{B}C + A\bar{C}$

$$\bar{A}B(C + \bar{C}) + (A + \bar{A})\bar{B}C + A\bar{C}(B + \bar{B})$$

$$\bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + A\bar{C}B + A\bar{C}\bar{B}$$

$$m_3 + m_2 + m_5 + m_1 + m_6 + m_4$$

$$\sum m(1, 2, 3, 4, 5, 6)$$

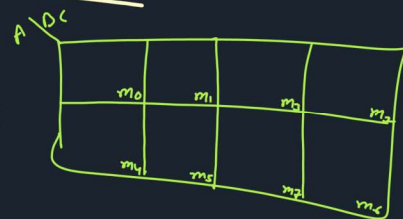

BC \ A	$\bar{B}\bar{C}$		$\bar{B}C$		$B\bar{C}$		$BC$	
	00	01	11	10	00	01	11	10
0 $\bar{A}$	0	1	1	0	0	1	1	0
1 $A$	1	1	1	1	1	1	1	1



$$2) f(A, B, C) = \sum m(0, 2, 3, 5, 7)$$

		BC			
		$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
A	$\bar{A}$	1 $m_0$		1 $m_2$	1 $m_3$
	$A$		1 $m_4$	1 $m_5$	

## TECHNICAL CLASSES

Procedure for grouping:-  $[2^0, 2^1, 2^2, \dots, 2^n]$   
 $[1, 2, 4, 8, 16, 32]$

- ① Only adjacent square can be grouped.
- ② The number of 1's or 0's in group must be 1, 2, 4, 8, ... So on.
  - Pair:- The group of two 1's or 0's
  - Quad:- The group of four 1's or 0's
  - Octate:- The group of eight 1's or 0's

⑧:- Simplify the given expression:-

$$1) f(A, B, C) = \sum m(0, 1, 3, 5, 7) = \bar{A}\bar{B} + C$$

		BC			
		$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
A	$\bar{A}$	1 $m_0$	1 $m_1$	1 $m_2$	
	$A$		1 $m_4$	1 $m_5$	

$$\bar{A}\bar{B} + C$$



Since 2011



# Technical Classes

तकनीकी शिक्षा के लिए No.1 संस्थान

Online -- Download  
Technical Classes  
App from PlayStore



## Offline & Online

- Polytechnic + B.Tech Semester
- For ME, CE, EE, ECE, CSE
- BCECE LEET Entrance Exam
- Polytechnic Entrance Exam
- SSC, RRB & All J.E. Exams

Contact – 93347 89450/ 91555 63777



Offline -- Technical Classes, Rajiv Nagar, Patna-24